

[Quality matter: This exam. measures ILOs a1 & a4, a5, a8, b2 & b3, b4 & b5.]

Psychrometric chart with student is allowed

Try the following questions.

Question no. 1 ( 5 points).

Define the following:

Coefficient of performance, Relative humidity – Latent heat – Sensible heat factor –  
Dew point temperature

Question no. 2 (4 points).

A 8 kg/s of an air stream at 10° C and 50% RH is mixed with 2 kg/s of an air stream at 35° C DBT and 0.014 kg w.v/kg d.a humidity ratio . find the DPT of the mixture.

Question no. 3 ( 6 points).

A 2 kg/s of air stream at 8 °C DBT and 5 °C WBT is heated sensibly up to 24° C DBT, then a 20 g w.v./s of moisture is added in a humidifying process. Calculate the sensible load and sensible heat factor.

Question no 4 ( 6 points).

A 60 cmm of moist air at a 32 °C DBT and 22 °C WBT enters a cooling and a dehumidifying coil. If it is desired that the air leaves the coil at 18 °C DBT and 16 °C WBT, determine the following:

- the effective surface temperature of the coil
- coil bypass factor
- the coil cooling capacity

Question no. 5 ( 10 points).

The space shown is to be conditioned has the following:

One storey space of height 4 m, west glass area 12 m<sup>2</sup>  
door 2.0mx 1.5 m

At the hour of calculation you have:

heat transmission through glass = 45 W/m<sup>2</sup>

solar heat gain through glass = 460 W/m<sup>2</sup>

CLF for solar heat gain 0.7


U for west wall 3.5 W/m<sup>2</sup>. °C and for roof  
of 2.5 W/m<sup>2</sup>. °C.

CLTD<sub>corr</sub> for west wall 13° C, and for roof 17° C.

Outside design conditions: 40 C DBT and 27° C WBT, Inside design conditions 25 °C and 50 % R.H., lighting 25 W/m<sup>2</sup>, CLF = 0.7, Occupancy 25 persons, sensible heat gain per person 75 W and latent heat gain per person 65 W, CLF = 0.6

Ventilation air 12 m<sup>3</sup>/hr per person and infiltration air 6 m<sup>3</sup>/min.

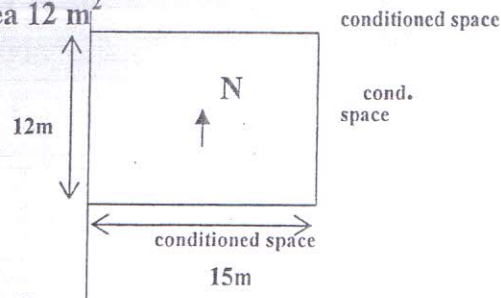Assume any missing data, calculate space cooling load.



Best wishes, Examiners: Prof. Ibrahim .M. Ismail + "The committee"



المادة: اللغة العربية



كلية الآداب

الزمن : ساعتان

قسم : اللغة العربية

الفرقة: الأولى - كلية الهندسة ( جميع الشعب )

امتحان الفصل الدراسي الأول يناير ٢٠١٥م

أجب عن الأسئلة الآتية :

( ١٠ درجات )

\*السؤال الأول :

- أ- " اللغة أفاظ يعبر بها كل قوم عن مقاصدهم " اشرح ذلك .  
ب- مثل لما يأتي : ( الاسم - الفعل - الحرف - همزة قطع - ألف الوصل -  
همزة متوسطة - همزة متطرفة - بعض علامات الترقيم ) .

( ١٥ درجة )

\*السؤال الثاني :

- قال الشاعر :

- ١- خدعوها بقولهم حسناء  
والغواني يغرهن الثناء  
٢- أتراها تناست اسمي لما  
كثرت في غرامها الأسماء  
٣- إن رأني تميل عني كأن  
لم يك بيني وبينها أشياء  
٤- نظرة فابتسامة فسلام  
فكلام فموعد فلقاء

أ- ماذا تعرف عن الشاعر ؟

- ب- اشرح الأبيات السابقة شرحاً أدبياً .  
ج- ضع عنواناً لها ، وما الغرض الشعري منها .  
د- استخرج من البيت الثالث صورة خيالية .

( ١٥ درجة )

\*السؤال الثالث :

- أ- درست سورتي : ( الفيل - والكوثر ) ما الهدف منهما ؟ وما نوع  
البلاغة في قوله تعالى : ( كعصف مأكول ) .  
ب- مثل لكل من : ( الإعلال - الإدغام - الإبدال ) .  
ج- ماذا تعرف عن علوم اللغة العربية ؟

مع أمنياتي التوفيق ،،،



## ملاحظات

## هامت

- الامتحان يقيس مهارة انتاج تصميمات معمارية تأخذ في الاعتبار اتساق النواحي الوظيفية والتشكيلية والانشائية وملاءمتها مع المحددات البيئية والمناخية للموقع.
- الامتحان مكون من صفتين.
- يرجى الالتزام بالنظافة والدقة في الرسم.
- يكون الحل النهائي في اللوحة البيضاء وليس في الشفافات.
- على الطالب فرض المعلومة التي يجدها ضرورية للتصميم إذا لزم الأمر.

يُراد إقامة "معهد عالي للهندسة" في أحد المواقع بمدينة أسيوط الجديدة على مساحة تبلغ ثمانية آلاف متر مربع (٨٠٠٠ م<sup>٢</sup>) كما يبين الكروكي المرفق، والمطلوب عمل التصميم المعماري للمعهد بتشكيل كتلة مميزة ونسبة بنائية لا تتجاوز ٤٠% من مساحة الأرض، ويراعى في التصميم أن يشتمل على العناصر التالية:

## أولاً: الفراغات التعليمية:

- عدد ١٥ فصل دراسي يسع كل منها ٥٠ طالب.
- عدد ٤ صالتي رسم تسع كل منها ٥٠ طالب.
- عدد ٢ مدرج يسع كل منها ١٠٠ طالب.
- عدد ١ قاعة مؤتمرات ومحاضرات تسع ٣٠٠ شخص.
- عدد ٢ معمل حاسب آلي مجهز لعدد ٥٠ طالب (ملحق به غرفة لأمين المعمل)
- مكتبة لعدد ٥٠ مستخدم.
- قاعة سيمينار تسع ٥٠ طالب.

## ثانياً: مبنى الورش:

- مبنى للورش بمساحة حوالي ٦٠٠ م<sup>٢</sup>، لها مدخل خاص للتخديم متصل بأحد الشوارع.
- غرف تغيير ملابس للعمال (عدد ١٠ كبائن + دواليب حفظ) وأدشاش (عدد ١٠)، ودورات مياه (عدد ٥).
- مخازن بمسطح اجمالي حوالي ٢٠٠ م<sup>٢</sup>.

## ثالثاً: الفراغات التكميلية:

## - الإدارة، وتشمل:

- مكتب عميد المعهد بمساحة ٥٠ متر مربع.
- مكتب رئيس مجلس ادارة المعهد بمساحة ٥٠ متر مربع.
- غرفة السكرتارية بمساحة ٢٠ متر مربع.
- غرفة اجتماعات بمساحة ٥٠ متر مربع.
- غرفة وكيل المعهد بمساحة ٢٠ متر مربع.
- غرف إدارية بمجموع مساحات ٢٠٠ متر مربع.
- عيادة طبية ملحق بها غرفة للعزل بمساحة مناسبة.
- قاعة رصد درجات بمساحة ٢٠ متر مربع.
- عدد ٨ مكاتب أعضاء هيئة التدريس بمساحة ٣٠ متر مربع لكل مكتب.
- عدد ٢ مكتب لمعاوني هيئة التدريس بمساحة ٢٠ متر مربع لكل مكتب.

## رابعاً: الفراغات الخدمية:

- كافتريا بمساحة ١٥٠ متر مربع ملحق بها أوفيس للتخديم عليها.
- مصلى للطلاب مع توفير مكان للوضوء.
- دورات مياه للطلاب، ودورات مياه لأعضاء هيئة التدريس والإدارة.
- مجموعة مخازن بمساحات متعددة بمجموع مساحة ٢٠٠ متر مربع.

## خامساً: الفراغات المفتوحة:


- فراغ مظلل بمساحة مناسبة ومناطق انتظار سيارات.
- ملعب خماسي بأبعاد ٢٥×١٥ م.

من فضلك اقلب الورقة

## المسطحات والمعايير اللازمة لكل عنصر طبقاً للاشتراطات

متوسط نصيب الطالب من المساحة	الفصل والمدرج	المكتبة ومعمل الحاسب الآلي	معمل الحاسب الآلي	قاعة المؤتمرات	صالة الرسم وقاعة السيمينار
١٠٢ - ١٠٤ م <sup>٢</sup>	١٠٧٥ م <sup>٢</sup>	١٠٧٥ م <sup>٢</sup>	١٠٧٥ م <sup>٢</sup>	١٠٠٠ م <sup>٢</sup>	٢٠٠٠ م <sup>٢</sup>

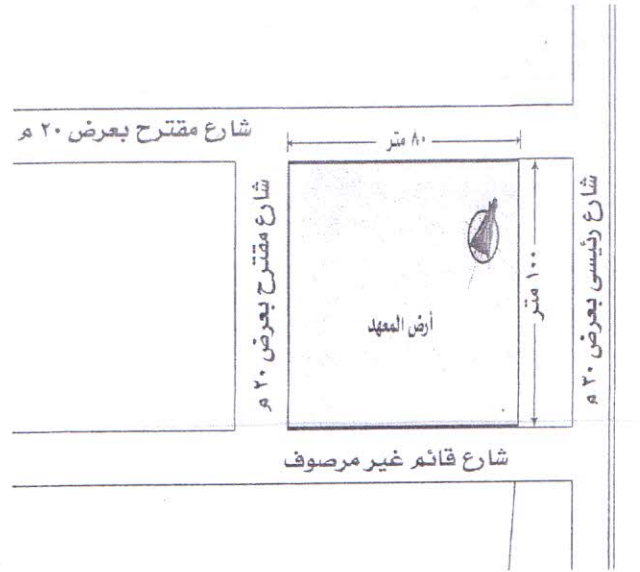يراعى توفير ١ دورة مياه لكل ٢٥ - ٣٠ طالب ، دورة مياه لكل ٢٠ عضو هيئة تدريس لا يقل عرض الطرقات فى الفراغات التعليمية عن ١٠٨ م تزيد إلى ٣ م فى حالة التخدير على الناحيتين الحد الأدنى لعدد السلالم التى تخدم أى مبنى هو سلمين (عرض القلبة لا يقل عن ١٠٥ م) لا تزيد مسافة السير بين أبعد فراغ والسلم عن ١٨٠٠٠ م



### كروكي الموقع العام

المطلوب توضيح فكرة الحل من خلال الرسومات التالية:

- المساقط الأفقية موضحاً عليها الطريقة الانشائية
  - قطاع معمارى رأسى (أو قطاعات) فى مبنى المعهد وقاعة المؤتمرات.
  - الواجهة الرئيسية.
  - الموقع العام.
  - توضيح التكوين الكتلي للمشروع من خلال لقطة منظورية.
  - أى رسومات أخرى يراها الطالب لازمة لتوضيح فكرة الحل.
- مقياس رسم ٢٠٠/١ أو ٤٠٠/١  
مقياس رسم ٢٠٠/١  
مقياس رسم ٢٠٠/١  
مقياس رسم ٤٠٠/١

توزع درجات الامتحان كالتالى:

- تحقيق المعدلات والعلاقات الوظيفية بشكل منطقي سليم ٢٥ درجات
- مراعاة الاعتبارات البيئية (التوجيه والاضاءة والتهوية). ٥ درجات
- تحقيق التميز التشكيلي للكتلة والمسقط الافقي والواجهة، وحسن التعبير عنها. ٢٥ درجات
- حسن اختيار الطريقة الانشائية وصحة التعبير عنها في المساقط والواجهة والقطاع. ٢٠ درجات
- تصميم ورسم واطهار الموقع العام ٥ درجات

دقة ونظافة الرسم وطريقة الإظهار يكون لها اعتبار عند التقويم

انتهت الأسئلة

دعواتنا بالتوفيق،، د. حنان رفعت محمد د. محمد رفاعه فهمي د. محمد محمد عزمي د. ريم وعظ أمجد + اللج

د. ريم وعظ أمجد

د. محمد محمد عزمي

د. محمد رفاعه فهمي

د. حنان رفعت محمد

الامتحان مكون من أربع صفحات، الإجابة في نفس ورقة الأسئلة، النهاية العظمى ١٠٠ درجة.  
الإجابة النهائية يجب أن تكون مكتوبة في المكان المخصص لها ولن يلتفت لغير ذلك.

**Question 1:**

a) The op-amp in the circuit of Fig.a is ideal. Calculate the following: (10 Marks)

- $I_1$
- $I_2$
- $I_3$
- $I_4$
- $V_o$

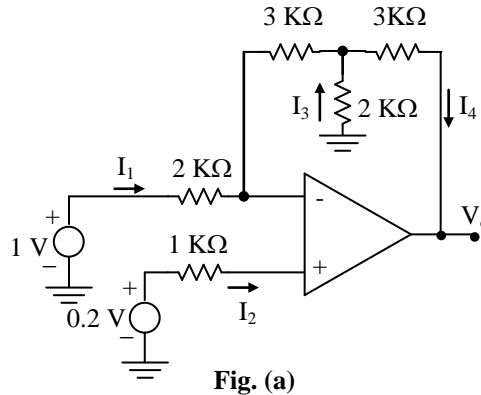


Fig. (a)

b) The switch in the circuit of Fig. (b) has been in position a for a long time. At  $t=0$  it moves to position b. Calculate the following: (10 Marks)

- $v_c(0^+)$
- $i_L(0^+)$
- $v_o(0^-)$
- $v_o(0^+)$
- $i_c(0^+)$

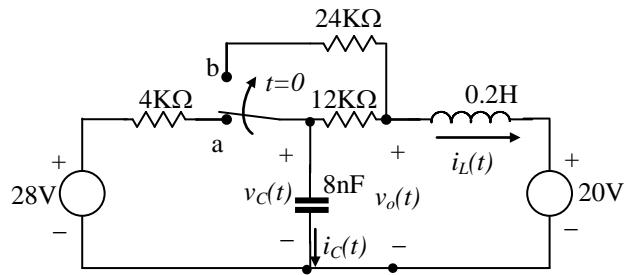


Fig. (b)

c) The circuit of Fig. (c) operates at radian frequency  $\omega = 100$  rad/sec. Find the mutual inductance  $M$ , the reflected impedance  $Z_r$  and the input impedance at port a-b. (6 Marks)

- $M$
- $Z_r$
- $Z_{in}$

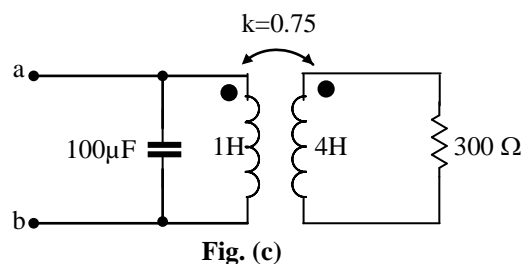


Fig. (c)

**Question 2:**

a) The switch in the circuit shown in Fig.a has been closed for a long time before it opens at  $t = 0$ . Find  $v(t)$  for  $0 \leq t \leq \infty$ . (10 Marks)

$i_L(0^+) =$

$v(0^+) =$

$v(\infty) =$

$\tau =$

$v(t) =$

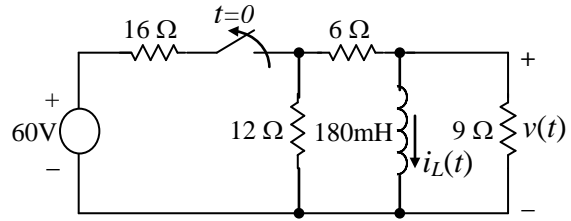


Fig. a

b) A balanced Y-connected load having an impedance of  $18\Omega$ /phase is connected in parallel with a balanced  $\Delta$ -connected load having an impedance of  $36\Omega$ /phase. The parallel loads are fed from lines having an impedance of  $2\Omega$ /line. The magnitude of the line-to-neutral voltage at the Y-load is 720 V. Calculate the following:

(10 Marks)

The magnitude of the line current

The magnitude of the phase current in the  $\Delta$ - load

The magnitude of the phase current in the Y- load

The magnitude of the line voltage at the sending end

The total power dissipated in the loads

c) For the two-port of Fig. (c), Calculate:

(8 Marks)

$z_{11} =$

$a_{21} =$

$h_{12} =$

$y_{22} =$

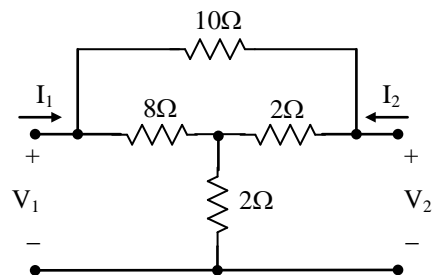


Fig. (c)

**Question 3:**


a) Find the first four Fourier coefficients of the voltage waveform of Fig.(a). (8 Marks)

$$a_0 = 6.7$$

$$C_1 = 5.5 \angle 150^\circ$$

$$C_2 = 2.76 \angle 30^\circ$$

$$C_3 = 0$$

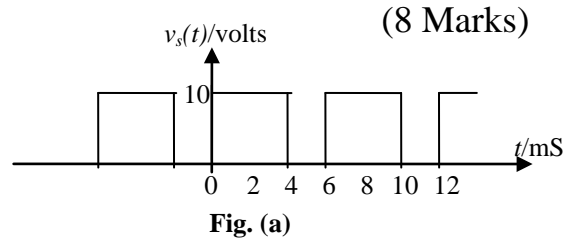


b) The voltage waveform of Fig.(a) is applied to the circuit of Fig. (b). Find the Fourier coefficients of the output voltage  $v_{ld}$ . (8 Marks)

$$V_{ld0} = 6 \text{ V}$$


$$V_{ld1} = 4.85 \angle 138.2^\circ \text{ V}$$

$$V_{ld2} = 2.29 \angle 7.3^\circ \text{ V}$$

$$V_{ld3} = 0$$

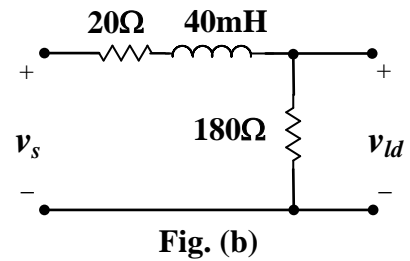

c) Sketch the Bode Diagram of the voltage transfer function:  $H_v(s) = \frac{1000(s + 100)}{(s + 10)(s + 1000)}$  (8 Marks)

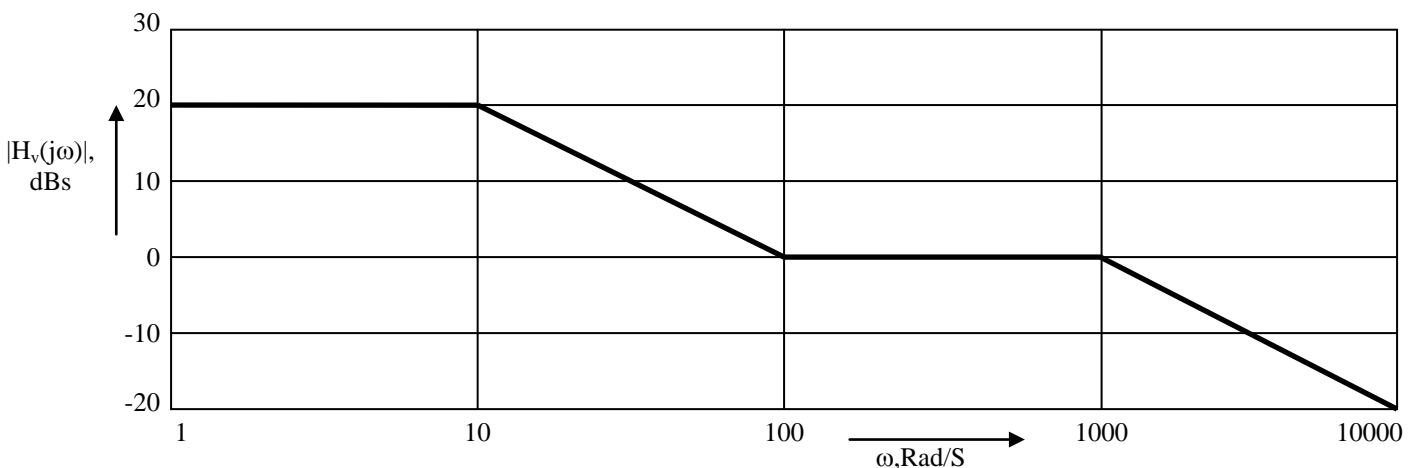

**Question 4:**

- a) Find the voltage transfer function and its poles and zeros for the circuit of Fig.a. (10 Marks)

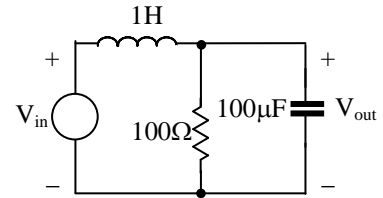


Fig.(a)

$$H_v(s) = \frac{10^4}{s^2 + 100s + 10^4}$$

**Poles:**  $-50 + j 86.6, -50 - j 86.6$

**Zeros:**  $\infty, \infty$

- b) The switch in the circuit shown in Fig.b has been opened for a long time before it closes at  $t = 0$ . Find  $v_c(t)$  for  $t \geq 0$ . (12 Marks)

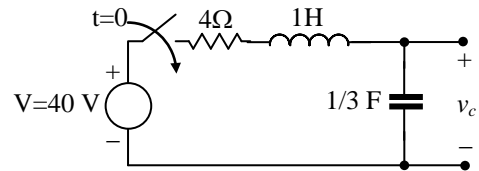


Fig. (b)

$$V_C(s) = \frac{120}{s(s^2 + 4s + 3)}$$

$$= \frac{120}{s(s+1)(s+3)}$$

$$= \frac{40}{s} - \frac{60}{s+1} + \frac{20}{s+3}$$

$$v_c(t) = [40 - 60e^{-t} + 20e^{-3t}]u(t) V$$



الامتحان مكون من أربع صفحات، الإجابة في نفس ورقة الأسئلة، النهاية العظمى ١٠٠ درجة.  
الإجابة النهائية يجب أن تكون مكتوبة في المكان المخصص لها ولن يلتفت لغير ذلك.

**Question 1:**

a) The voltage waveform  $v_g$  shown in Fig.(a-1) is applied to the circuit of Fig.(a-2). Sketch  $v_o$  and  $v_1$  versus  $t$ , assuming ideal op-amp. (10 Marks)

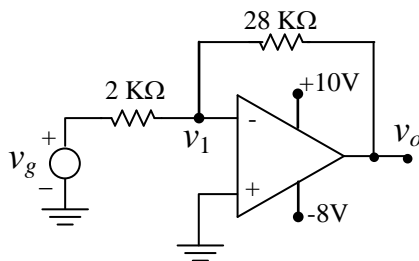


Fig. (a-2)


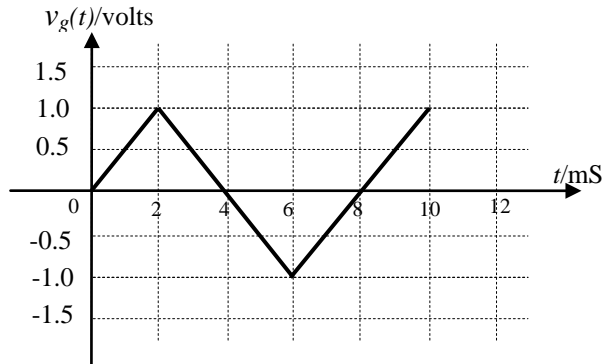
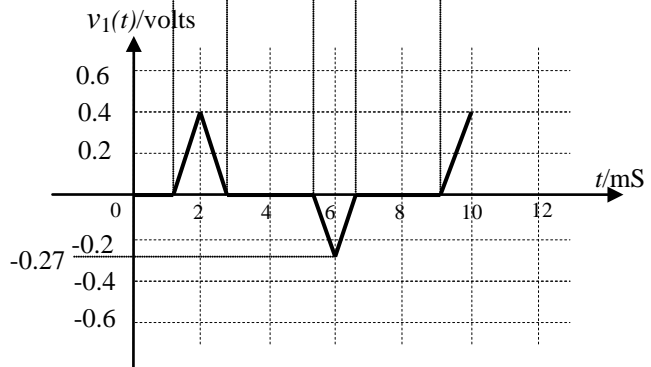


Fig. (a-1)

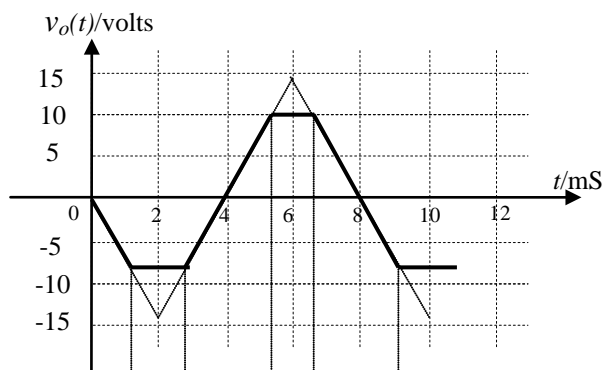

b) The switch in the circuit shown in Fig.b has been opened for a long time before it closes at  $t = 0$ . Find  $i_o(t)$  for  $0 \leq t \leq \infty$ . (10 Marks)

$i_L(0^+) =$  1 A

$i_o(0^+) =$  0.5 A

$i_o(\infty) =$  1.5 A

$\tau =$  0.5 S

$i_o(t) =$   $1.5 - e^{-2t} \text{ A}, 0 \leq t \leq \infty$

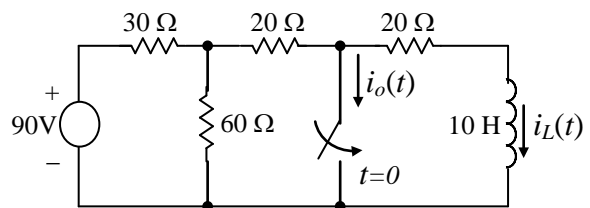


Fig. b

**Question 2:**

- a) i) Write the two mesh equations for the circuit of Fig.(a) and solve them to find  $I_1$ ,  $I_2$ , and the power dissipated in  $R_L$ . (10 Marks)
- ii) Find the Thevenin equivalent circuit at the output port, hence find the value of  $R_L$  that consumes maximum power, and the value of this power. (6 Marks)

The first mesh equation

$$80 I_1 - 20 I_2 + V_1 = 400$$

The second mesh equation

$$-20 I_1 + 105 I_2 - V_2 = 0$$

- $I_1 =$  0.25 A
- $I_2 =$  1 A
- $P_L =$  85 W
- $R_{Th} =$  15Ω
- $V_{Th} =$  100 V
- $P_{max} =$  166.7 W

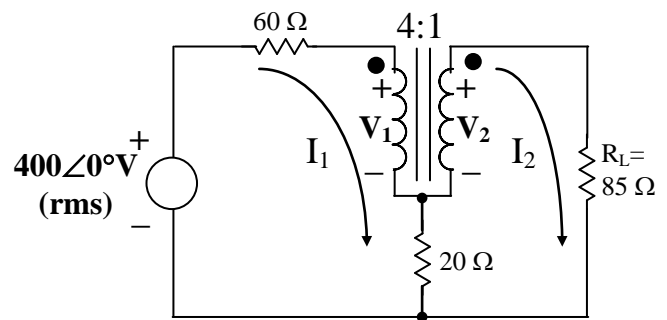


Fig. (a)

- b) A three-phase Y-connected +ve sequence source having the phase voltage  $V_a=220\angle 0^\circ\text{V}$ . The source resistance is  $2\ \Omega/\text{Phase}$ . The source supplies a balanced  $\Delta$ -connected load having a load impedance of  $36\angle 30^\circ\Omega/\text{Phase}$ . The three lines connecting the source to the load have a resistance of  $1\ \Omega/\text{Line}$ . Find the following: (10 Marks)

The magnitude of the line current 15 A

The magnitude of the phase current in the  $\Delta$ - load 8.66 A

The magnitude of the line voltage at the sending end 334.5 V

The magnitude of the line voltage at the load 312 V

The total active power dissipated in the load 7015 W

**Question 3:**


a) Find the mean value, RMS value, period, and fundamental frequency in Hz, for the voltage waveform of Fig.(a). (8 Marks)

Mean value = 6.67 V

RMS value = 8.165 V

Period = 6 mS

Fundamental frequency = 166.7 Hz

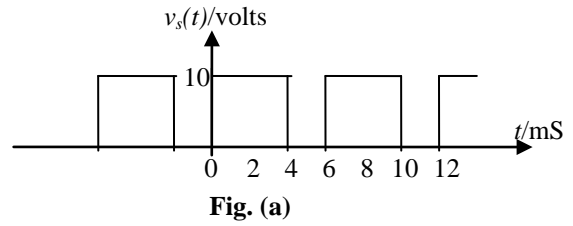

- b) i) What is the type of filter shown Fig.(b)? (2 Marks)  
 ii) Write the voltage transfer function  $H_v(s)$  of that filter. (2 Marks)  
 iii) Find the filter cut-off frequency  $f_c$ . (2 Marks)  
 iv) What is the maximum value of  $H_v(s)$ ? (2 Marks)  
 v) At what frequency will  $|H_v(s)|$  equals half its maximum value? (2 Marks)


type of filter High pass filter

$H_v(s) =$   $\frac{0.9}{s + 10^4}$


$f_c =$  1592 Hz

$H_v(s)|_{\max} =$  0.9

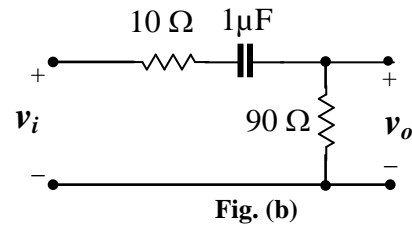Frequency of  $\frac{1}{2}$  max value = 919 Hz




c) Sketch the Bode Diagram of the voltage transfer function:  $H_v(s) = \frac{20000 s}{(s + 20)(s + 1000)}$  (6 Marks)

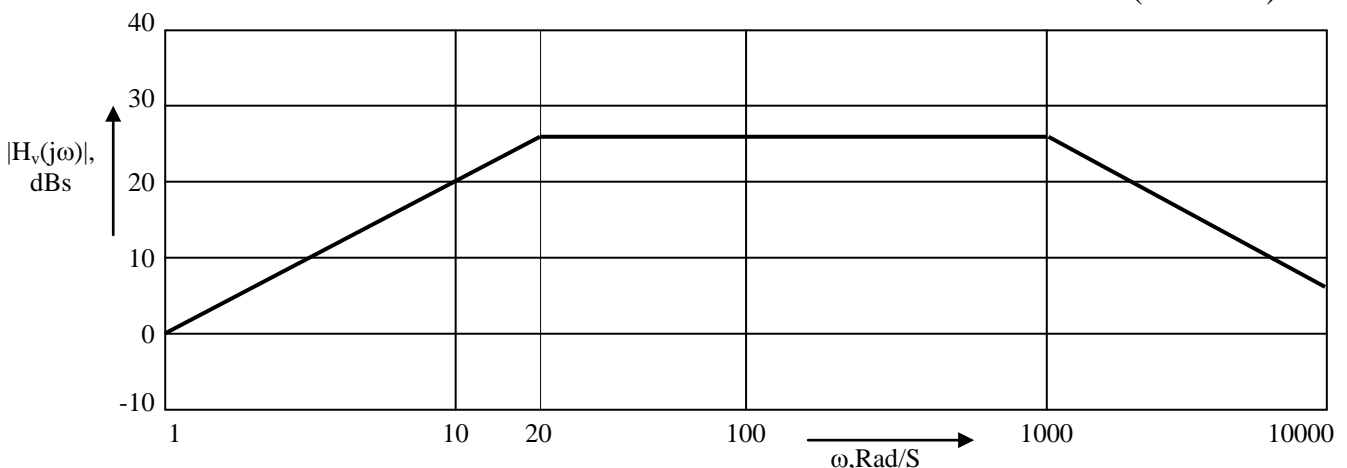

**Question 4:**

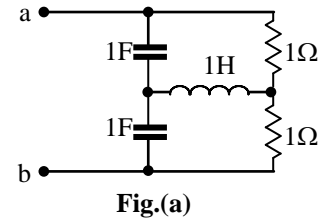- a) Find the s-domain expression of the input impedance seen looking into the terminals a, b of the circuit of Fig.(a). Find also the poles and zeros of that impedance. (10 Marks)




$$Z_{in}(s) = \frac{2s^2 + 3s + 1}{2s(s^2 + s + 1)}$$

**Poles**    **0, (-0.5 + j 0.866), (-0.5 - j 0.866)**

**Zeros**    **-0.5, -1, ∞**

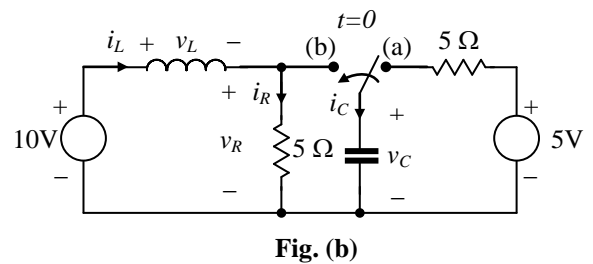- b) The switch in the circuit of Fig. (b) is moved from (a) to (b) at  $t = 0$ . Find the following currents and voltages: (12 Marks)



$i_R(0^-)$     **2 A**

$i_R(0^+)$     **1 A**

$i_C(0^+)$     **1 A**

$i_L(0^+)$     **2 A**

$v_L(0^+)$     **5 V**

$v_R(\infty)$     **10 V**

- c) The  $a$ -parameters of a certain two-port are  $a_{11}= 3$ ,  $a_{12}= 10 \Omega$ ,  $a_{21}= 0.5 S$ ,  $a_{22}= 2$ . Find the  $h$ -parameters. (8 Marks)

$h_{11} =$     **5  $\Omega$**

$h_{12} =$     **-0.5**

$h_{21} =$     **0.5**

$h_{22} =$     **0.25 S**

\*\*\*\*\*

أطيب التمنيات بالتوفيق  
أ.د. مجدى مفيد دوس

\*\*\*\*\*



الامتحان مكون من أربع صفحات، الإجابة في نفس ورقة الأسئلة، النهاية العظمى ١٠٠ درجة.  
الإجابة النهائية يجب أن تكون مكتوبة في المكان المخصص لها ولن يلتفت لغير ذلك.

**Question 1:**

a) The op-amp in the non-inverting amplifier of Fig.a is ideal. Find the  $i_1$ ,  $i_2$ ,  $v_1$ ,  $i_3$ ,  $v_o$ , and  $i_o$ .

(12 Marks)

- $i_1 = 0.1 \text{ mA}$
- $i_2 = 0.2 \text{ mA}$
- $v_1 = 4 \text{ V}$
- $i_3 = 0.2 \text{ mA}$
- $v_o = 8 \text{ V}$
- $i_o = 0.4 \text{ mA}$

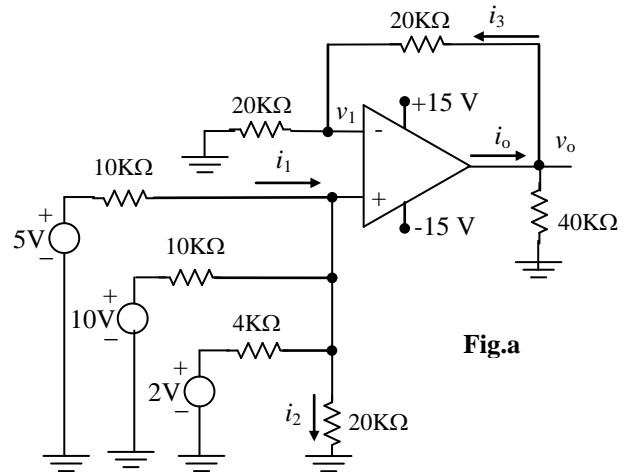


Fig.a

b) The switch in the circuit shown in Fig.b has been in position (a) for a long time before it moves to (b) at  $t = 0$ . After 5 mSec, the inductance current  $i_L$  dropped to 80% of its initial value. Find the value of  $L$ .

(12 Marks)

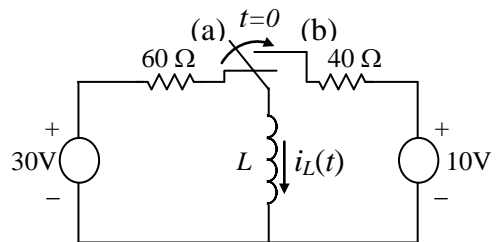


Fig. b

$i_L(0^+) = 0.5 \text{ A}$

$i_L(\infty) = 0.25 \text{ A}$

$i(t) = 0.25 + 0.25e^{-t/\tau}$

$i(5\text{mS}) = 0.25 \left( 1 + e^{-\frac{5}{\tau}} \right) = 0.4 \text{ A}$

$\tau = 9.788 \text{ mS}$

$L = 392 \text{ mH}$

**Question 2:**

a) A three-phase  $\Delta$ -connected +ve sequence source having the phase voltage  $V_{ab}=220\angle 0^\circ\text{V}$ . The source resistance is  $1\ \Omega$  / Phase. The source supplies an unbalanced  $\Delta$ -connected resistive load having  $R_{ab} = 10\Omega$ ,  $R_{bc} = 9\Omega$  and  $R_{ca} = 21\Omega$ . The three lines connecting the source to the load have negligible resistance. The load power is measured using the two wattmeter method. The first wattmeter  $W_1$  is connected between lines A and B, while the second one  $W_2$  is connected between lines C and B. Find the following: (12 Marks)

The phase current $\overline{I_{AB}}$ at the load =	<b>20<math>\angle 0^\circ</math> A</b>
The Line current $\overline{I_A}$ =	<b>26.46<math>\angle -19.1^\circ</math> A</b>
The line voltage $\overline{V_{AB}}$ at the load =	<b>200<math>\angle 0^\circ</math> V</b>
The reading of $W_1$ =	<b>5 KW</b>
The reading of $W_2$ =	<b>5.35 KW</b>
The total power dissipated in the load =	<b>10.35 KW</b>

- b) i) Find the voltage transfer function of the circuit of Fig.(b). (6 Marks)  
 ii) Find the poles and zeros of the transfer function. (4 Marks)  
 iii) Find the magnitude of the transfer function at  $\omega = 5$  Rad/Sec. (2 Marks)

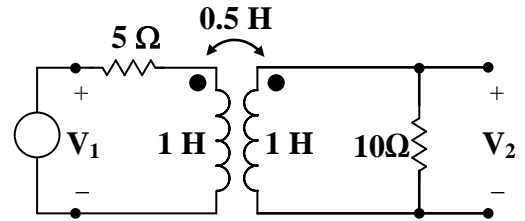


Fig. (b)

$$(2s + 10)I_1 + s I_2 = 2 V_1$$

$$s I_1 + (2s + 20)I_2 = 0$$

$$H_v(s) = \frac{20s}{3s^2 + 60s + 200}$$

Poles: **- 4.23 , - 15.77 S<sup>-1</sup>**


Zeros: **0,  $\infty$**

$|H_v(j5)| =$  **0.308**

**Question 3:**

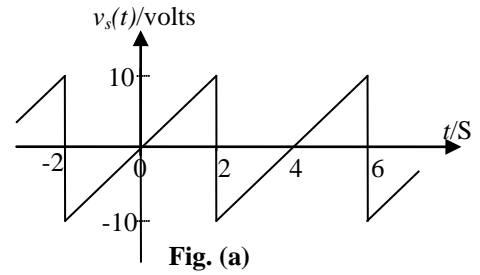
a) Find the first four non-zero terms of the Fourier series of the periodic voltage waveform shown in Fig.(a). (8 Marks)

$$\begin{aligned}
 b_n(t) &= \frac{2}{T} \int_{-\frac{T}{2}}^{\frac{T}{2}} 5t \cdot \sin(n\omega_0 t) dt = -\frac{10}{n\omega_0 T} \int_{-\frac{T}{2}}^{\frac{T}{2}} t \cdot d\cos(n\omega_0 t) \\
 &= -\frac{5}{n\pi} \left[ t \cdot \cos(n\omega_0 t) - \frac{1}{n\omega_0} \sin(n\omega_0 t) \right]_{-\frac{T}{2}}^{\frac{T}{2}} \\
 &= -\frac{5}{n\pi} \left[ t \cdot \cos(n\omega_0 t) - \frac{1}{n\omega_0} \sin(n\omega_0 t) \right]_{-\frac{T}{2}}^{\frac{T}{2}} = -\frac{20}{n\pi} \cos(n\pi) \\
 b_1 &= 20/\pi, b_2 = -10/\pi, b_3 = 20/3\pi, b_4 = -5/\pi,
 \end{aligned}$$



b) There is no energy stored in the circuit of Fig.b at the time the switch is closed:

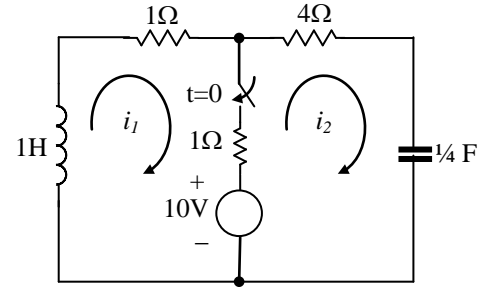- i) Write the two mesh equations of the circuit. (4 Marks)
- ii) Find  $I_1(s)$  and  $I_2(s)$ . (4 Marks)
- iii) Find  $i_1(t)$  and  $i_2(t)$ . (4 Marks)



The first s-domain mesh equation:  
 $(s^2 + 2s) I_1 - s I_2 = -10$

The second s-domain mesh equation:  
 $-s I_1 + (5s + 4) I_2 = 10$


$$I_1(s) = \frac{-8}{s(s + 1.6)} = \frac{5}{s + 1.6} - \frac{5}{s}$$

$$I_2(s) = \frac{2}{s + 1.6}$$

$$i_1(t) = [-5 + 5e^{-1.6t}]u(t)A$$

$$i_2(t) = 2e^{-1.6t}u(t)A$$

c) Sketch the Bode Diagram of the voltage transfer function:  $H_v(s) = \frac{1000(s + 200)}{(s + 20)(s + 1000)}$  (6 Marks)

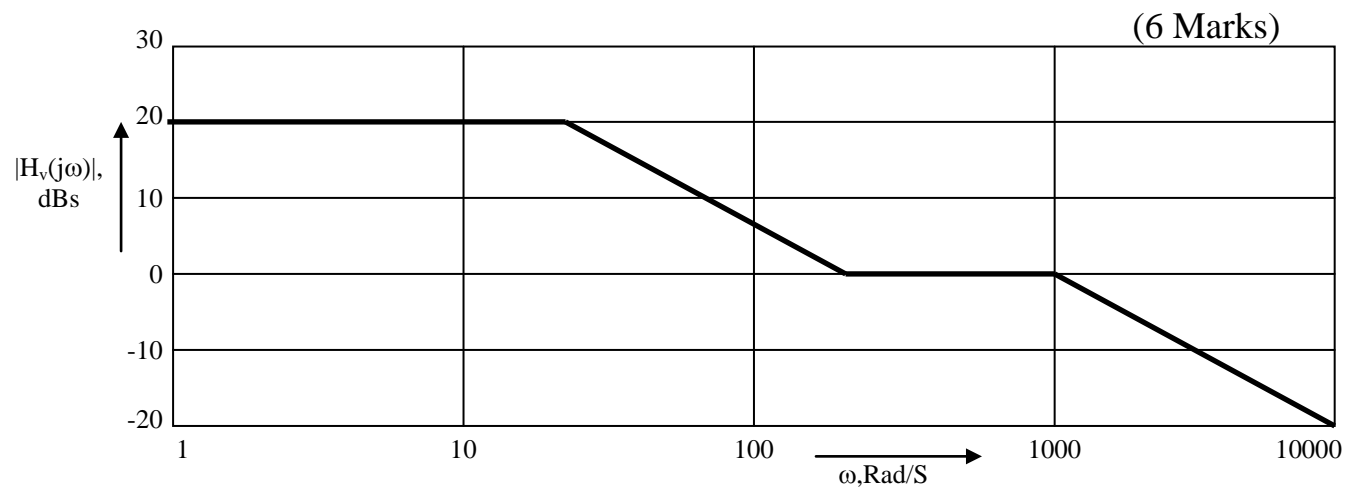

**Question 4:**

a) The switch in the circuit of Fig. (a) has been open a long time before closing at  $t = 0$ .

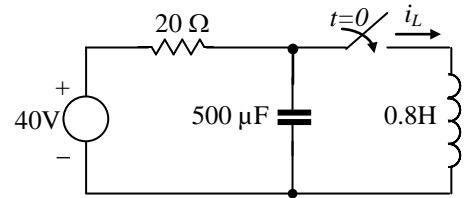


Fig. (a)

- i) Find  $i_L(0^+)$ ,  $i_L(\infty)$ ,  $v_L(0^+)$ ,  $\frac{di_L}{dt}(0^+)$ . (8 Marks)
- ii) Write the differential equation of  $i_L(t)$ . (2 Marks)
- iii) Write the characteristic equation and find its roots. (4 Marks)
- iv) The constants in the solution for  $i_L(t)$ . (2 Marks)
- v) Find  $i_L(t)$  for  $t \geq 0$ . (2 Marks)

$i_L(0^+) = 0$

$i_L(\infty) = 2 \text{ A}$

$v_L(0^+) = 40 \text{ V}$

$\frac{di_L}{dt}(0^+) = \frac{v_L(0^+)}{L} = 50 \text{ A/S}$

the differential equation of  $i_L(t)$   

$$\frac{d^2 i}{dt^2} + \frac{1}{RC} \cdot \frac{di}{dt} + \frac{1}{LC} \cdot i = \frac{2}{LC}$$

the characteristic equation  

$$s^2 + 100 s + 2500 = 0$$

roots of the characteristic equation  

$$s_1 = s_2 = -50$$

The constants  

$$D_1 = -50, D_2 = -2$$

$$i_L(t) = 2 - (50 t + 2) e^{-50t}$$

b) Find the  $h$  parameters of the circuit shown in Fig.(b). (8 Marks)

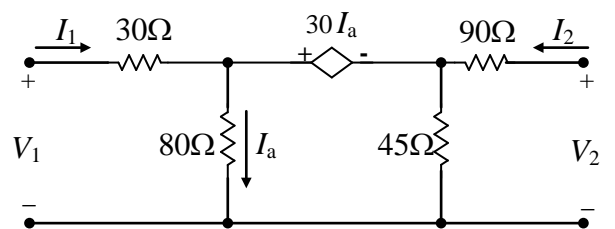


Fig.(b)

$h_{11} = 60 \Omega$

$h_{12} = 0.333$

$h_{21} = -0.21$

$h_{22} = 8.8 \text{ mS}$

\*\*\*\*\*

أطيب التمنيات بالتوفيق  
 أ.د. مجدى مفيد دوس

\*\*\*\*\*





الامتحان مكون من أربع صفحات، الإجابة في نفس ورقة الأسئلة، النهاية العظمى ١٠٠ درجة.  
الإجابة النهائية يجب أن تكون مكتوبة في المكان المخصص لها وخطوات الحل تكون في الصفحة المقابلة.

**Question #1: (12 Points)**

The two op amps in the circuit in Fig.1 are ideal. Calculate  $v_{o1}$ ,  $v_{o2}$ ,  $i_{o1}$  and  $i_{o2}$ .

- $v_{o1} = 2.125 \text{ V}$
- $v_{o2} = 2.5 \text{ V}$
- $i_{o1} = 0.25 \text{ mA}$
- $i_{o2} = 1.75 \text{ mA}$

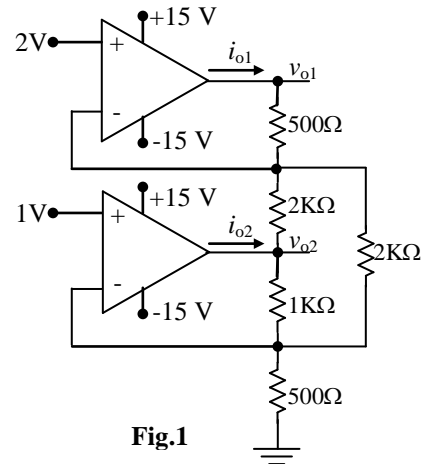


Fig.1

**Question #2: (16 Points)**

The voltage waveform shown in Fig.2(a) is applied to the circuit of Fig.2(b). The initial voltage on the capacitor is zero. Calculate and sketch  $v_o(t)$ .


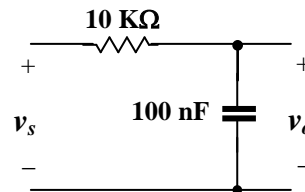
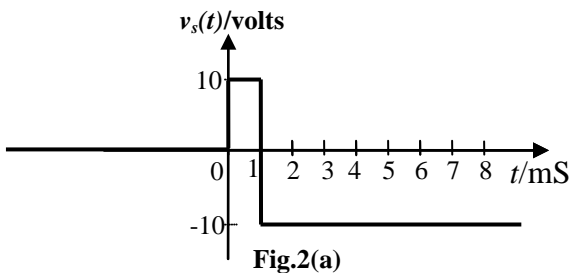


Fig.2(b)

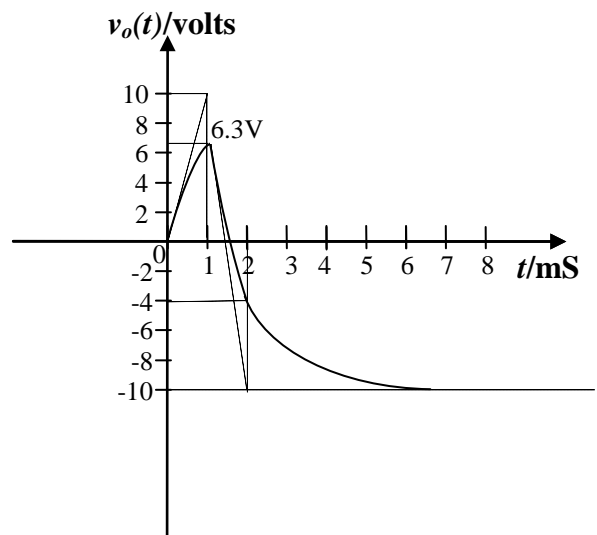- $v_o(0^+) = 0$
- $v_o(\infty)_1 = 10 \text{ V}$
- $\tau = 1 \text{ mS}$
- $v_o(t) = 10(1 - e^{-t}) \text{ V}$   
 $0 \leq t \leq 1 \text{ mS}$
- $v_o(1\text{mS}) = 6.3 \text{ V}$
- $v_o(\infty) = -10 \text{ V}$
- $v_o(t) = -10 + 16.3 e^{-(t-1)} \text{ V}$   
 $1\text{mS} \leq t \leq \infty$



**Question #3: (10 Points)**

The voltage response for the circuit in Fig.3 is known to be  $v(t) = D_1 t e^{-500t} + D_2 e^{-500t}$ ,  $t \geq 0$ .

The initial current in the inductor ( $I_0$ ) is -10 mA, and the initial voltage on the capacitor ( $V_0$ ) is 8 V. The inductor has an inductance of 4 H.

- Find the values of  $R$ ,  $C$ ,  $D_1$  and  $D_2$ .
- Find  $i_C(t)$  for  $t \geq 0^+$ .

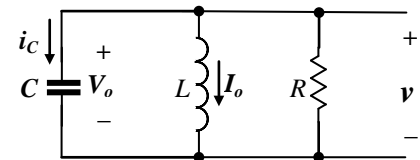


Fig.3

$$R = 1 \text{ K}\Omega$$

$$C = 1 \text{ }\mu\text{F}$$

$$D_1 = 6000 \text{ V/S}$$

$$D_2 = 8 \text{ V}$$

$$i_C(t) = -3 t e^{-500t} + 2 \times 10^{-3} e^{-500t} \text{ A}$$

**Question #4: (12 Points)**

A three-phase Y-connected +ve sequence source having the phase voltage  $V_a = 260 \angle 0^\circ \text{ V}$ . The source resistance is  $1 \text{ }\Omega/\text{Phase}$ . The source supplies a balanced  $\Delta$ -connected load having an impedance of  $(27 + j15) \text{ }\Omega/\text{Phase}$ . The three lines connecting the source to the load have a resistance of  $2 \text{ }\Omega/\text{Line}$ . Find the following:

The Line current $\overline{I_A}$ =	$20 \angle -22.6^\circ \text{ A}$
The phase current $\overline{I_{AB}}$ at the load =	$11.55 \angle 7.4^\circ \text{ A}$
The line voltage $\overline{V_{AB}}$ at the load =	$356.7 \angle 36.4^\circ \text{ V}$
The phase voltage $\overline{V_a}$ at the source terminals =	$241.7 \angle 1.8^\circ \text{ V}$
The line voltage $\overline{V_{ab}}$ at the source terminals =	$418.6 \angle 31.8^\circ \text{ V}$
The total power dissipated in the load =	$10.8 \text{ KW}$

**Question #5: (12 Points)**

The sinusoidal voltage source in the circuit of Fig.5 is operating at a frequency of 200 Krad/s. The coefficient of coupling is adjusted until the peak amplitude of  $i_1$  is pure real.

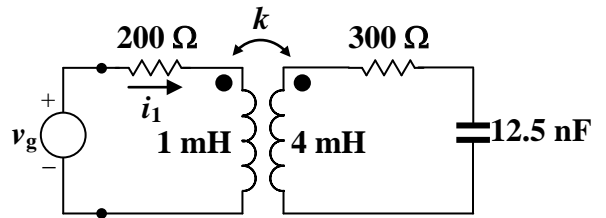


Fig.5

- a) What is the value of  $k$ ?
- b) What is the peak amplitude of  $i_1$  if  $v_g = 112 \cos(2 \times 10^5 t) \text{ V}$  ?

$$Z_r = 64 k^2(3 - j4)$$

$$i_1 = \frac{v_g}{200 + j200 + 64k^2(3 - j4)}$$

$$4 \times 64 k^2 = 200$$

$$k = 0.88$$

$$i_{1(\text{peak})} = 0.32 \text{ A}$$

**Question #6: (12 Points)**

Find the voltage transfer function and its poles and zeros for the circuit of Fig.6. If we consider this circuit as a bandpass filter, find approximate values for its magnitude transfer function at  $\omega = 0$  and at its central frequency. Find also the value of its bandwidth.

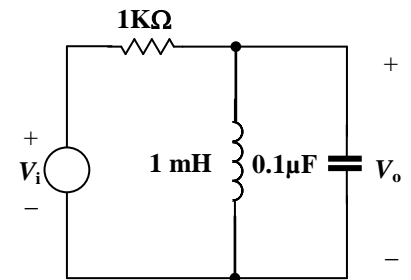


Fig.6

$$H_v(s) = \frac{10^4 s}{s^2 + 10^4 s + 10^{10}}$$

Poles:  $-5 \pm j 99.87 \text{ Krad/s}$

Zeros:  $0, \infty$

$$|H_v(0)| = 0$$

$$|H_v(j\omega_0)| = 1$$

$$\text{BW} = 10^4 \text{ rad/s}$$

**Question #7: (12 Points)**

There is no energy stored in the circuit of Fig.7 at the time the current source is energized. Use the Laplace Transform to find the nodal voltages.

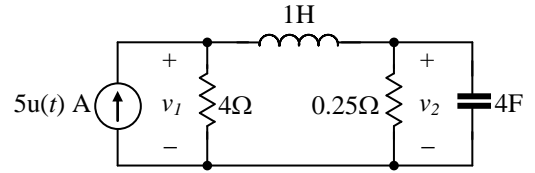


Fig.7

Eq. (1):  $(s + 4)V_1 - 4 V_2 = 20$

Eq. (2):  $-V_1 + (4s^2 + 4s + 1) V_2 = 0$

$V_1(s) = \frac{20(s^2 + s + 0.25)}{s(s^2 + 5s + 4.25)}$

$V_2(s) = \frac{5}{s(s^2 + 5s + 4.25)}$

$v_1(t) = 1.18 - 16.38e^{-1.09t} + 35.2e^{-3.91t}$

$v_2(t) = 1.18 - 1.63e^{-1.09t} + 0.45e^{-3.91t}$

**Question #8: (6 Points)**

A periodic voltage having a period of  $10\pi \mu\text{S}$  is given by the following Fourier series:

$$v_g = 150 \sum_{n=1,3,5,\dots}^{\infty} \frac{1}{n} \sin \frac{n\pi}{2} \cos n\omega_o t \text{ V}$$

This periodic voltage is applied to the circuit shown in Fig.8. Find the amplitude and phase angle of the first three components of  $v_o$ .

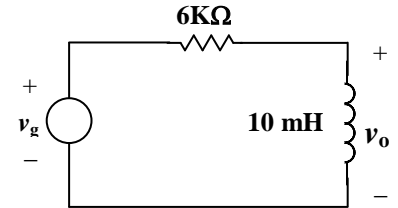


Fig.8

$\omega_o = 2\pi/T = 200 \text{ Krad/s}$

$v_g = 150 \cos \omega_o t - 50 \cos 3\omega_o t + 30 \cos 5\omega_o t$

$v_o = \frac{j2n}{6 + j2n} v_g$

$V_{o1} = 47.43 \angle 71.6^\circ \text{ V}$

$V_{o3} = 35.34 \angle -135^\circ \text{ V}$

$V_{o5} = 25.73 \angle 31^\circ \text{ V}$

**Question #9: (8 Points)**

Find the s-domain expressions for the  $a$  parameters of the two-port circuit shown in Fig.9.

$a_{11} = 1 + \frac{1}{4s}$

$a_{12} = s + \frac{1}{4} + \frac{1}{s}$

$a_{21} = \frac{1}{4}$

$a_{22} = \frac{s}{4} + 1$

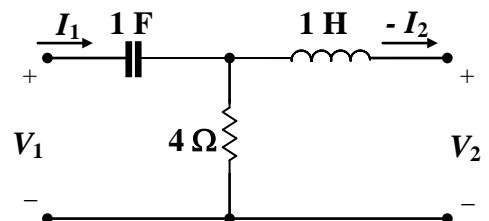


Fig.9

\*\*\*\*\*

أطيب التمنيات بالتوفيق  
أ.د. مجدى مفيد دوس

\*\*\*\*\*



الامتحان مكون من أربع صفحات، الإجابة في نفس ورقة الأسئلة، النهاية العظمى ١٠٠ درجة.  
الإجابة النهائية يجب أن تكون مكتوبة في المكان المخصص لها وخطوات الحل تكون في الصفحة المقابلة.

**Attempt all questions, full mark: 100 Points**


**Time: 3 Hours**

**Question #1: (12 Points)**

The nonlinear device ( $D$ ) used in the circuit of Fig.1 has a characteristic given by:

$$i_d = I e^{\alpha v_d}, \text{ where } v_d > 0 \text{ and } i_d > 0.$$

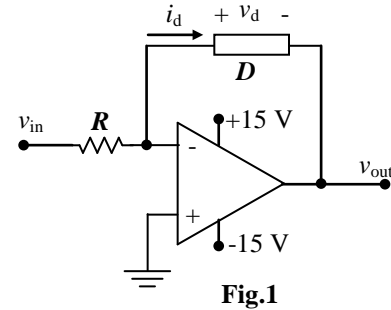Assuming ideal operational amplifier, and that the nonlinear device is operating with positive values of  $v_d$  and  $i_d$ ,



- find an expression relating  $v_{out}$  to  $v_{in}$ . (8 Points)
- if  $I = 0.5 \mu\text{A}$ ,  $\alpha = 40 \text{ V}^{-1}$  and  $R = 1 \text{ K}\Omega$ , find  $v_{out}$  for  $v_{in} = 5 \text{ V}$ . (4 Points)

$$v_{out} = -\frac{1}{\alpha} \ln \frac{v_{in}}{RI}$$

$$v_{out} \text{ (for } v_{in} = 5 \text{ V)} = -230 \text{ mV}$$

**Question #2: (14 Points)**

The two switches (a) and (b) in the circuit of Fig.2 operate simultaneously. Prior to  $t=0$  switch (a) was open and switch (b) was close for a long time. At  $t=0$ , switch (a) is closed and switch (b) is opened.

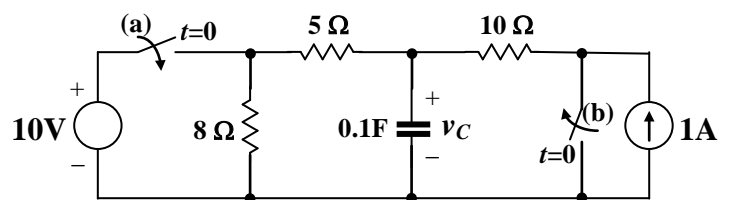


Fig.2

- Find  $v_C(0^+)$ ,  $i_C(0^+)$ ,  $v_C(\infty)$ ,  $i_C(\infty)$ , and the time constant  $\tau$ . (10 Points)
- Find  $v_C(t)$  and  $i_C(t)$  for  $t \geq 0$ . (4 Points)

**Hint:** use the superposition theorem.

$$v_C(0^+) = 0$$

$$v_C(\infty) = 15 \text{ V}$$

$$i_C(0^+) = 3 \text{ A}$$

$$i_C(\infty) = 0$$

$$\tau = 0.5 \text{ S}$$

$$v_C(t) = 15(1 - e^{-2t}) \text{ V}$$

$$i_C(t) = 3 e^{-2t} \text{ A}$$

**Question #3: (12 Points)**

Consider the circuit in Fig.3 with two inputs  $v(t)=4\delta(t)$  V and  $i(t)=2\delta(t)$  A. The inductor and capacitor have zero initial state, i.e.  $v_C(t=0^-) = 0$  and  $i_L(t=0^-) = 0$ .

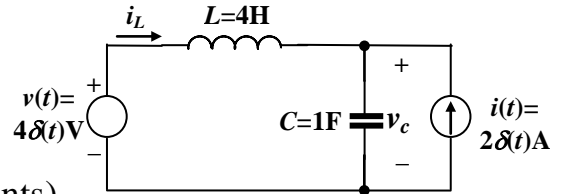



Fig.3

- a) Draw the s domain equivalent circuit. (2 Points)
- b) Find the capacitor voltage  $v_C(t)$ , for  $t \geq 0$ . (6 Points)
- c) What are the inductor current  $i_L$  and the capacitor voltage  $v_C$  at  $t=0+$ ? (4 Points)

$$V_C \left( s + \frac{1}{4s} \right) = 2 + \frac{1}{s}$$

$$V_C(s) = \frac{2s + 1}{s^2 + 0.25}$$

$$v_C(t) = 2 \cos 0.5t + 2 \sin 0.5t$$

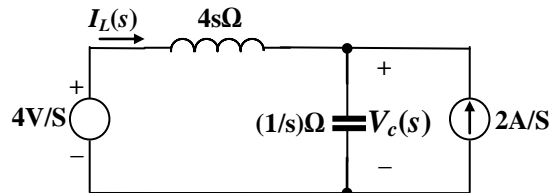

$$v_C(t) = 2\sqrt{2} \cos(0.5t + 45^\circ)$$

$$v_C(0^+) = 2 \text{ V}$$

$$i_L(0^+) = 1 \text{ A}$$

**Question #4: (12 Points)**

a) A three-phase Y-connected +ve sequence source having the phase voltage  $V_a=240\angle 0^\circ$  V and negligible source resistance. The source supplies a balanced  $\Delta$ -connected load having an impedance of  $60\angle 30^\circ \Omega$ /phase. The three lines connecting the source to the load have negligible resistance. The load power is measured using the two wattmeter method. The first wattmeter  $W_1$  is connected between lines A and B, while the second one  $W_2$  is connected between lines C and B. Find the following:

The phase current  $\overline{I_{AB}}$  at the load =

$$6.928\angle 0^\circ \text{ A}$$

The Line current  $\overline{I_A}$  =

$$12\angle -30^\circ \text{ A}$$

The line voltage  $\overline{V_{AB}}$  at the load =

$$415.69 \angle 30^\circ \text{ V}$$

The reading of  $W_1$  =

$$2.494 \text{ KW}$$

The reading of  $W_2$  =

$$4.988 \text{ KW}$$


The total power dissipated in the load =

$$7.482 \text{ KW}$$

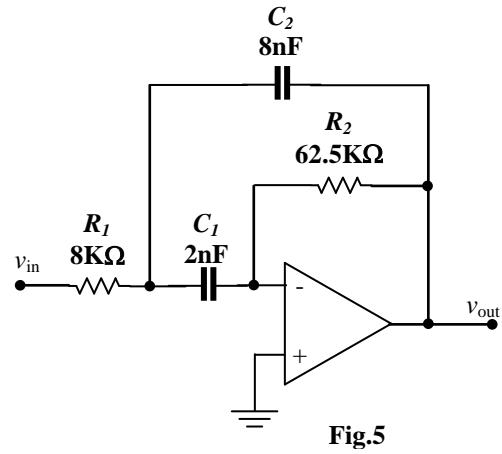**Question #5: (14 Points)**

Consider the circuit of Fig.5, the operational amplifier is ideal. It is required to:

- Find an expression for the voltage transfer function  $H_v(s) = V_{out}(s)/V_{in}(s)$ . (6 points)
- Compute the numerical values of poles and zeros of the transfer function. (4 points)
- If the input is a sinusoidal waveform given by:  $v_{in}(t) = 10 \cos(10^4 t + 30^\circ)$  V; give the expression for the output  $v_{out}(t)$ . (4 points)



$$H_v(s) = \frac{-\frac{1}{R_1 C_2} s}{s^2 + \frac{1}{R_2} \left( \frac{1}{C_1} + \frac{1}{C_2} \right) s + \frac{1}{R_1 R_2 C_1 C_2}} = \frac{-1.5625 \times 10^4 s}{s^2 + 10^4 s + 1.25 \times 10^8}$$


**Poles:**  $-5 - j 10 \text{ Krad/S}, -5 + j 10 \text{ Krad/S}$

**Zeros:**  $0, \infty$

**$V_{out}(t) = 15.1585 \cos(10^4 t - 135.96^\circ)$  V**

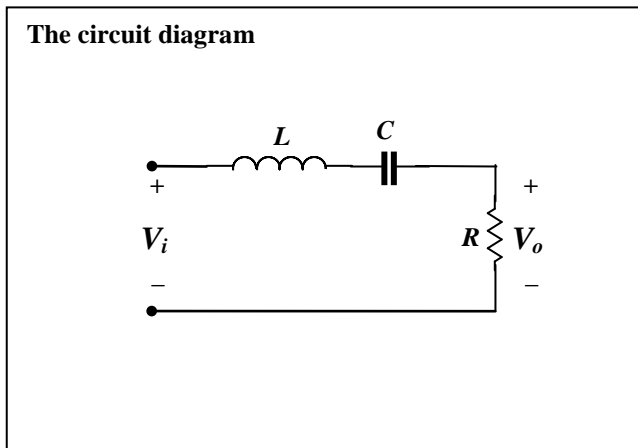**Question #6: (12 Points)**



- A series *RLC* band-pass filter has a center, or resonant, frequency of 50 kHz and a quality factor of 4. Find the band-width, the upper cutoff frequency, and the lower cut-off frequency. (6 Points)
- Use a 5 nF capacitor to design the filter. Draw the circuit diagram and specify the values of *R* and *L*. (6 Points)



<b>BW = 12.5 KHz</b>	<b><math>f_1 = 44.14 \text{ KHz}</math></b>	<b><math>f_2 = 56.64 \text{ KHz}</math></b>
<b><math>R = 159.2 \Omega</math></b>	<b><math>L = 2.026 \text{ mH}</math></b>	

**Question #7: (12 Points)**

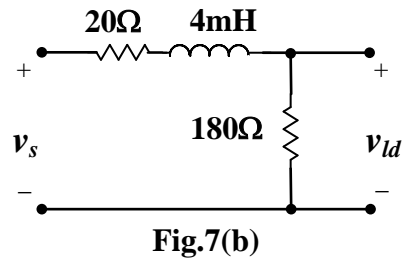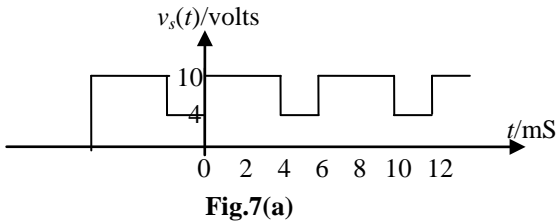- a) Find the first four Fourier coefficients of the voltage waveform of Fig.7(a). (4 Marks)
- b) The voltage waveform of Fig.7(a) is applied to the circuit of Fig.7(b). Find the Fourier coefficients of the output voltage  $v_{ld}$ . (4 Marks)
- c) Find the *RMS* values of the source voltage and the load voltage. (4 Marks)



$$a_0 = \boxed{8 \text{ V}}$$

$$V_{ld0} = \boxed{7.2 \text{ V}}$$

$$C_1 = \boxed{3.308 \angle 120^\circ \text{ V}}$$

$$V_{ld1} = \boxed{2.377 \angle 83^\circ \text{ V}}$$

$$C_2 = \boxed{1.645 \angle 60^\circ \text{ V}}$$

$$V_{ld2} = \boxed{0.8227 \angle 3.55^\circ \text{ V}}$$

$$C_3 = \boxed{0}$$


$$V_{ld3} = \boxed{0}$$

$$V_{s(RMS)} = \boxed{8.49 \text{ V}}$$

$$V_{ld(RMS)} = \boxed{7.42 \text{ V}}$$

**Question #8: (12 Points)**

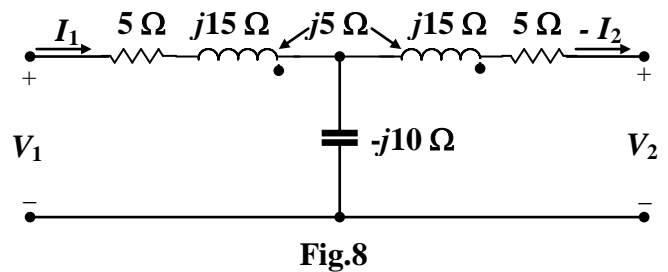- a) Find the transmission parameters of the two-port network of Fig.8. (8 Points)
- b) A voltage source  $V_s = 75 \angle 0^\circ \text{ V}$  and source impedance  $Z_s = 1 \angle 0^\circ \Omega$  is applied to the input port, and a load  $Z_L = 10 \angle 0^\circ \Omega$  is connected to the output port, find  $V_2$ . (4 Points)



$$a_{11} = \boxed{-1/3 + j(1/3)}$$

$$a_{12} = \boxed{-10/3 + j5 \Omega}$$

$$a_{21} = \boxed{j(1/15) \text{ S}}$$

$$a_{22} = \boxed{-1/3 + j(1/3)}$$

$$V_2 = \boxed{8.01 \angle -85.7^\circ \text{ V}}$$





الامتحان مكون من أربع صفحات، الإجابة في نفس ورقة الأسئلة، النهاية العظمى ١٠٠ درجة.  
الإجابة النهائية يجب أن تكون مكتوبة في المكان المخصص لها وخطوات الحل تكون في الصفحة المقابلة.

Attempt all questions, full mark: 100 Points

Time: 3 Hours

**Question #1: (12 Points)**

The circuit shown in Fig.1 is used to measure the change in resistance experienced by strain gages.

- Derive an expression for the output voltage  $V_{out}$  in terms of the resistance values and the reference voltage  $V_{ref}$ , assuming ideal op-amp and neglecting  $\Delta R^2$  w.r.t.  $R^2$ . (8 Points)
- If  $R = 160 \Omega$ ,  $\Delta R = 1 \Omega$ ,  $R_f = 1.2 \text{ K}\Omega$ , and  $V_{ref} = 8 \text{ V}$ ; find the value  $V_{out}$ . (4 Points)

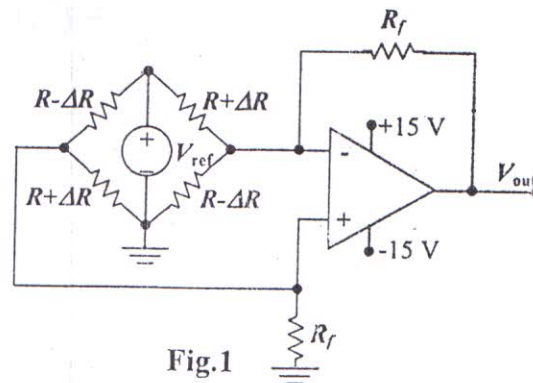


Fig.1

Expression for  $V_{out}$ :

$$V_{out} =$$

Value of  $V_{out}$ :

$$V_{out} =$$

**Question #2: (16 Points)**

In the circuit shown in Fig.2, the initial currents in inductors  $L_1$  and  $L_2$  are 8A and 1A respectively. The switch is opened at  $t = 0$ .

- Find  $i(t)$ , for  $t \geq 0$ . (8 Points)
- Find  $v(t)$ , for  $t \geq 0$ . (2 Points)
- Find  $i_1(t)$  and  $i_2(t)$ , for  $t \geq 0$ . (4 Points)
- Determine the total energy stored in the inductors as  $t \rightarrow \infty$ . (2 Points)

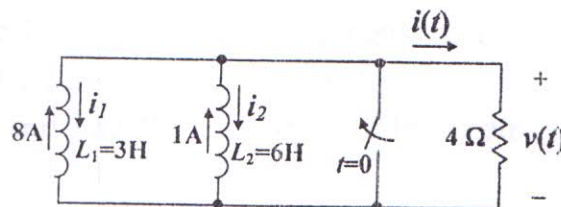


Fig.2

$$i(0^+) =$$

$$i(\infty) =$$

$$\tau =$$

$$i(t) =$$

$$v(t) =$$

$$i_1(t) =$$

$$i_2(t) =$$

Energy stored in the inductors as  $t \rightarrow \infty =$

**Question #3: (12 Points)**

The switch in the circuit shown in Fig.3 has been in position (a) for a long time. At  $t = 0$ , it moves to position (b). Find  $i(0^+)$ ,  $v_c(0^+)$ ,  $di(0^+)/dt$ , the roots of the characteristic equation  $s_1, s_2$  and  $i(t)$  for  $t \geq 0$ .

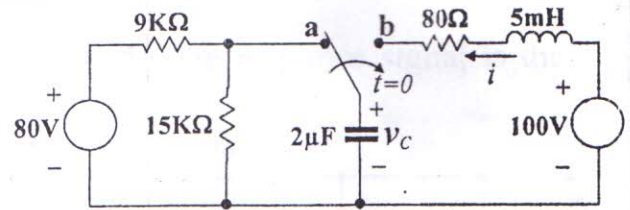


Fig. 3

$i(0^+) =$

$v_c(0^+) =$

$di(0^+)/dt =$

$s_1 =$

$s_2 =$

$i(t) =$

**Question #4: (12 Points)**

A three-phase  $\Delta$ -connected -ve sequence source having the phase voltage  $V_{ab}=240\angle 0^\circ\text{V}$  and negligible source resistance. The source supplies a resistive unbalanced  $\Delta$ -connected load having impedances:  $R_{AB}= 60 \Omega$ ,  $R_{BC}= 40 \Omega$ , and  $R_{CA}= 80 \Omega$ . The three lines connecting the source to the load have negligible resistances. The load power is measured using the two wattmeter method. The first wattmeter  $W_1$  is connected between lines A and B, while the second one  $W_2$  is connected between lines C and B. Find the following:

- The phase current  $\overline{I_{AB}}$  at the load =
- The Line current  $\overline{I_A} =$
- The Line current  $\overline{I_C} =$
- The reading of  $W_1 =$
- The reading of  $W_2 =$
- The total power dissipated in the load =

**Question #5: (14 Points)**

The voltage source  $v_g$  drives the circuit shown in Fig.5. The response signal is the voltage across the capacitor,  $v_o$ .

- Calculate the numerical expression for the voltage transfer function  $H_v(s) = V_o(s)/V_g(s)$ . (6 points)
- Calculate the numerical values for the poles and zeros of the transfer function. (4 points)
- The circuit is driven by a step voltage source, namely,  $v_g = 50u(t)$ , find  $v_o(t)$ . (4 points)

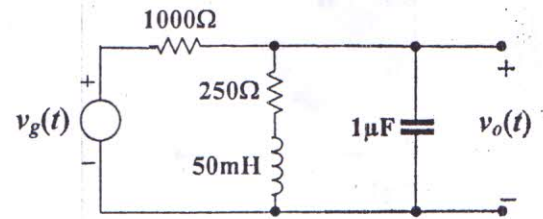


Fig.5

$H_v(s) =$

Poles:

Zeros:

$V_{out}(t) =$

**Question #6: (12 Points)**

The ideal transformer used in the circuit of Fig.6 has a turns ratio  $N_2/N_1=3$ .

- Find the reflected impedance at terminals a-b of that transformer. (6 Points)
- Calculate the value of the currents  $I_1, I_2, I_3$ , and  $I_4$ . (6 Points)

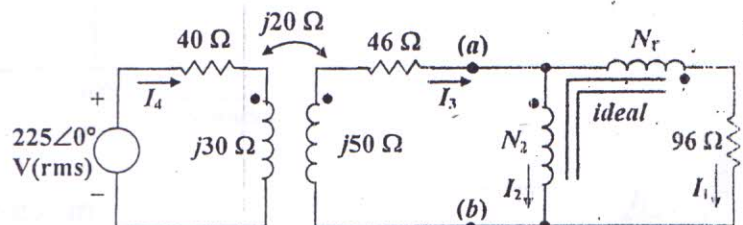


Fig.6

$Z_R =$

$I_1 =$

$I_2 =$

$I_3 =$

$I_4 =$

**Question #7: (6 Points)**

- a) Calculate the impedance of the circuit shown in Fig.7 at radian frequency of 2 Krad/S. (2 Points)  
 b) At what finite frequency ( $\omega_r$ ) does the impedance of the circuit become purely resistive? What is the impedance at that frequency? (4 Points)

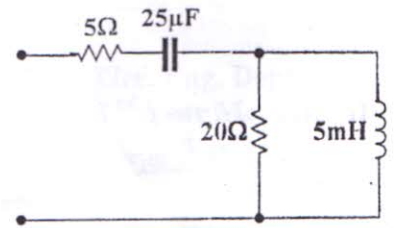


Fig.7


$Z(2\text{Krad}) =$

$\omega_r =$

$Z(\omega_r) =$

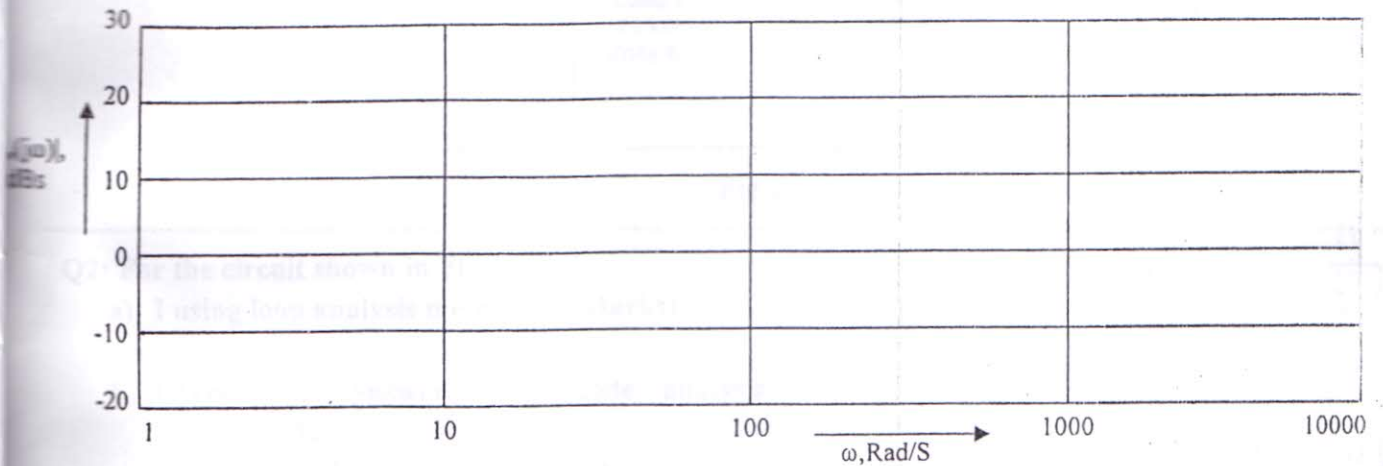**Question #8: (8 Points)**

Sketch the Bode Diagram of the voltage transfer function:  $H_v(s) = \frac{1000(s+100)}{(s+10)(s+1000)}$



**Question #9: (8 Points)**

The y parameters for the two-port network in Fig.9 are:  $y_{11} = 2\text{mS}$ ,  $y_{12} = -0.2\text{mS}$ ,  $y_{21} = 10\text{mS}$ , and  $y_{22} = -0.5\text{mS}$ . Find  $V_1$ ,  $V_2$ ,  $I_1$ , and  $I_2$ .

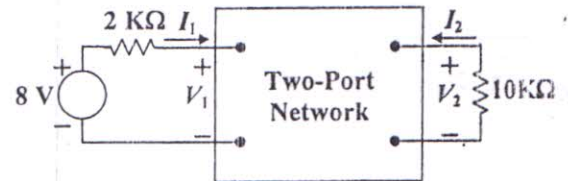


Fig.9

$V_1 =$

$V_2 =$

$I_1 =$

$I_2 =$

2

الامتحان مكون من أربع صفحات، الإجابة في نفس ورقة الأسئلة، النهاية العظمى ١٠٠ درجة.  
الإجابة النهائية يجب أن تكون مكتوبة في المكان المخصص لها ولن يلتفت لغير ذلك.

**Question 1:**

a) The op-amp in the circuit of Fig.a is ideal. Calculate the following: (10 Marks)

- $I_1$
- $I_2$
- $I_3$
- $I_4$
- $V_o$

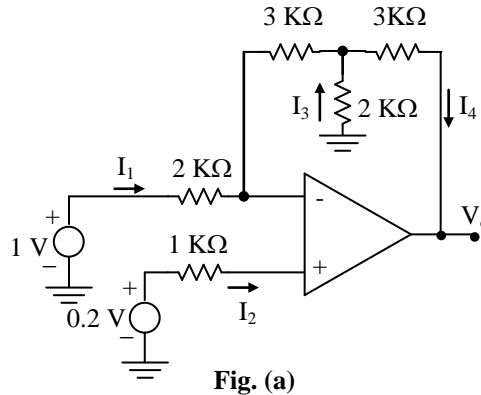


Fig. (a)

b) The switch in the circuit of Fig. (b) has been in position a for a long time. At  $t=0$  it moves to position b. Calculate the following: (10 Marks)

- $v_c(0^+)$
- $i_L(0^+)$
- $v_o(0^-)$
- $v_o(0^+)$
- $i_c(0^+)$

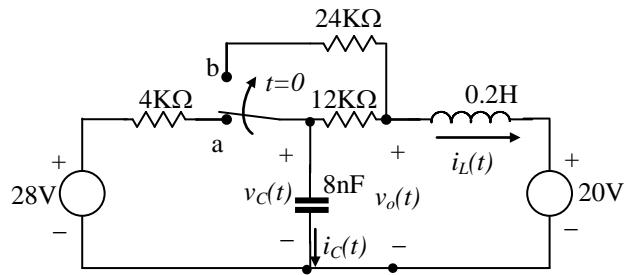


Fig. (b)

c) The circuit of Fig. (c) operates at radian frequency  $\omega = 100$  rad/sec. Find the mutual inductance  $M$ , the reflected impedance  $Z_r$  and the input impedance at port a-b. (6 Marks)

- $M$
- $Z_r$
- $Z_{in}$

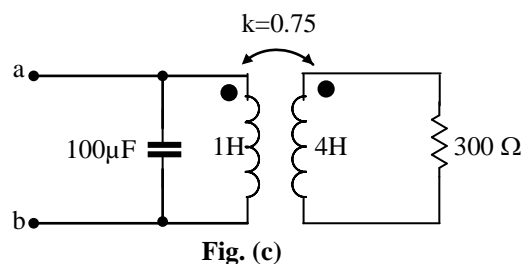


Fig. (c)

**Question 2:**

a) The switch in the circuit shown in Fig.a has been closed for a long time before it opens at  $t = 0$ . Find  $v(t)$  for  $0 \leq t \leq \infty$ . (10 Marks)

$i_L(0^+) =$

$v(0^+) =$

$v(\infty) =$

$\tau =$

$v(t) =$

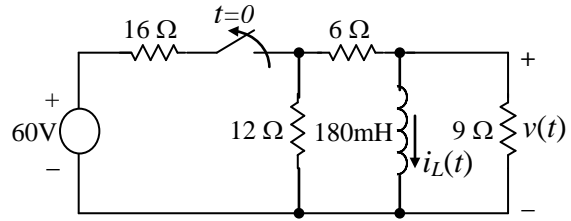


Fig. a

b) A balanced Y-connected load having an impedance of  $18\Omega$ /phase is connected in parallel with a balanced  $\Delta$ -connected load having an impedance of  $36\Omega$ /phase. The parallel loads are fed from lines having an impedance of  $2\Omega$ /line. The magnitude of the line-to-neutral voltage at the Y-load is 720 V. Calculate the following:

(10 Marks)

The magnitude of the line current

The magnitude of the phase current in the  $\Delta$ - load

The magnitude of the phase current in the Y- load

The magnitude of the line voltage at the sending end

The total power dissipated in the loads

c) For the two-port of Fig. (c), Calculate:

(8 Marks)

$z_{11} =$

$a_{21} =$

$h_{12} =$

$y_{22} =$

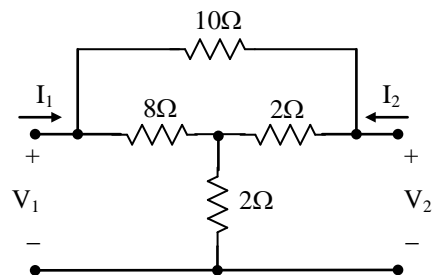


Fig. (c)

**Question 3:**

a) Find the first four Fourier coefficients of the voltage waveform of Fig.(a). (8 Marks)

$$a_0 = 6.7$$

$$C_1 = 5.5 \angle 150^\circ$$

$$C_2 = 2.76 \angle 30^\circ$$

$$C_3 = 0$$

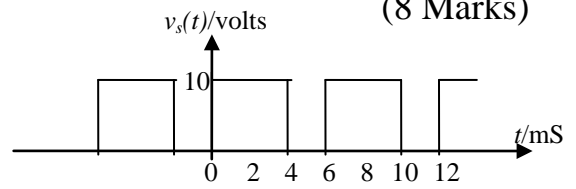


Fig. (a)

b) The voltage waveform of Fig.(a) is applied to the circuit of Fig. (b). Find the Fourier coefficients of the output voltage  $v_{ld}$ . (8 Marks)

$$V_{ld0} = 6 \text{ V}$$

$$V_{ld1} = 4.85 \angle 138.2^\circ \text{ V}$$

$$V_{ld2} = 2.29 \angle 7.3^\circ \text{ V}$$

$$V_{ld3} = 0$$


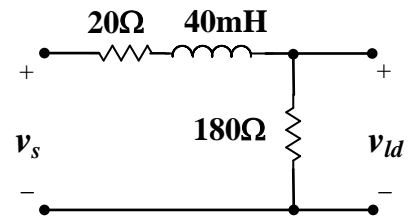


Fig. (b)

c) Sketch the Bode Diagram of the voltage transfer function:  $H_v(s) = \frac{1000(s+100)}{(s+10)(s+1000)}$

(8 Marks)

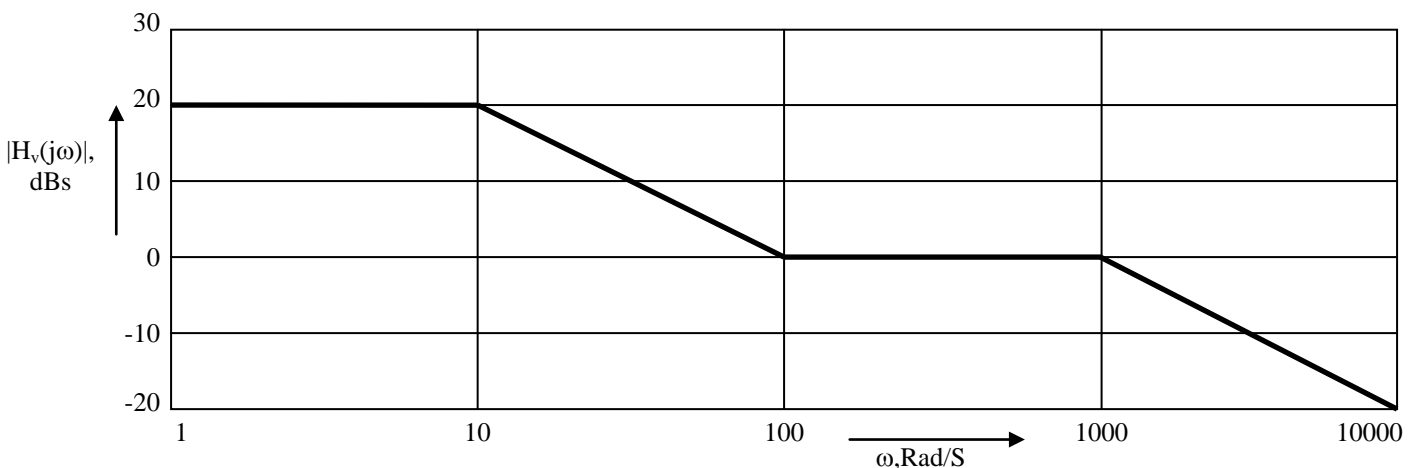

**Question 4:**

- a) Find the voltage transfer function and its poles and zeros for the circuit of Fig.a. (10 Marks)

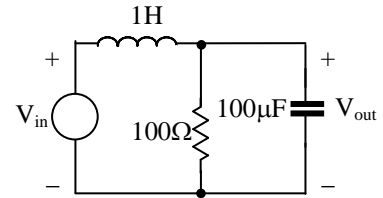


Fig.(a)

$$H_v(s) = \frac{10^4}{s^2 + 100s + 10^4}$$

**Poles:**  $-50 + j 86.6, -50 - j 86.6$

**Zeros:**  $\infty, \infty$

- b) The switch in the circuit shown in Fig.b has been opened for a long time before it closes at  $t = 0$ . Find  $v_c(t)$  for  $t \geq 0$ . (12 Marks)

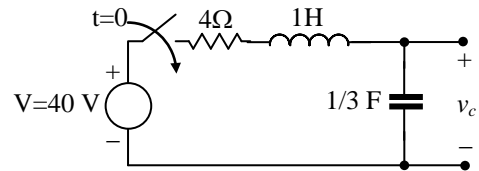


Fig. (b)

$$V_C(s) = \frac{120}{s(s^2 + 4s + 3)}$$

$$= \frac{120}{s(s+1)(s+3)}$$

$$= \frac{40}{s} - \frac{60}{s+1} + \frac{20}{s+3}$$

$$v_c(t) = [40 - 60e^{-t} + 20e^{-3t}]u(t) V$$



الامتحان مكون من أربع صفحات، الإجابة في نفس ورقة الأسئلة، النهاية العظمى ١٠٠ درجة.  
الإجابة النهائية يجب أن تكون مكتوبة في المكان المخصص لها ولن يلتفت لغير ذلك.

**Question 1:**

a) The voltage waveform  $v_g$  shown in Fig.(a-1) is applied to the circuit of Fig.(a-2). Sketch  $v_o$  and  $v_1$  versus  $t$ , assuming ideal op-amp. (10 Marks)

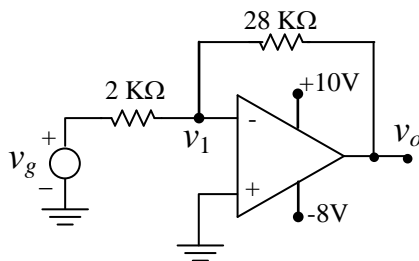


Fig. (a-2)


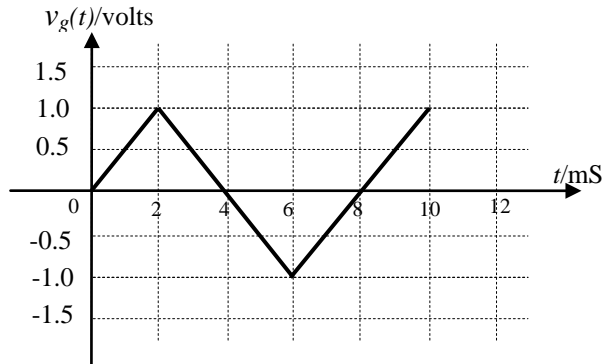
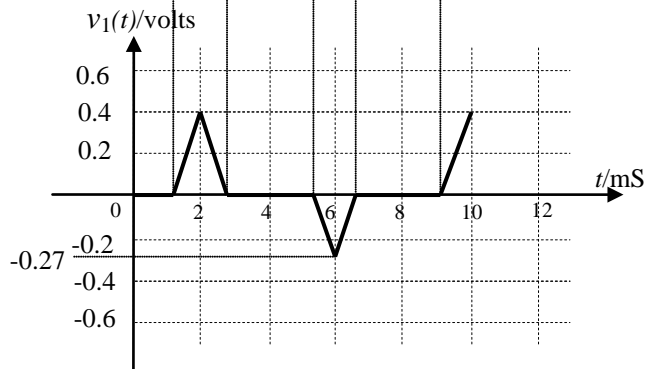


Fig. (a-1)

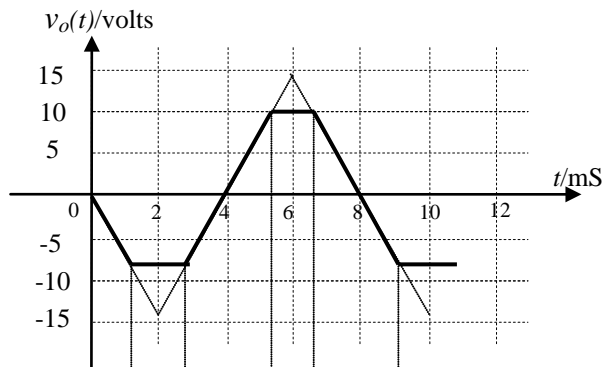

b) The switch in the circuit shown in Fig.b has been opened for a long time before it closes at  $t = 0$ . Find  $i_o(t)$  for  $0 \leq t \leq \infty$ . (10 Marks)

$i_L(0^+) =$  1 A

$i_o(0^+) =$  0.5 A

$i_o(\infty) =$  1.5 A

$\tau =$  0.5 S

$i_o(t) =$   $1.5 - e^{-2t} \text{ A}, 0 \leq t \leq \infty$

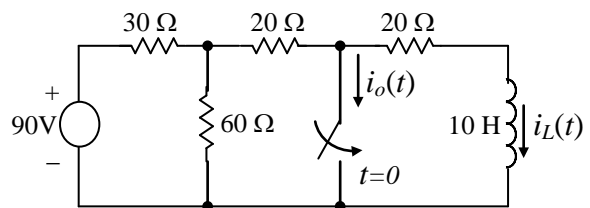


Fig. b

**Question 2:**

- a) i) Write the two mesh equations for the circuit of Fig.(a) and solve them to find  $I_1$ ,  $I_2$ , and the power dissipated in  $R_L$ . (10 Marks)
- ii) Find the Thevenin equivalent circuit at the output port, hence find the value of  $R_L$  that consumes maximum power, and the value of this power. (6 Marks)

The first mesh equation

**$80 I_1 - 20 I_2 + V_1 = 400$**

The second mesh equation

**$-20 I_1 + 105 I_2 - V_2 = 0$**

$I_1 =$  **0.25 A**

$I_2 =$  **1 A**

$P_L =$  **85 W**

$R_{Th} =$  **15Ω**

$V_{Th} =$  **100 V**

$P_{max} =$  **166.7 W**

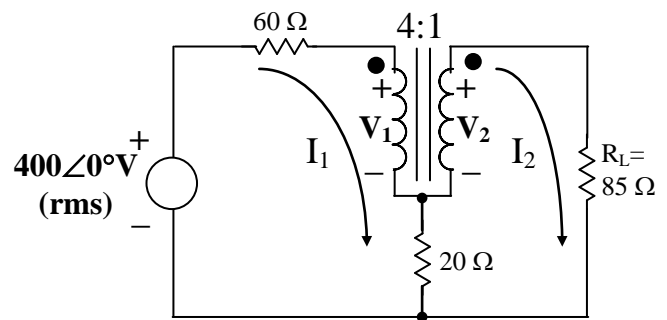


Fig. (a)

- b) A three-phase Y-connected +ve sequence source having the phase voltage  $V_a=220\angle 0^\circ\text{V}$ . The source resistance is  $2\ \Omega/\text{Phase}$ . The source supplies a balanced  $\Delta$ -connected load having a load impedance of  $36\angle 30^\circ\Omega/\text{Phase}$ . The three lines connecting the source to the load have a resistance of  $1\ \Omega/\text{Line}$ . Find the following: (10 Marks)

The magnitude of the line current **15 A**

The magnitude of the phase current in the  $\Delta$ - load **8.66 A**

The magnitude of the line voltage at the sending end **334.5 V**

The magnitude of the line voltage at the load **312 V**

The total active power dissipated in the load **7015 W**

**Question 3:**


a) Find the mean value, RMS value, period, and fundamental frequency in Hz, for the voltage waveform of Fig.(a). (8 Marks)

Mean value = 6.67 V

RMS value = 8.165 V

Period = 6 mS

Fundamental frequency = 166.7 Hz

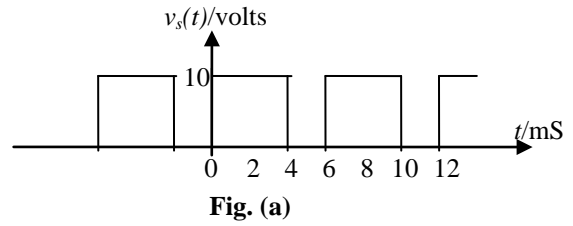

- b) i) What is the type of filter shown Fig.(b)? (2 Marks)  
 ii) Write the voltage transfer function  $H_v(s)$  of that filter. (2 Marks)  
 iii) Find the filter cut-off frequency  $f_c$ . (2 Marks)  
 iv) What is the maximum value of  $H_v(s)$ ? (2 Marks)  
 v) At what frequency will  $|H_v(s)|$  equals half its maximum value? (2 Marks)


type of filter High pass filter

$H_v(s) =$   $\frac{0.9}{s + 10^4}$


$f_c =$  1592 Hz

$H_v(s)|_{\max} =$  0.9

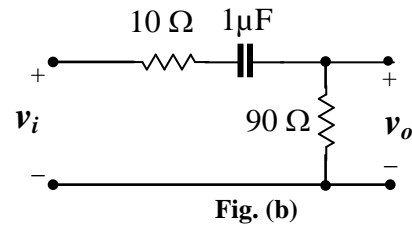Frequency of  $\frac{1}{2}$  max value = 919 Hz




c) Sketch the Bode Diagram of the voltage transfer function:  $H_v(s) = \frac{20000 s}{(s + 20)(s + 1000)}$  (6 Marks)

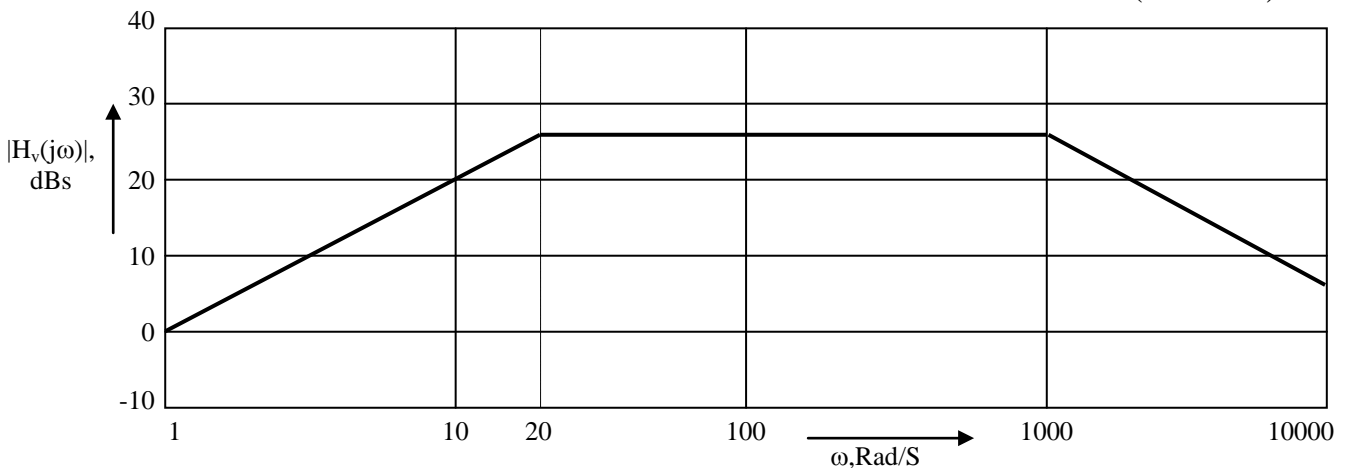

**Question 4:**

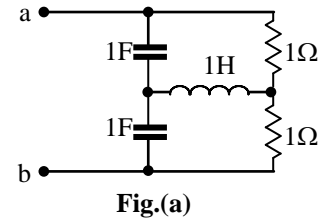- a) Find the s-domain expression of the input impedance seen looking into the terminals a, b of the circuit of Fig.(a). Find also the poles and zeros of that impedance. (10 Marks)




$$Z_{in}(s) = \frac{2s^2 + 3s + 1}{2s(s^2 + s + 1)}$$

**Poles**    **0, (-0.5 + j 0.866), (-0.5 - j 0.866)**

**Zeros**    **-0.5, -1, ∞**

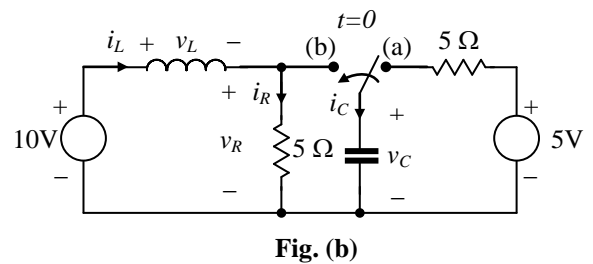- b) The switch in the circuit of Fig. (b) is moved from (a) to (b) at  $t = 0$ . Find the following currents and voltages: (12 Marks)



$i_R(0^-)$     **2 A**

$i_R(0^+)$     **1 A**

$i_C(0^+)$     **1 A**

$i_L(0^+)$     **2 A**

$v_L(0^+)$     **5 V**

$v_R(\infty)$     **10 V**

- c) The  $a$ -parameters of a certain two-port are  $a_{11}= 3$ ,  $a_{12}= 10 \Omega$ ,  $a_{21}= 0.5 S$ ,  $a_{22}= 2$ . Find the  $h$ -parameters. (8 Marks)

$h_{11} =$     **5  $\Omega$**

$h_{12} =$     **-0.5**

$h_{21} =$     **0.5**

$h_{22} =$     **0.25 S**

\*\*\*\*\*

أطيب التمنيات بالتوفيق  
أ.د. مجدى مفيد دوس

\*\*\*\*\*



الامتحان مكون من أربع صفحات، الإجابة في نفس ورقة الأسئلة، النهاية العظمى ١٠٠ درجة.  
الإجابة النهائية يجب أن تكون مكتوبة في المكان المخصص لها ولن يلتفت لغير ذلك.

**Question 1:**

a) The op-amp in the non-inverting amplifier of Fig.a is ideal. Find the  $i_1$ ,  $i_2$ ,  $v_1$ ,  $i_3$ ,  $v_o$ , and  $i_o$ .

(12 Marks)

- $i_1 = 0.1 \text{ mA}$
- $i_2 = 0.2 \text{ mA}$
- $v_1 = 4 \text{ V}$
- $i_3 = 0.2 \text{ mA}$
- $v_o = 8 \text{ V}$
- $i_o = 0.4 \text{ mA}$

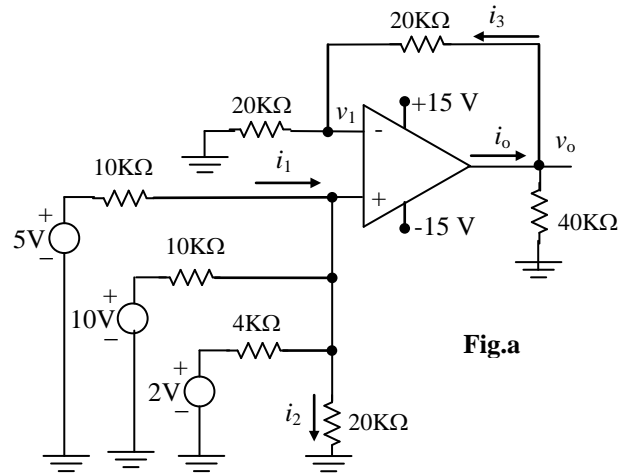


Fig.a

b) The switch in the circuit shown in Fig.b has been in position (a) for a long time before it moves to (b) at  $t = 0$ . After 5 mSec, the inductance current  $i_L$  dropped to 80% of its initial value. Find the value of  $L$ .

(12 Marks)

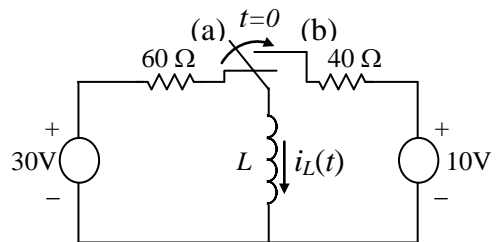


Fig. b

$i_L(0^+) = 0.5 \text{ A}$

$i_L(\infty) = 0.25 \text{ A}$

$i(t) = 0.25 + 0.25e^{-t/\tau}$

$i(5\text{mS}) = 0.25 \left( 1 + e^{-\frac{5}{\tau}} \right) = 0.4 \text{ A}$

$\tau = 9.788 \text{ mS}$

$L = 392 \text{ mH}$

**Question 2:**

a) A three-phase  $\Delta$ -connected +ve sequence source having the phase voltage  $V_{ab}=220\angle 0^\circ\text{V}$ . The source resistance is  $1\ \Omega$  / Phase. The source supplies an unbalanced  $\Delta$ -connected resistive load having  $R_{ab} = 10\Omega$ ,  $R_{bc} = 9\Omega$  and  $R_{ca} = 21\Omega$ . The three lines connecting the source to the load have negligible resistance. The load power is measured using the two wattmeter method. The first wattmeter  $W_1$  is connected between lines A and B, while the second one  $W_2$  is connected between lines C and B. Find the following: (12 Marks)

The phase current $\overline{I_{AB}}$ at the load =	<b>20<math>\angle 0^\circ</math> A</b>
The Line current $\overline{I_A}$ =	<b>26.46<math>\angle -19.1^\circ</math> A</b>
The line voltage $\overline{V_{AB}}$ at the load =	<b>200<math>\angle 0^\circ</math> V</b>
The reading of $W_1$ =	<b>5 KW</b>
The reading of $W_2$ =	<b>5.35 KW</b>
The total power dissipated in the load =	<b>10.35 KW</b>

- b) i) Find the voltage transfer function of the circuit of Fig.(b). (6 Marks)  
 ii) Find the poles and zeros of the transfer function. (4 Marks)  
 iii) Find the magnitude of the transfer function at  $\omega = 5$  Rad/Sec. (2 Marks)

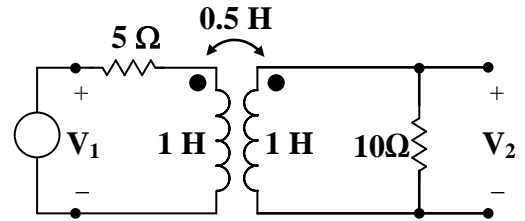


Fig. (b)

$$(2s + 10)I_1 + s I_2 = 2 V_1$$

$$s I_1 + (2s + 20)I_2 = 0$$

$$H_v(s) = \frac{20s}{3s^2 + 60s + 200}$$

Poles: **- 4.23 , - 15.77 S<sup>-1</sup>**

Zeros: **0,  $\infty$**

$|H_v(j5)| =$  **0.308**

**Question 3:**


a) Find the first four non-zero terms of the Fourier series of the periodic voltage waveform shown in Fig.(a). (8 Marks)

$$b_n(t) = \frac{2}{T} \int_{-\frac{T}{2}}^{\frac{T}{2}} 5t \cdot \sin(n\omega_0 t) dt = -\frac{10}{n\omega_0 T} \int_{-\frac{T}{2}}^{\frac{T}{2}} t \cdot d\cos(n\omega_0 t)$$

$$= -\frac{5}{n\pi} \left[ t \cdot \cos(n\omega_0 t) - \frac{1}{n\omega_0} \sin(n\omega_0 t) \right]_{-\frac{T}{2}}^{\frac{T}{2}}$$


$$= -\frac{5}{n\pi} \left[ t \cdot \cos(n\omega_0 t) - \frac{1}{n\omega_0} \sin(n\omega_0 t) \right]_{-\frac{T}{2}}^{\frac{T}{2}} = -\frac{20}{n\pi} \cos(n\pi)$$

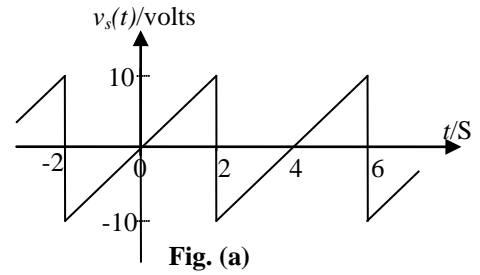$b_1 = 20/\pi, b_2 = -10/\pi, b_3 = 20/3\pi, b_4 = -5/\pi,$



b) There is no energy stored in the circuit of Fig.b at the time the switch is closed:

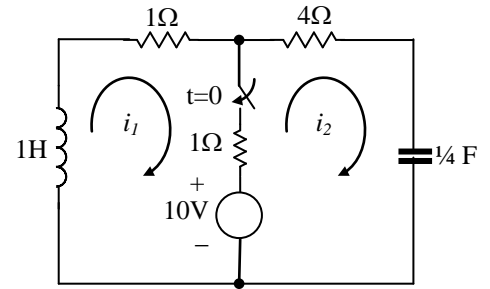- i) Write the two mesh equations of the circuit. (4 Marks)
- ii) Find  $I_1(s)$  and  $I_2(s)$ . (4 Marks)
- iii) Find  $i_1(t)$  and  $i_2(t)$ . (4 Marks)



The first s-domain mesh equation:  
 $(s^2 + 2s) I_1 - s I_2 = -10$

The second s-domain mesh equation:  
 $-s I_1 + (5s + 4) I_2 = 10$


$$I_1(s) = \frac{-8}{s(s + 1.6)} = \frac{5}{s + 1.6} - \frac{5}{s}$$

$$I_2(s) = \frac{2}{s + 1.6}$$

$$i_1(t) = [-5 + 5e^{-1.6t}]u(t)A$$

$$i_2(t) = 2e^{-1.6t}u(t)A$$

c) Sketch the Bode Diagram of the voltage transfer function:  $H_v(s) = \frac{1000(s + 200)}{(s + 20)(s + 1000)}$  (6 Marks)

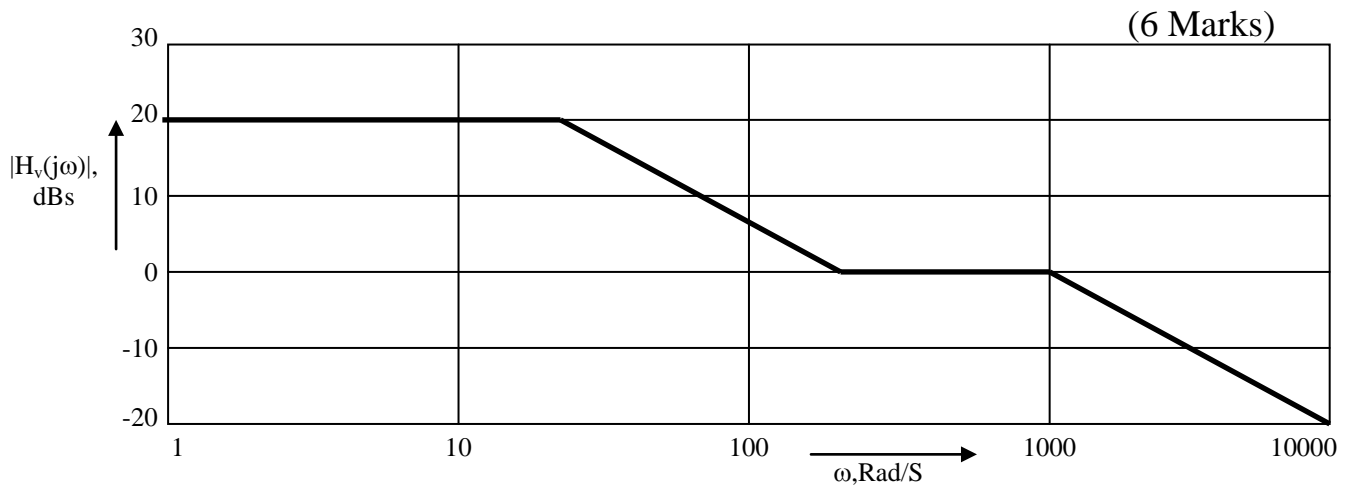

**Question 4:**

- a) The switch in the circuit of Fig. (a) has been open a long time before closing at  $t = 0$ .
- Find  $i_L(0^+)$ ,  $i_L(\infty)$ ,  $v_L(0^+)$ ,  $\frac{di_L}{dt}(0^+)$ . (8 Marks)
  - Write the differential equation of  $i_L(t)$ . (2 Marks)
  - Write the characteristic equation and find its roots. (4 Marks)
  - The constants in the solution for  $i_L(t)$ . (2 Marks)
  - Find  $i_L(t)$  for  $t \geq 0$ . (2 Marks)

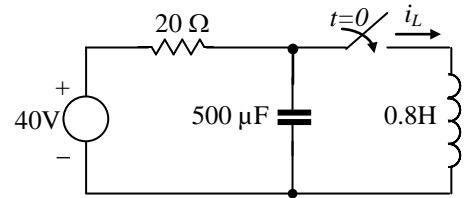


Fig. (a)

$i_L(0^+) = 0$

$i_L(\infty) = 2 \text{ A}$

$v_L(0^+) = 40 \text{ V}$

$\frac{di_L}{dt}(0^+) = \frac{v_L(0^+)}{L} = 50 \text{ A/S}$

the differential equation of  $i_L(t)$

$$\frac{d^2 i}{dt^2} + \frac{1}{RC} \cdot \frac{di}{dt} + \frac{1}{LC} \cdot i = \frac{2}{LC}$$

the characteristic equation

$$s^2 + 100 s + 2500 = 0$$

roots of the characteristic equation

$$s_1 = s_2 = -50$$

The constants

$$D_1 = -50, D_2 = -2$$

$$i_L(t) = 2 - (50 t + 2) e^{-50t}$$

- b) Find the  $h$  parameters of the circuit shown in Fig.(b). (8 Marks)

$h_{11} = 60 \Omega$

$h_{12} = 0.333$

$h_{21} = -0.21$

$h_{22} = 8.8 \text{ mS}$

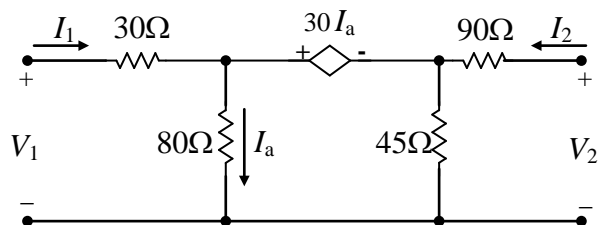


Fig.(b)

\*\*\*\*\*

أطيب التمنيات بالتوفيق  
أ.د. مجدى مفيد دوس

\*\*\*\*\*





الامتحان مكون من أربع صفحات، الإجابة في نفس ورقة الأسئلة، النهاية العظمى ١٠٠ درجة.  
الإجابة النهائية يجب أن تكون مكتوبة في المكان المخصص لها وخطوات الحل تكون في الصفحة المقابلة.

**Question #1: (12 Points)**

The two op amps in the circuit in Fig.1 are ideal. Calculate  $v_{o1}$ ,  $v_{o2}$ ,  $i_{o1}$  and  $i_{o2}$ .

- $v_{o1} = 2.125 \text{ V}$
- $v_{o2} = 2.5 \text{ V}$
- $i_{o1} = 0.25 \text{ mA}$
- $i_{o2} = 1.75 \text{ mA}$

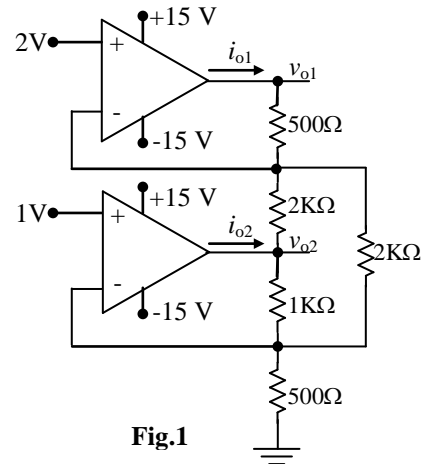


Fig.1

**Question #2: (16 Points)**

The voltage waveform shown in Fig.2(a) is applied to the circuit of Fig.2(b). The initial voltage on the capacitor is zero. Calculate and sketch  $v_o(t)$ .


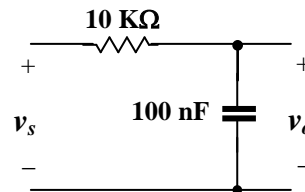
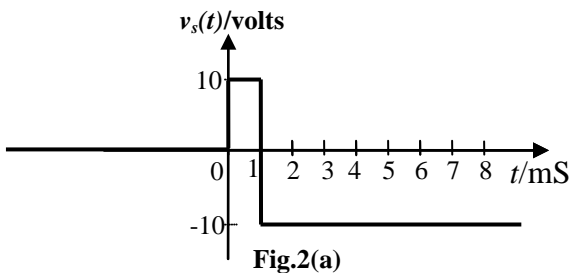


Fig.2(b)

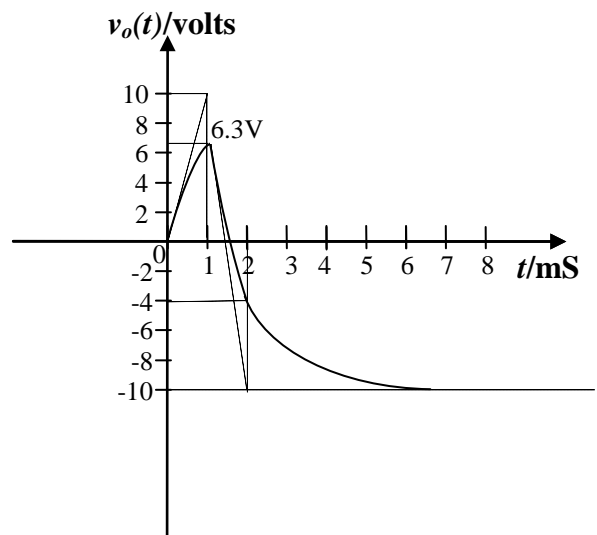- $v_o(0^+) = 0$
- $v_o(\infty)_1 = 10 \text{ V}$
- $\tau = 1 \text{ mS}$
- $v_o(t) = 10(1 - e^{-t}) \text{ V}$   
 $0 \leq t \leq 1 \text{ mS}$
- $v_o(1\text{mS}) = 6.3 \text{ V}$
- $v_o(\infty) = -10 \text{ V}$
- $v_o(t) = -10 + 16.3 e^{-(t-1)} \text{ V}$   
 $1\text{mS} \leq t \leq \infty$



**Question #3: (10 Points)**

The voltage response for the circuit in Fig.3 is known to be  $v(t) = D_1 t e^{-500t} + D_2 e^{-500t}$ ,  $t \geq 0$ .

The initial current in the inductor ( $I_0$ ) is -10 mA, and the initial voltage on the capacitor ( $V_0$ ) is 8 V. The inductor has an inductance of 4 H.

- a) Find the values of  $R$ ,  $C$ ,  $D_1$  and  $D_2$ .
- b) Find  $i_C(t)$  for  $t \geq 0^+$ .

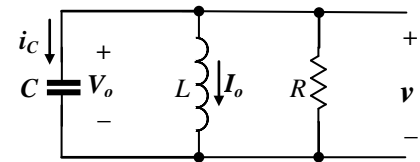


Fig.3

$R = 1 \text{ K}\Omega$

$C = 1 \text{ }\mu\text{F}$

$D_1 = 6000 \text{ V/S}$

$D_2 = 8 \text{ V}$

$i_C(t) = -3 t e^{-500t} + 2 \times 10^{-3} e^{-500t} \text{ A}$

**Question #4: (12 Points)**

A three-phase Y-connected +ve sequence source having the phase voltage  $V_a = 260 \angle 0^\circ \text{ V}$ . The source resistance is  $1 \text{ }\Omega/\text{Phase}$ . The source supplies a balanced  $\Delta$ -connected load having an impedance of  $(27 + j15) \text{ }\Omega/\text{Phase}$ . The three lines connecting the source to the load have a resistance of  $2 \text{ }\Omega/\text{Line}$ . Find the following:

The Line current $\overline{I_A} =$	$20 \angle -22.6^\circ \text{ A}$
The phase current $\overline{I_{AB}}$ at the load =	$11.55 \angle 7.4^\circ \text{ A}$
The line voltage $\overline{V_{AB}}$ at the load =	$356.7 \angle 36.4^\circ \text{ V}$
The phase voltage $\overline{V_a}$ at the source terminals =	$241.7 \angle 1.8^\circ \text{ V}$
The line voltage $\overline{V_{ab}}$ at the source terminals =	$418.6 \angle 31.8^\circ \text{ V}$
The total power dissipated in the load =	$10.8 \text{ KW}$

**Question #5: (12 Points)**

The sinusoidal voltage source in the circuit of Fig.5 is operating at a frequency of 200 Krad/s. The coefficient of coupling is adjusted until the peak amplitude of  $i_1$  is pure real.

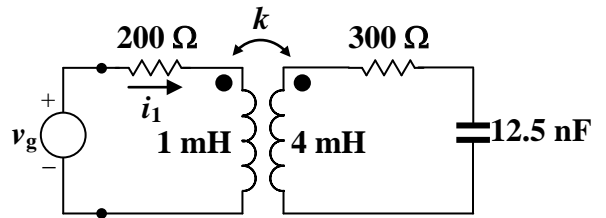


Fig.5

- a) What is the value of  $k$ ?
- b) What is the peak amplitude of  $i_1$  if  $v_g = 112 \cos(2 \times 10^5 t) \text{ V}$  ?

$$Z_r = 64 k^2(3 - j4)$$

$$i_1 = \frac{v_g}{200 + j200 + 64k^2(3 - j4)}$$

$$4 \times 64 k^2 = 200$$

$$k = 0.88$$

$$i_{1(\text{peak})} = 0.32 \text{ A}$$

**Question #6: (12 Points)**

Find the voltage transfer function and its poles and zeros for the circuit of Fig.6. If we consider this circuit as a bandpass filter, find approximate values for its magnitude transfer function at  $\omega = 0$  and at its central frequency. Find also the value of its bandwidth.

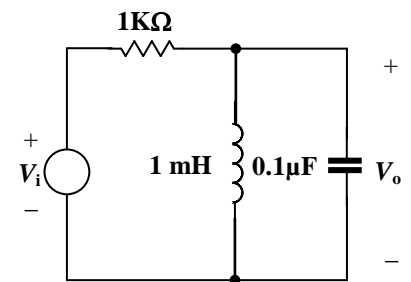


Fig.6

$$H_v(s) = \frac{10^4 s}{s^2 + 10^4 s + 10^{10}}$$

Poles:  $-5 \pm j 99.87 \text{ Krad/s}$

Zeros:  $0, \infty$

$$|H_v(0)| = 0$$

$$|H_v(j\omega_0)| = 1$$

$$\text{BW} = 10^4 \text{ rad/s}$$

**Question #7: (12 Points)**

There is no energy stored in the circuit of Fig.7 at the time the current source is energized. Use the Laplace Transform to find the nodal voltages.

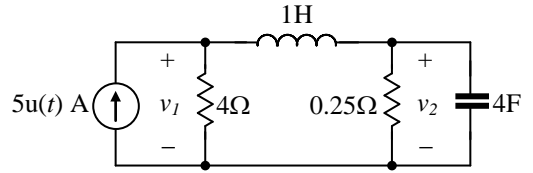


Fig.7

Eq. (1):  $(s + 4)V_1 - 4 V_2 = 20$

Eq. (2):  $-V_1 + (4s^2 + 4s + 1) V_2 = 0$

$V_1(s) = \frac{20(s^2 + s + 0.25)}{s(s^2 + 5s + 4.25)}$

$V_2(s) = \frac{5}{s(s^2 + 5s + 4.25)}$

$v_1(t) = 1.18 - 16.38e^{-1.09t} + 35.2e^{-3.91t}$

$v_2(t) = 1.18 - 1.63e^{-1.09t} + 0.45e^{-3.91t}$

**Question #8: (6 Points)**

A periodic voltage having a period of  $10\pi \mu\text{s}$  is given by the following Fourier series:

$$v_g = 150 \sum_{n=1,3,5,\dots}^{\infty} \frac{1}{n} \sin \frac{n\pi}{2} \cos n\omega_o t \text{ V}$$

This periodic voltage is applied to the circuit shown in Fig.8. Find the amplitude and phase angle of the first three components of  $v_o$ .

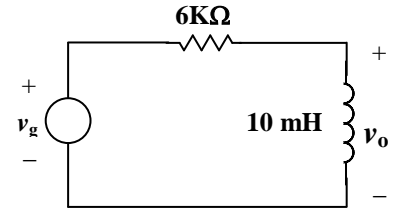


Fig.8

$\omega_o = 2\pi/T = 200 \text{ Krad/s}$

$v_g = 150 \cos \omega_o t - 50 \cos 3\omega_o t + 30 \cos 5\omega_o t$

$v_o = \frac{j2n}{6 + j2n} v_g$

$V_{o1} = 47.43 \angle 71.6^\circ \text{ V}$

$V_{o3} = 35.34 \angle -135^\circ \text{ V}$

$V_{o5} = 25.73 \angle 31^\circ \text{ V}$

**Question #9: (8 Points)**

Find the s-domain expressions for the  $a$  parameters of the two-port circuit shown in Fig.9.

$a_{11} = 1 + \frac{1}{4s}$

$a_{12} = s + \frac{1}{4} + \frac{1}{s}$

$a_{21} = \frac{1}{4}$

$a_{22} = \frac{s}{4} + 1$

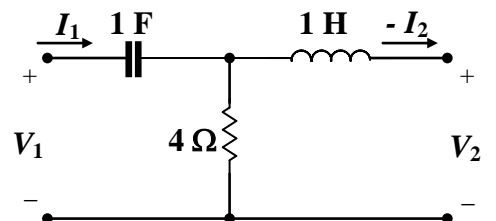


Fig.9

\*\*\*\*\*

أطيب التمنيات بالتوفيق  
أ.د. مجدى مفيد دوس

\*\*\*\*\*



Model Answer

Attempt all questions, full mark: 100 Points

Time: 3 Hours

Question #1: (12 Points)

The circuit shown in Fig.1 is used to measure the change in resistance experienced by strain gages.

- Derive an expression for the output voltage  $V_{out}$  in terms of the resistance values and the reference voltage  $V_{ref}$ , assuming ideal op-amp and neglecting  $\Delta R^2$  w.r.t.  $R^2$ . (8 Points)
- If  $R = 160 \Omega$ ,  $\Delta R = 1 \Omega$ ,  $R_f = 1.2 \text{ K}\Omega$ , and  $V_{ref} = 8 \text{ V}$ ; find the value  $V_{out}$ . (4 Points)

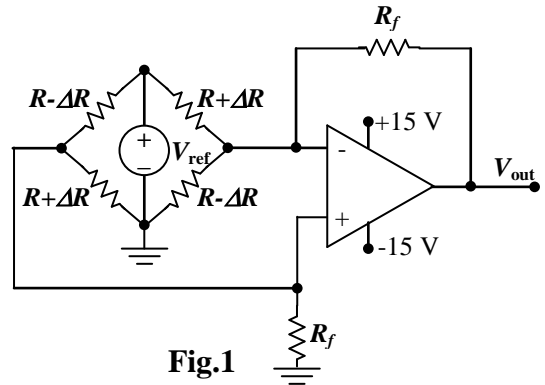


Fig.1

Expression for  $V_{out}$ :

$$V_{out} = \frac{2R_f \Delta R}{R^2} \cdot V_{ref}$$

Value of  $V_{out}$ :

$$V_{out} = 0.75 \text{ V}$$

Question #2: (16 Points)

In the circuit shown in Fig.2, the initial currents in inductors  $L_1$  and  $L_2$  are 8A and 1A respectively. The switch is opened at  $t = 0$ .

- Find  $i(t)$ , for  $t \geq 0$ . (8 Points)
- Find  $v(t)$ , for  $t \geq 0$ . (2 Points)
- Find  $i_1(t)$  and  $i_2(t)$ , for  $t \geq 0$ . (4 Points)
- Determine the total energy stored in the inductors as  $t \rightarrow \infty$ . (2 Points)

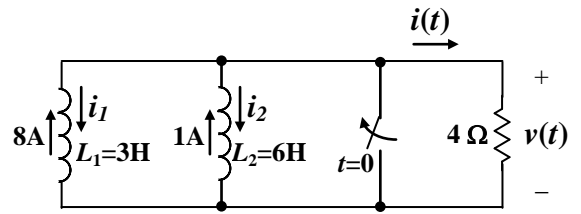


Fig.2

$$i(0^+) = 9 \text{ A}$$

$$i(\infty) = 0$$

$$\tau = 0.5 \text{ S}$$

$$i(t) = 9 e^{-2t} \text{ A}$$

$$v(t) = 36 e^{-2t} \text{ V}$$

$$i_1(t) = -2 - 6 e^{-2t} \text{ A}$$

$$i_2(t) = 2 - 3 e^{-2t} \text{ A}$$

$$\text{Energy stored in the inductors as } t \rightarrow \infty = 18 \text{ J}$$

**Question #3: (12 Points)**

The switch in the circuit shown in Fig.3 has been in position (a) for a long time. At  $t = 0$ , it moves to position (b). Find  $i(0^+)$ ,  $v_c(0^+)$ ,  $di(0^+)/dt$ , the roots of the characteristic equation  $s_1, s_2$  and  $i(t)$  for  $t \geq 0$ .

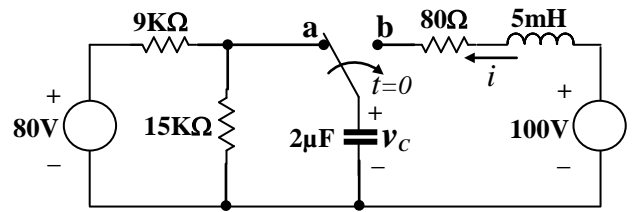


Fig. 3

$i(0^+) = 0$

$v_c(0^+) = 50 \text{ V}$

$di(0^+)/dt = 10^4 \text{ A/S}$

$s_1 = -8000 + j 6000$

$s_2 = -8000 - j 6000$

$i(t) = 1.6736 e^{-8000t} \sin(6000t) \text{ A}$

**Question #4: (12 Points)**

A three-phase  $\Delta$ -connected -ve sequence source having the phase voltage  $V_{ab}=240\angle 0^\circ \text{V}$  and negligible source resistance. The source supplies a resistive unbalanced  $\Delta$ -connected load having impedances:  $R_{AB}= 60 \Omega$ ,  $R_{BC}= 40 \Omega$ , and  $R_{CA}= 80 \Omega$ . The three lines connecting the source to the load have negligible resistances. The load power is measured using the two wattmeter method. The first wattmeter  $W_1$  is connected between lines A and B, while the second one  $W_2$  is connected between lines C and B. Find the following:

The phase current  $\overline{I_{AB}}$  at the load =

$4\angle 0^\circ \text{ A}$

The Line current  $\overline{I_A} =$

$6.08\angle 25.3^\circ \text{ A}$

The Line current  $\overline{I_C} =$

$7.94\angle 79.1^\circ \text{ A}$

The reading of  $W_1 =$

$1.32 \text{ KW}$

The reading of  $W_2 =$

$1.8 \text{ KW}$

The total power dissipated in the load =

$3.12 \text{ KW}$

**Question #5: (14 Points)**

The voltage source  $v_g$  drives the circuit shown in Fig.5. The response signal is the voltage across the capacitor,  $v_o$ .

- a) Calculate the numerical expression for the voltage transfer function  $H_v(s) = V_o(s)/V_g(s)$ . (6 points)
- b) Calculate the numerical values for the poles and zeros of the transfer function. (4 points)
- c) The circuit is driven by a step voltage source, namely,  $v_g = 50u(t)$ , find  $v_o(t)$ . (4 points)

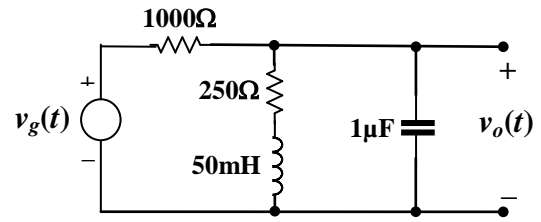


Fig.5

$$H_v(s) = \frac{1000(s + 5000)}{s^2 + 6000s + 25 \times 10^6}$$

**Poles:**  $-3000 + j4000, -3000 - j4000$

**Zeros:**  $-5000, \infty$

$$V_{out}(t) = [10 + 11.18 e^{-3000t} \cos(4000t - 153.4^\circ)]u(t) \text{ V}$$

**Question #6: (12 Points)**

The ideal transformer used in the circuit of Fig.6 has a turns ratio  $N_2/N_1 = 3$ .

- a) Find the reflected impedance at terminals a-b of that transformer. (6 Points)
- b) Calculate the value of the currents  $I_1, I_2, I_3$ , and  $I_4$ . (6 Points)

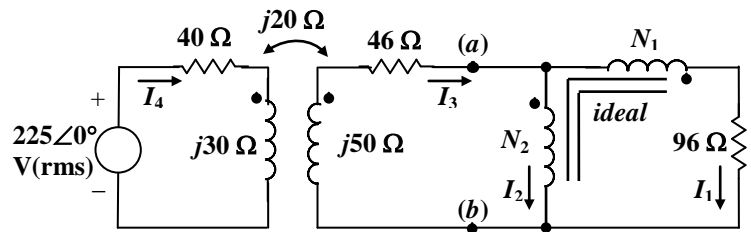


Fig.6

$$Z_R = \left(\frac{a}{1+a}\right)^2 R_L = 54\Omega$$

$$I_1 = 0.584 \angle 30.1^\circ \text{ A}$$

$$I_2 = 0.195 \angle 30.1^\circ \text{ A}$$

$$I_3 = 0.779 \angle 30.1^\circ \text{ A}$$

$$I_4 = 4.35 \angle -33.3^\circ \text{ A}$$

**Question #7: (6 Points)**

- a) Calculate the impedance of the circuit shown in Fig.7 at radian frequency of 2 Krad/S. (2 Points)
- b) At what finite frequency ( $\omega_r$ ) does the impedance of the circuit become purely resistive? What is the impedance at that frequency? (4 Points)

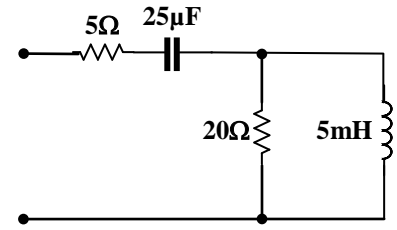


Fig.7


$Z(2\text{Krad}) = 9 - j12 \Omega$

$\omega_r = 4 \text{ Krad/S}$

$Z(\omega_r) = 15 \Omega$

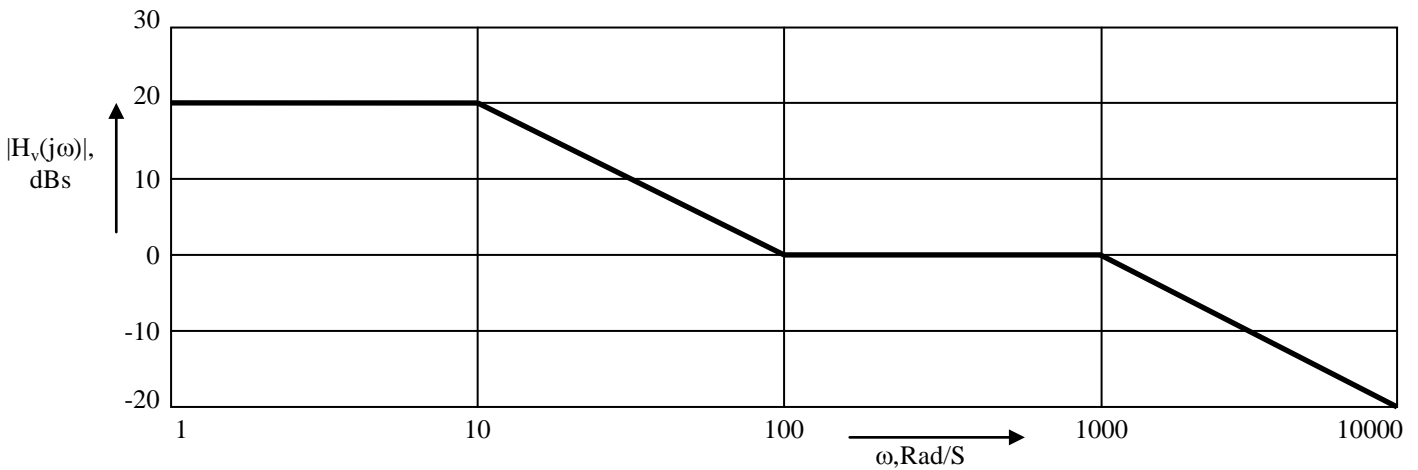**Question #8: (8 Points)**

Sketch the Bode Diagram of the voltage transfer function:  $H_v(s) = \frac{1000(s + 100)}{(s + 10)(s + 1000)}$



**Question #9: (8 Points)**

The y parameters for the two-port network in Fig.9 are:  $y_{11} = 2\text{mS}$ ,  $y_{12} = -0.2\text{mS}$ ,  $y_{21} = 10\text{mS}$ , and  $y_{22} = -0.5\text{mS}$ . Find  $V_1$ ,  $V_2$ ,  $I_1$ , and  $I_2$ .

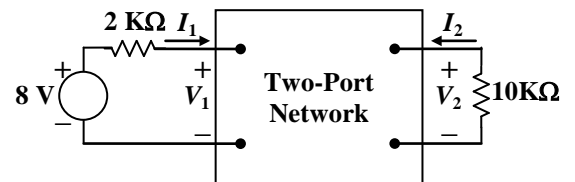


Fig.9

$V_1 = -1.6 \text{ V}$

$V_2 = -40 \text{ V}$

$I_1 = 4.8 \text{ mA}$

$I_2 = 4 \text{ mA}$






الامتحان مكون من أربع صفحات، الإجابة في نفس ورقة الأسئلة، النهاية العظمى ١٠٠ درجة.  
الإجابة النهائية يجب أن تكون مكتوبة في المكان المخصص لها وخطوات الحل تكون في الصفحة المقابلة.

**Attempt all questions, full mark: 100 Points**

**Time: 3 Hours**

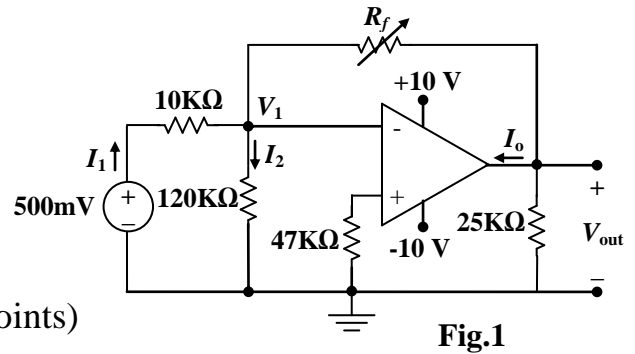**Question #1: (12 Points)**

The feedback resistance  $R_f$  in the circuit of Fig.1 is variable. Assuming ideal op-amp find:



- The range of values for  $R_f$  in which the op-amp does not saturate. (2 Points)
- $V_{out}$ ,  $I_o$ ,  $I_1$ , and  $I_2$  for  $R_f = 50 \text{ K}\Omega$ . (4 Points)
- $V_{out}$ ,  $V_1$ ,  $I_o$ ,  $I_1$ , and  $I_2$  for  $R_f = 360 \text{ K}\Omega$ . (6 Points)

a)  $0 \leq R_f \leq 200 \text{ K}\Omega$

b)  $V_{out} = -2.5 \text{ V}$        $I_o = 150 \mu\text{A}$        $I_1 = 50 \mu\text{A}$        $I_2 = 0$

c)  $V_{out} = -10 \text{ V}$        $V_1 = 200 \text{ mV}$        $I_o = 428.3 \mu\text{A}$        $I_1 = 30 \mu\text{A}$        $I_2 = 1.67 \mu\text{A}$

**Question #2: (16 Points)**

Both switches in the circuit in Fig.2 have been closed for a long time. At  $t = 0$ , both switches open simultaneously.

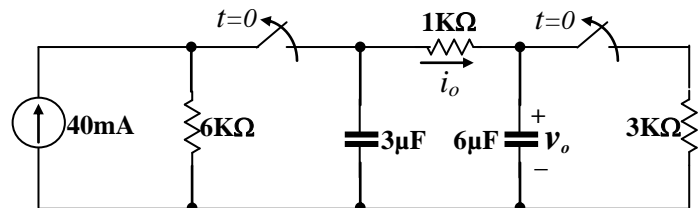


Fig. 2

$i_o(0^+) = 24 \text{ mA}$

$i_o(\infty) = 0$

$\tau = 2\text{mS}$

$i_o(t) = 24 e^{-500t}$

$v_o(t) = 80 - 8 e^{-500t}$

Energy trapped in the circuit = 28800  $\mu\text{J}$

**Question #3: (12 Points)**

The switch in the circuit shown in Fig.3 has been closed for a long time. The switch opens at  $t = 0$ . Find  $v_c(0^+)$ ,  $i_L(0^+)$ ,  $[dv_c/dt]_{0^+}$ , the roots of the characteristic equation  $s_1, s_2$  and  $v_c(t)$  for  $t \geq 0$ .

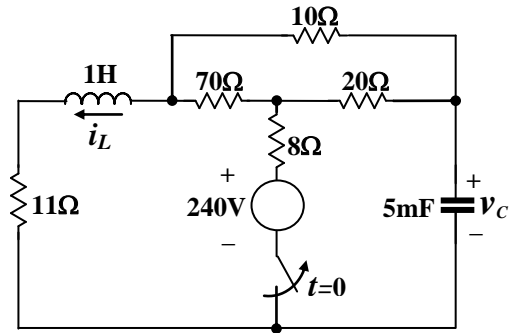


Fig. 3

$$v_c(0^+) = 108 \text{ V}$$

$$i_L(0^+) = 6 \text{ A}$$

$$[dv_c/dt]_{0^+} = - 1200 \text{ V/S}$$

$$s_1 = -10 - j10$$

$$s_2 = -10 + j10$$

$$v_c(t) = (108 \cos 10t - 12 \sin 10t)e^{-10t} \text{ volts}$$

**Question #4: (12 Points)**

A three-phase Y-connected +ve sequence source having the phase voltage  $V_a=220\angle 0^\circ\text{V}$ . The source resistance is  $1 \Omega/\text{Phase}$ . The source supplies a balanced  $\Delta$ -connected load having an impedance of  $(30 + j12) \Omega/\text{Phase}$ . The three lines connecting the source to the load have an impedance of  $1+j1 \Omega/\text{Line}$ . Find the following:

The Line current  $\overline{I_B} =$  **16.9  $\angle$ -142.6° A**

The phase current  $\overline{I_{AB}}$  at the load=**9.77  $\angle$ 7.4° A**

The Line voltage  $\overline{V_{BC}} =$  **315.6  $\angle$ -90.8° V**

The phase voltage  $\overline{V_a}$  at the source terminals=**204.5  $\angle$ 1.8° V**

The Line voltage  $\overline{V_{ab}}$  at the source terminals=**354.2  $\angle$ 31.8° V**

The total power dissipated in the load = **8.592 KW**

**Question #5: (12 Points)**

Use the Laplace transform to find  $v_o$  and  $v_1$  in the circuit shown in Fig.5 if  $i_g = 10u(t)$  mA and  $\alpha = 75$  mA/V. There is no energy stored in the circuit at  $t=0$ .

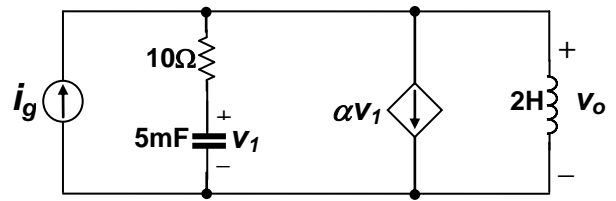


Fig.5

$$V_o(s) = \frac{0.1(s + 20)}{s^2 + 20s + 100} = \frac{0.1}{s + 10} + \frac{1}{(s + 10)^2}$$

$$V_1(s) = \frac{2}{(s + 10)^2}$$

$$v_o(t) = (t + 0.1)e^{-10t} \text{ volts}$$

$$v_1(t) = 2te^{-10t} \text{ volts}$$

**Question #6: (12 Points)**

The linear transformer used in the circuit of Fig.6 has a coupling coefficient  $k = 0.5$ .

a) Calculate the impedance reflected into the primary winding  $Z_r$ . (4 Points)

b) Calculate the impedance seen looking into the primary terminals of the transformer  $Z_{ab}$ . (2 Points)

c) Calculate the Thevenin equivalent with respect to the terminals  $c,d$ . (6 Points)

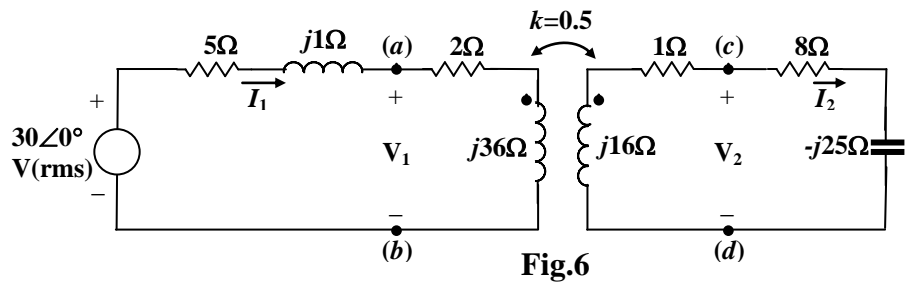


Fig.6

$$Z_r = 8 + j8 = 11.31 \angle 45^\circ \Omega$$

$$Z_{ab} = 10 + j44 = 45.12 \angle 77.2^\circ \Omega$$


$$Z_{Th} = 1.71 + j12.24 = 12.36 \angle 82^\circ \Omega$$

$$V_{Th} = 9.39 + j1.77 = 9.56 \angle 10.7^\circ \text{ V}$$

**Question #7: (8 Points)**

Fig.7 shows an *R-L* high pass filter.

- a) What is the transfer function,  $H(s) = V_o(s)/V_i(s)$ , of this filter? (4 Points)
- b) What is the cutoff frequency of this filter? (2 Points)
- c) What is the maximum value of the transfer function; and at what frequency does it occur? (2 Points)

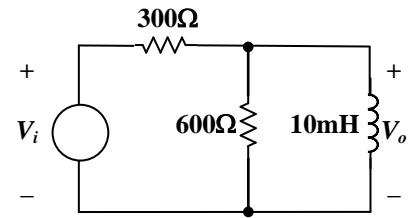

**Fig.7**


$$H(s) = \frac{2s}{3s + 6 \times 10^4}$$

$\omega_c = 2 \times 10^4 \text{ Rad/Sec}$

$H_{max} = 2/3 \quad \text{at } \omega = \infty$

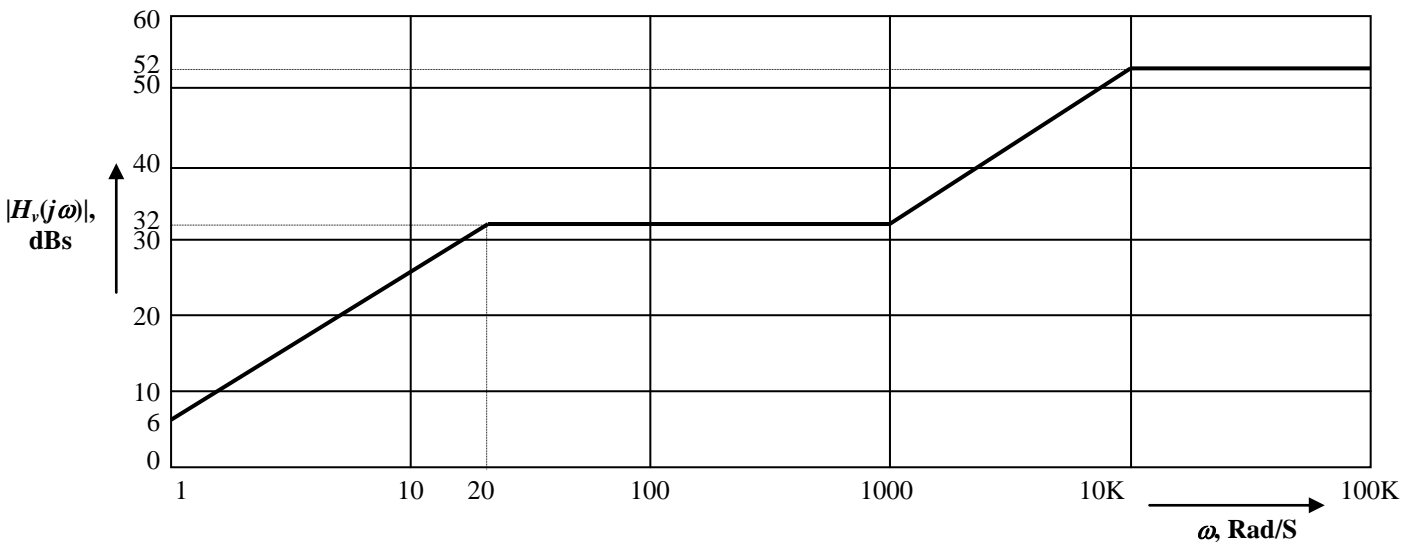
**Question #8: (8 Points)**

Sketch the Bode Diagram of the voltage transfer function:  $H_v(s) = \frac{400s(s+1000)}{(s+20)(s+10000)}$



**Question #9: (8 Points)**

Find the *h* parameters of the two-port circuit shown in Fig.9.

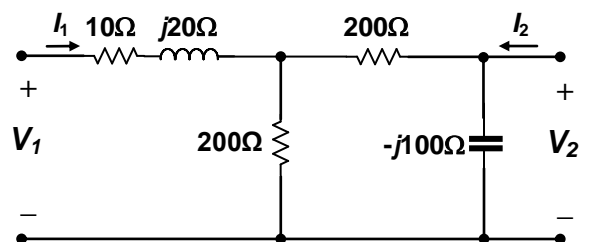

**Fig.9**

$h_{11} = 110 + j20 \Omega$

$h_{12} = 0.5$

$h_{21} = -0.5$

$h_{22} = 2.5 + j10 \text{ mS}$

**Answer All Questions, assume any missing data you may need.**

1. a) Draw a neat sketch showing a double railway?  
b) What are the types of sleepers which are used in railroad, describe the advantage of each type?  
c) A railway line of Max. speed 140 km/hr, with normal track width, wooden sleeper and distance from centerline to centerline is 60 cm, the Max. axial load is 26 ton, and distance between axis is more than 3.0 m.  
It is required to:
  - i) Design cross section of Vignole Rail from first assumption.
  - ii) Draw Vignole Rail with scale 1:1.
  - iii) Bending and normal stress in sleeper which cross section is 26x16 cm, if the plate width under rail is 150 mm
  
2. a) Draw a flow chart showing the main stages in transportation planning procedure.  
b) State the main factors affecting highways design.  
c) It is proposed to widen a two-way highway because of traffic congestion, where counts show that the ADT (2007) is 3500 vehicle/day of which 15% trucks. A traffic development due to improvements on land adjacent to the highway by the end of the design period (2027) is expected to be 600 pcu's/hour.  
Average normal traffic growth 5% /year,  
(D<sub>HV</sub>/ADT) = 0.15,  
Directional distribution factor (D) = 70%,  
Practical lane capacity = 600 pcu's/hour.  
It is required to:
  - i) Design the cross section of the proposed new highway.
  - ii) Draw your designed cross section showing all dimensions, where the original ground level = (11.00) m and the road level = (13.00) m.

*Examiners*

*Dr. Mahmoud Enieb*

*Dr. Ghada S. Moussa*



قسم الهندسة المعمارية  
مقرر شق الضوء- هم ٢٢٢  
ثانية عمارة - لائحة ٢٠٠٤  
الزمن: ٣ ساعات مع الصوت ونكف  
الدرجة: ٢٠ درجة

كلية الهندسة  
جامعة أسيوط  
إمتحان نهاية الفصل الدراسي الثاني  
2014 / 2015



ملاحظات هامة  
• الإمتحان يقيس مهارات أ. ١. ١، ب. ١٥. ٤، ج. ٢. ٢.  
• الإمتحان مكون من ١ صفحة - ٢ أسئلة + ٢ جداول

### أجب عن الأسئلة التالية

السؤال الأول (١٢ درجة):


المطلوب: اجب عن الأسئلة الآتية:

- أ. ماهي أنواع الإبهار طبقا للآتي: لطبيعة المصدر- كيفية النظر- ظروف الرؤية، وكيف يمكن تلافيه. (٣ درجات)
- ب. سطح عمل ابعاده  $٤*٤$  م والمطلوب حساب نوع توزيع الإضاءة لكي يتم تحقيق شدة استضاءة قدرها  $٣٥٠$  lux في حالات تركيب أجهزة إضاءة الفيض الكلي بالليومن لها كالأتي:  $٢٠٨٠٠-٢٠٨٠٠٠-١٠٩٤٧-١٣٨٦٦-٤١٦٠٠$  (٥ درجات)
- ج. فراغ على شكل منشور سداسي ناقص ضلع القاعدة  $٢٠$  م، والارتفاع عند اعلي نقطة  $٩$  م و اقل نقطة  $٦$  م، قس بين شدة الاستضاءة في نقطتين بالأرضية، الأولى في مركز الأرضية السداسية، والنقطة الثانية على المحيط مقابلة لنقطة في السقف وذلك في حالة تعليق نجفة بمركز السقف قوتها  $٤٠٠٠$  شمعة قياسية منخفضة عن المركز بمقدار  $٣$  م (٤ درجات)


السؤال الثاني: (٨ درجة)

المطلوب اجب عن الأسئلة الآتية:

- أ- ماذا تعرف عن نظام الإضاءة SOLAR TUBE و متى يمكن تطبيقه في المباني (٢ درجات)
- ب- احسب عدد الأجهزة وتوزيعها في فراغ مكتبة مدرسية- أبعادها موضحة بالرسم - والتي تكفل تحقيق مستوى استضاءة على مناخذ القراءة قدرها  $٥٥٠$  Lux لو كس بحيث يكون معامل الانعكاس للسقف Ceiling reflection  $٥٠\%$ ، وللجدران Wall reflection  $٣٠\%$ ، ومعامل الصيانة  $٠,٧٥$ .
- يستعمل مصباح الفلورسنت  $٤٠$  وات طولها  $٦٠$  سم والفيض التصميمي له  $١٧٠٠$  Lumen ليومن، و الأجهزة من النوع المركز ذات العواكس المرأوية. (٦ درجات)

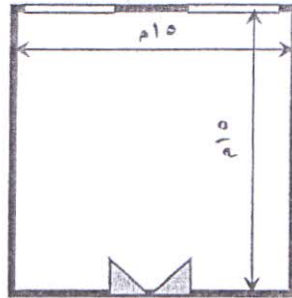

مسقط أفقي

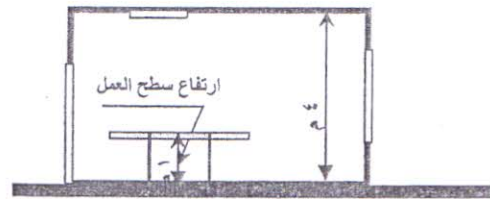

قطاع رأسي

انتهت الأسئلة

مع اطيب الدعاء بالتوفيق،،،،


د. محمد عبد الوهاب


+ الجواب

١


Appendix 3 continued  
Utilization factors

جدول ٣-١-٠  
عوامل الاستفاد

Luminaire, and Typical Light Output Ratio %	Typical Outline	Reflectance % عوامل الانعكاس										
		Basic	Celling	70			60			30		
		DLOR										
		Walls	50	30	10	50	30	10	50	30	10	
		% Room Index دليل الغرفة										
Colour-corrected mercury lamp مصباح زئبقى عاكس اللون		85	0.6	0.4	0.34	0.3	0.39	0.33	0.29	0.37	0.32	0.29
		0.8	0.53	0.48	0.41	0.51	0.45	0.4	0.49	0.43	0.4	
		1	0.62	0.55	0.49	0.58	0.52	0.48	0.58	0.51	0.46	
		1.25	0.68	0.6	0.55	0.64	0.58	0.53	0.61	0.56	0.51	
		1.5	0.72	0.65	0.59	0.68	0.62	0.57	0.65	0.59	0.54	
		2	0.81	0.73	0.67	0.75	0.69	0.64	0.69	0.65	0.61	
2.5	0.85	0.78	0.72	0.79	0.73	0.69	0.73	0.68	0.65			
3	0.9	0.83	0.78	0.83	0.78	0.75	0.77	0.73	0.7			
4	0.94	0.89	0.84	0.87	0.83	0.8	0.8	0.77	0.75			
5	0.97	0.92	0.89	0.9	0.87	0.84	0.83	0.79	0.77			

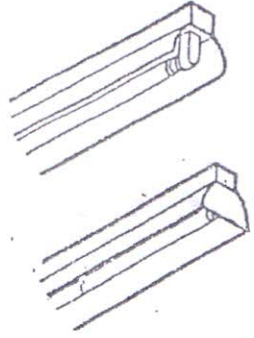Enamel trough (75-85) مخروطية مغلي	Typical Outline	Reflectance %										
		Basic	Celling	70			60			30		
		DLOR										
		Walls	50	30	10	50	30	10	50	30	10	
		% Room Index										
Enamel trough (85-83)		75	0.6	0.38	0.31	0.28	0.35	0.31	0.28	0.35	0.31	0.28
		0.8	0.45	0.4	0.37	0.44	0.4	0.37	0.44	0.4	0.37	
		1	0.49	0.45	0.4	0.49	0.44	0.4	0.48	0.43	0.4	
		1.25	0.55	0.49	0.40	0.53	0.49	0.45	0.52	0.48	0.44	
		1.5	0.58	0.54	0.49	0.57	0.53	0.49	0.55	0.52	0.49	
		2	0.64	0.59	0.55	0.61	0.58	0.55	0.6	0.58	0.54	
2.5	0.68	0.63	0.6	0.65	0.62	0.59	0.64	0.61	0.58			
3	0.7	0.65	0.62	0.67	0.64	0.61	0.65	0.63	0.61			
4	0.73	0.7	0.67	0.7	0.67	0.65	0.67	0.66	0.64			
5	0.75	0.72	0.69	0.73	0.7	0.67	0.7	0.68	0.66			

Dispersive industrial reflector (77) عاكس مبعثر صناعي	Typical Outline	Reflectance %										
		Basic	Celling	70			60			30		
		DLOR										
		Walls	50	30	10	50	30	10	50	30	10	
		% Room Index										
Industrial reflector (72-76) عاكس صناعي مبعثر		70	0.8	0.39	0.38	0.33	0.39	0.38	0.33	0.39	0.35	0.7
		0.8	0.48	0.43	0.4	0.48	0.43	0.4	0.48	0.43	0.4	
		1	0.52	0.48	0.45	0.52	0.48	0.45	0.52	0.48	0.4	
		1.25	0.58	0.53	0.5	0.58	0.53	0.48	0.58	0.52	0.4	
		1.5	0.6	0.57	0.54	0.59	0.57	0.53	0.59	0.55	0.4	
		2	0.65	0.62	0.59	0.63	0.6	0.58	0.63	0.59	0.4	
2.5	0.67	0.64	0.62	0.65	0.62	0.61	0.65	0.62	0.4			
3	0.69	0.68	0.64	0.67	0.64	0.63	0.67	0.64	0.4			
4	0.71	0.68	0.67	0.69	0.67	0.65	0.69	0.66	0.4			
5	0.72	0.7	0.69	0.71	0.69	0.67	0.71	0.67	0.4			

Industrial reflector (72-76) عاكس صناعي مبعثر	Typical Outline	Reflectance %										
		Basic	Celling	70			60			30		
		DLOR										
		Walls	50	30	10	50	30	10	50	30	10	
		% Room Index										
Aluminium reflector (72) or (83)		70	0.8	0.39	0.38	0.33	0.39	0.38	0.33	0.39	0.35	0.7
		0.8	0.48	0.43	0.4	0.48	0.43	0.4	0.48	0.43	0.4	
		1	0.52	0.48	0.45	0.52	0.48	0.45	0.52	0.48	0.4	
		1.25	0.58	0.53	0.5	0.58	0.53	0.48	0.58	0.52	0.4	
		1.5	0.6	0.57	0.54	0.59	0.57	0.53	0.59	0.55	0.4	
		2	0.65	0.62	0.59	0.63	0.6	0.58	0.63	0.59	0.4	
2.5	0.67	0.64	0.62	0.65	0.62	0.61	0.65	0.62	0.4			
3	0.69	0.68	0.64	0.67	0.64	0.63	0.67	0.64	0.4			
4	0.71	0.68	0.67	0.69	0.67	0.65	0.69	0.66	0.4			
5	0.72	0.7	0.69	0.71	0.69	0.67	0.71	0.67	0.4			

مصابيح التوهج ومصابيح الفلورسنت

القيمة المسمية بالبرون  
 (للدفن الزمينة)  
 القطر  
 القوية  
 الفلوية  
 القطر  
 القوية  
 الفلوية  
 القطر  
 القوية  
 الفلوية

مصابيح التوهج

القيمة المسمية بالبرون

القيمة المسمية بالبرون  
 11. قوت  
 14. قوت  
 24. قوت  
 1.0  
 1.5  
 2.0  
 3.0  
 4.0  
 5.0  
 6.0  
 7.0  
 8.0  
 9.0  
 10.0  
 12.0  
 15.0  
 20.0  
 25.0  
 30.0  
 35.0  
 40.0  
 45.0  
 50.0  
 60.0  
 70.0  
 80.0  
 90.0  
 100.0

125	10	15	150	4
245	12	15	225	6
360	15	15	200	8
439	21	15	525	12
800	40	25	450	15
750	40	28	480	15
1100	50	28	700	20
9150	40	28	900	20
1850	40	28	900	20
1700	40	28	700	20
4700	50	28	1200	20
4250	70	25	1500	25
4750	80	28	1500	25
5700	88	28	1800	25
5700	95	28	1500	25
7100	95	28	1800	25
7700	100	28	2200	25
8700	120	28	2200	25

القيمة المسمية لباقي أنواع الفلورسنت  
 يمكن الحصول على هذه القيم بغيره القيمة المسمية  
 للدفن الزمينة في العاصمات التالية:

- WHITE 1
- WARM WHITE 1
- DAYLIGHT 0.95
- NATURAL 0.75
- HOME-LITE 0.7
- DELUXE WARM WHITE 0.65
- KOLOR-RITE 0.65
- COLOUR MATCHING (Hortilight) 0.6
- GRAPHIC A 47 0.6
- DELUXE NATURAL 0.55
- SOFTON 0.55
- TRUCOLOUR 0.5
- ARTIFICIAL DAYLIGHT 0.4

القيمة المسمية على الترتيب

200	225	70	1.0	20
290	225	70	1.5	20
775	575	70	1.5	70
1570	1170	1220	70	100
2040	---	---	78	125
2040	---	---	78	125
---	1970	5370	80	170
---	2720	2250	80	175
---	4200	8000	110	232
---	7700	8900	110	232
---	12400	---	180	200
---	17200	---	180	200
---	27500	---	170	235



ب- اشرح طريقة عمل الارضيات التراتزو مع توضيح اجابتك باسكتشات. (١٠ درجات)



برامج الهندسة المدنية  
مقرر الانشاء المعماري (A101)  
الفرقة الاولى - لائحة ٢٠٠٤  
الزمن: ٣ ساعات  
النهاية العظمى: ١٠٠ درجة

جامعة اسيوط

كلية الهندسة  
قسم الهندسة المعمارية  
امتحان نهاية الفصل الدراسي الثاني  
٢٠١٤/٢٠١٥ - يونيو ٢٠١٥



ملاحظات هامة  
• الامتحان يقسم مهارات ٣، ١، ٤، ١٠، ج، ١٤، ج، ١٥  
• الاجابة تتم في ورقة الاسئلة ويجب مراعاة الدقة ونظافة الرسومات  
• وضع اجابتك باسكتشات كلما أمكن  
• الامتحان في أربعة ورقات مقاس B3  
• الدقة في الرسم ونظافة اللوحة عامل مؤثر في الدرجة

السؤال الأول:

- ٢٠ درجة)  
١٠ درجات)  
أ- نكر الفرق بين (مع توضيح اجابتك بالرسم كلما أمكن ذلك):  
- أنواع المباني سابقة التجهيز الخطية والمستوية والصندوقية.

- مصطلح الكمرات المعتبة والكمرات المخدمة.



السؤال الثاني:

أ- عرف المصطلحات الآتية:

الطية:

بئر السلم:

مفتاح العقد:

تنفيخ العقد:

الفانوس:

(٣٠ درجة)

(١٠ درجات)

ب- ماهي اشتراطات البناء بالاحجار:

١-

٢-

٣-

٤-

٥-

(١٠ درجات)

ج- اذكر مع الرسم بكروكيات:


- أنواع الاساسات السطحية (لكل نوع رسمة واحدة فقط)

(١٠ درجات)

- أنواع الطبقات العازلة.

السؤال الثالث:

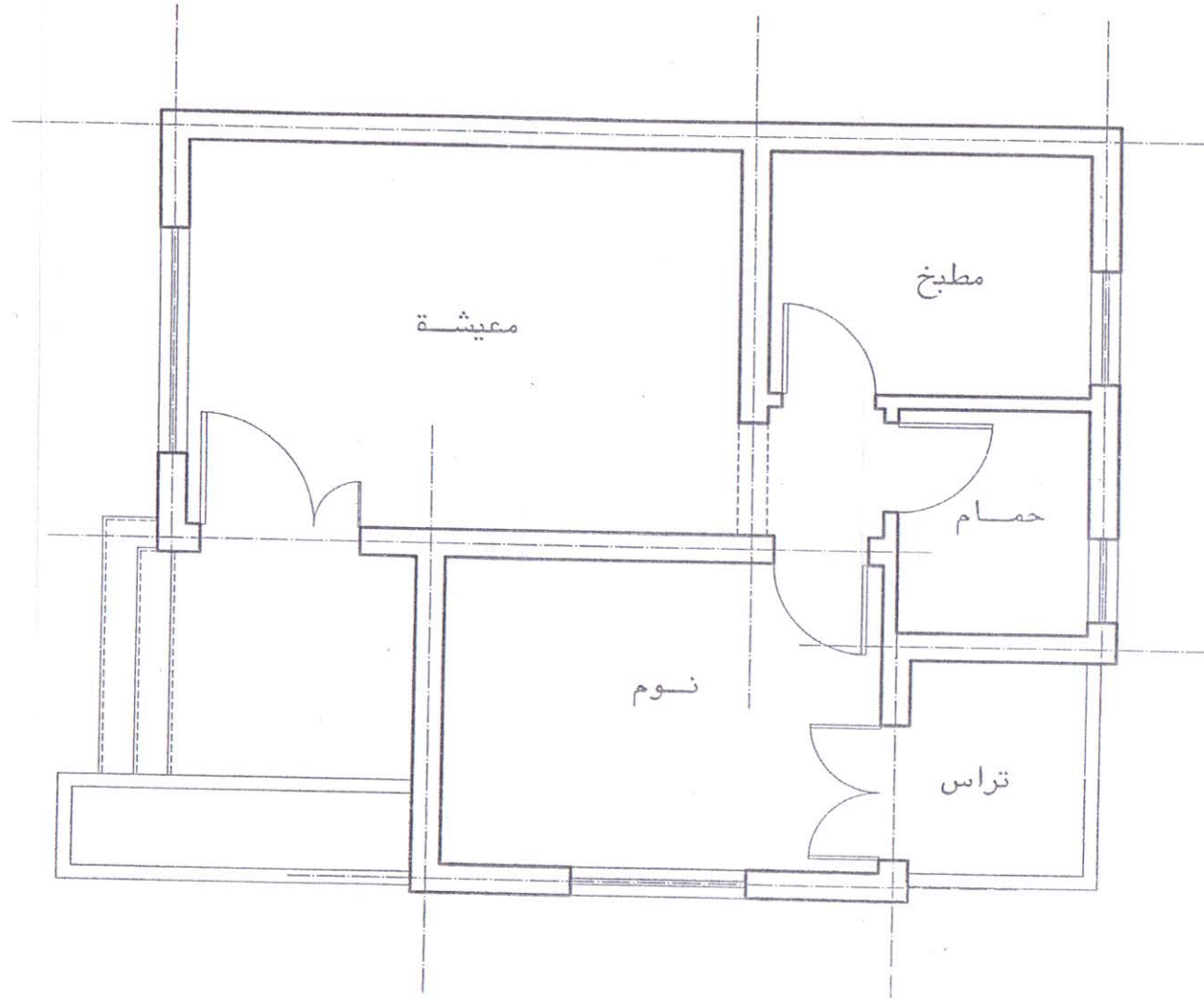يبين الرسم التالي مسقطاً أفقياً لشاليه مكون من دور واحد - والمطلوب اكمال المسقط الأفقى التالى ليصبح رسماً تنفيذياً. (مقياس الرسم ١/٥٠) (٢٥ درجة)




٣

(أ) ارسم الواجهة الامامية للشاليه مبينا عليها كافة الابعاد والبيانات بمقياس رسم ١/٥٠ (١٠ درجات)



(ب) ارسم تقصيلة لفاصل إنشائي بين مبنيين أحدهما مستمر والآخر منتهى على أن تحتوى التقصيلة على السقف النهائى لأحدهما والسقف الاوسط للمبنى الأخر مع إظهار كافة الطبقات على الرسم وكتابة انواعها ومقاساتها. (مقياس الرسم ١/٢٠) (١٠ درجات)

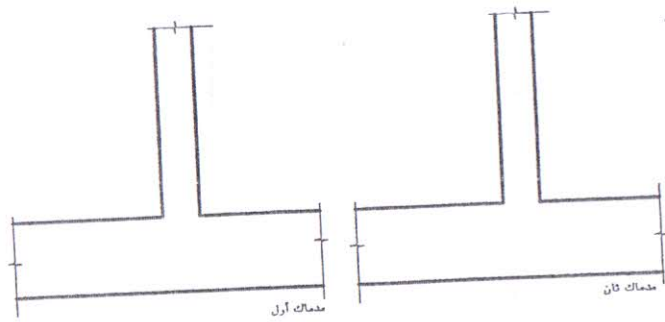ج- يبين الرسم التالى مسقطا افقيا لمبنيين متتاليين فى حائط -  
والمطلوب استكمال رسم المسقطين. (مقياس الرسم ١/٢٠) (٥ درجات)



حائطين متعامدين سمك طوبية على نصف طوبية

مع خالص تمنياتنا لكم بالتفويق والنجاح .....

د/ نادر مصطفى عبد الكريم - د/ محمد عبد الوهاب العزازى واللجنة





برنامج الهندسة المعمارية  
مقرر الظل والمنظور  
هعم ١٢٦  
الفرقة الأولى - لائحة ٢٠٠٤  
الزمن: ٤ ساعات  
الدرجة: ٧٠ درجة

قسم الهندسة المعمارية  
كلية الهندسة  
جامعة أسيوط  
إمتحان نهاية الفصل الدراسي الثاني  
٢٠١٤ - ٢٠١٥ م - دور مايو ٢٠١٥



### ملاحظات هامة

الإمتحان يقيس مهارات أ. مفاهيم ونظريات الرياضيات والعلوم الملائمة لتخصص الهندسة المعمارية. أ. ٢٠ النمذجة المادية، والتخيل متعدد الأبعاد، وتطبيقات الوسائط المتعددة، والتصميم بمساعدة الحاسب ب. ١٤ التفكير ثلاثي الأبعاد وربط صور الأماكن والأوقات مع الابتكار والإبداع في اعداد التصميم ج. ٦ استخدام مدى واسع من الأدوات التحليلية والتقنيات والتجهيزات والحزم البرمجية المرتبطة بالهندسة المعمارية وتطوير برمجيات الحاسوب المطلوبة. ج. ١٨ اظهار الخيال والإبداع. د. ٢ العمل في بيئة ضاغطة وضمن قيود

- الإمتحان مكون من ثلاثة أسئلة في أربعة ورقات (ورقة الأسئلة وثلاثة لوحات).
- الدقة في الرسم ونظافة اللوحة عامل مؤثر في الدرجة وللطالب الحرية في استخدام الألوان والأوراق الملونة والخامات.
- الصق الورقة رقم (٣) الخاصة بالانعكاس والورقة رقم (٤) والخاصة بالظل في المستويات ثنائية البعد وثلاثية الأبعاد بعد رسم المطلوب فيها في لوحة الاجابة.

### أجب عن الأسئلة التالية

السؤال الأول (٣٥ درجة) :

أمامك رسم معماري لمبنى كما هو موضح بالورقة رقم (٢). والمطلوب رسم المنظور الخارجي من الجهة المبينة بالشكل وبارتفاع خط النظر المناسب.

السؤال الثاني (١٥ درجة):

أمامك في الورقة رقم (٣) منظور لمبنى يطل على بحيرة، والمطلوب رسم انعكاس هذا المبنى على مستوى سطح الماء.

السؤال الثالث: (٢٠ درجة):

في الورقة رقم (٤) المطلوب رسم ما يلي ثم لصق الورقة في لوحة الاجابة:

(١٠ درجات)

أ- الظل على المستويات الأفقية والرأسية للتمرين رقم (س)

(١٠ درجات)

ب- الظل على المجسمات الأربعة الموضحة رقم (ص)

ورقة رقم (١)


----- إنتهت الأسئلة -----

مع تمنياتنا بالنجاح والتوفيق،،،،،


د.م. ممدوح علي يوسف + اللجنة



الواجهة الامامية

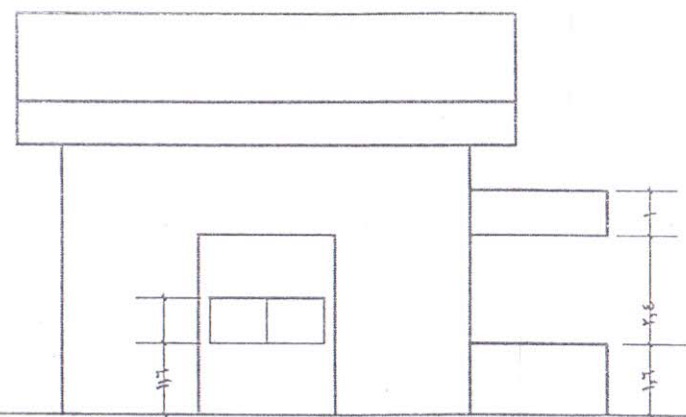


الواجهة الجانبية

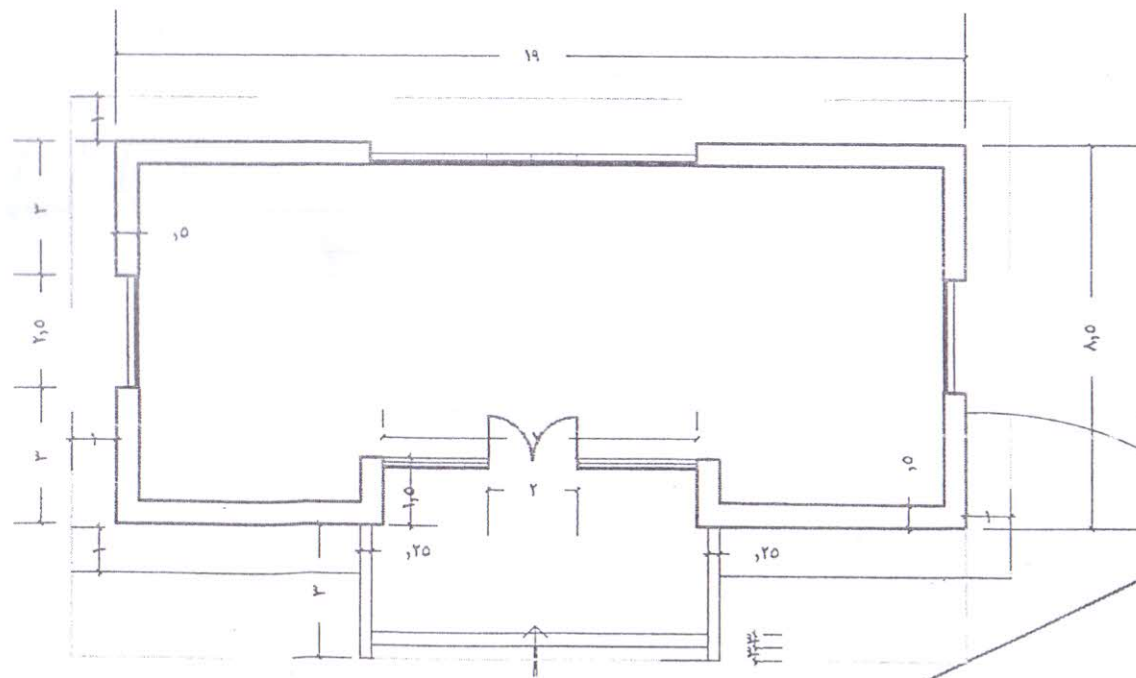

المطلوب رسم المنظور للمبنى  
وتخير ارتفاع خط النظر







مستوى الصورة يميل  
بزاوية 6.0 درجة

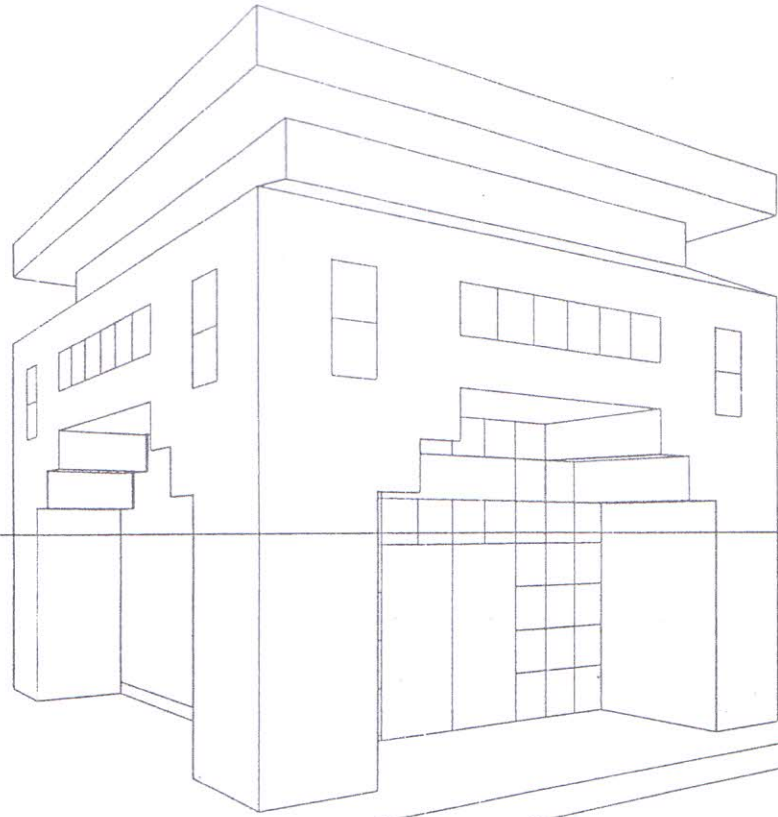

مادة الظل والمنظور  
المطلوب رسم الانعكاس

ورقة رقم ( ٣ )

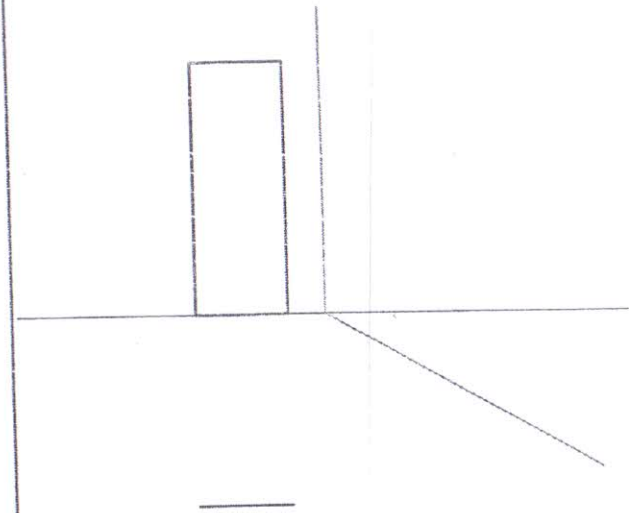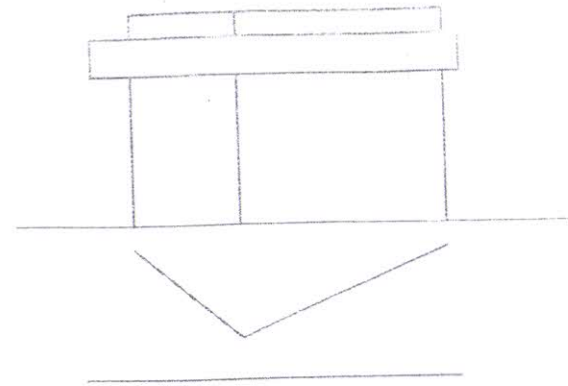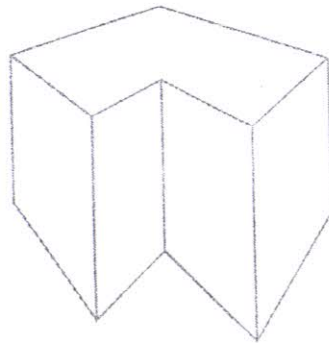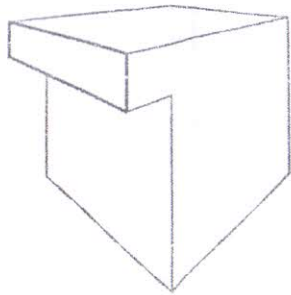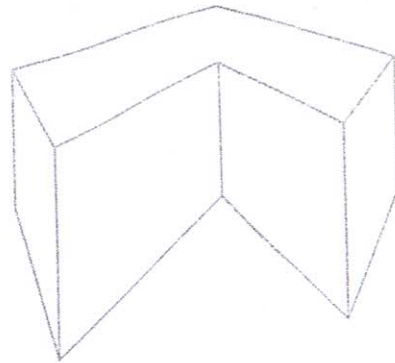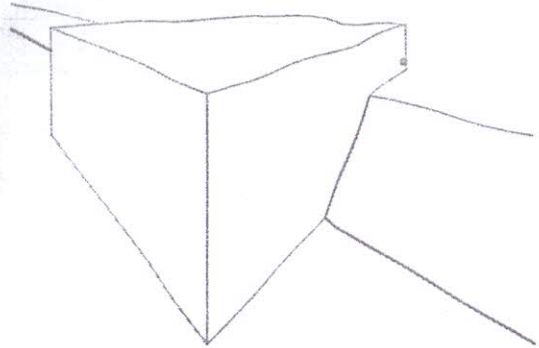كلية الهندسة - جامعة اسيوط  
قسم الهندسة المعمارية  
امتحان دور مايو ٢٠١٢



المطلوب رسم الظل (س)

كلية الهندسة - جامعة اسبوط  
قسم الهندسة المعمارية

المطلوب رسم الظل على المخطط (س)

ورقة رقم ( ٤ )

والله  
الأبعد

سوال  
تكره  
كل ويه

الثاني

الور  
٤

ش:

م  
الظ  
نجد





- Important remarks
- The Exam consists of 5 questions on 6 pages plus two white pages.
  - Answers should be in the specified area only.
  - You can use the white page for drafts
  - Read the questions carefully.

**Question no. 1** (19 points).

a) (6 pt) Determine whether the following statements are true or false. (In the box write just "√" or "X")

1	The <code>&gt;&gt; clc</code> command erases all variables in the workspace while the <code>&gt;&gt; clear</code> command clears all commands from the command window.	
2	The following is acceptable as a variable name: <code>2x</code> .	
3	In an input prompt:  <code>&gt;&gt; x = input('What is your name ?')</code> You Must enter your name as a letters.	
4	For any vector $A$ , $(A * A)$ will give the same results as $(A .* A)$ .	
5	Workspace variables cannot be saved and they are deleted completely when ending the MATLAB session and cannot be retrieved.	
6	The symbol <code>%</code> designates a comment which is not executed by MATLAB.	
7	The "for" loop is used when the looping process must terminate when a specified condition is satisfied and thus the number of passes is not known in advance.	
8	The semicolon <code>(.)</code> suppresses output when used with MATLAB commands and <code>(;)</code> terminates the MATLAB line.	
9	The Transpose command ( <code>trans</code> ) interchanges the rows and columns of a matrix and ( <code>inv</code> ) produces the inverse of the matrix.	
10	The <code>disp</code> command displays string during program execution while <code>echo</code> command displays array or string.	
11	The <code>&gt;&gt; eye(2,5)</code> produces an identity matrix with 2 rows and 5 columns.	
12	The <code>&gt;&gt; repmat(3,3,3)</code> produces a square matrix with 3 rows and 3 columns and all elements value is 3.	



b) (7 pt) For  $a = 2, b = 3, c = 4$  and  $d = 5$  Determine which of the following statements will correctly execute and provide the result. If the command will not correctly execute, state why it will not.

Statement	Correct or incorrect	Result: if it is correct or Why if it is incorrect
$X1=2*b*\sin(c*d)*\cos(a*b)$		
$X2=a*b*\tan(c*d)*\exp(ab)$		
$X3=\log(a*b)*\ln(a*b)*\text{sqrt}(2*a)$		
$X4=2*c*d*\tanh(a)*\text{acos}(b)*b*\sin(a)$		
$X5=a*b*s*d*(\text{sqrt}(c*d+a+b))$		
$X6=a*d*c*\text{asin}(1/b)*\text{acos}(1/b)*d$		
$X7=a^2*b^3*d^4*C^5$		

c) (6 pt) For the vector  $X=[5\ 1\ 3\ 2\ 6\ 8\ 9\ 7]$ . Find the value of the following Logical Expression.

Logical Expression	Value
$X1=X(X \leq 9)$	
$X2=X([2:\text{end}-2])$	
$X3=X(X \sim= 8)$	
$X4=[X(1:4)\ X(\text{end}-2:\text{end})]$	
$X5=[X(2:-1:1)\ X(\text{end}-1:\text{end})]$	
$X6=X(X \leq 3)$	

C

**Question no. 2 (12 points).**

- a) (7 pt) (Let  $x = [1 \ 4 \ 8]$ ,  $y = [2 \ 1 \ 5]$ ,  $A = [3 \ 1 \ 6; 5 \ 2 \ 7]$  and  $B = [3;6;4]$ . Determine which of the following statements will correctly execute and provide the result. If the command will not correctly execute, state why it will not.).

Statement	Correct or incorrect	Result: if it is correct or Why if it is incorrect
$x + y$		
$x + y'$		
$x * y$		
$x \cdot y'$		
$x * B$		
$A * B$		
$y * B$		

- b) (5 pt) Write a MATLAB code to plot the function  $T = 6\ln(t) - 7e^{0.2t}$  over the interval  $1 \leq t \leq 5$ . Put a title on the plot and properly label the axis where T represents the temperature, °C and t represents time, min.

**Question no. 3** (10 points).

- a) (5 pt) Write a script file using conditional statements to evaluate the following assuming scalar  $x$  has a value;

$$y = \begin{cases} x^2 & x < -1 \\ 2 & -1 \leq x \leq 1 \\ x + 5 & 1 < x \end{cases}$$

- b) (5 pt) Write a MATLAB code to create a square matrix ( $N \times N$ ). The matrix has diagonal elements equal  $N^3$  and all the other elements equal  $N^2$ . The input to the code is the number of element  $N$  and the output is the matrix in the matrix form.

2

**Question no. 4** (10 points).

a) (5 pt) Use a MATLAB code to solve the following set of equations:-


$$3x + 2y - z = 1$$

$$2x - 2y + 4z = -2$$

$$-x + 0.5y - z = 0$$



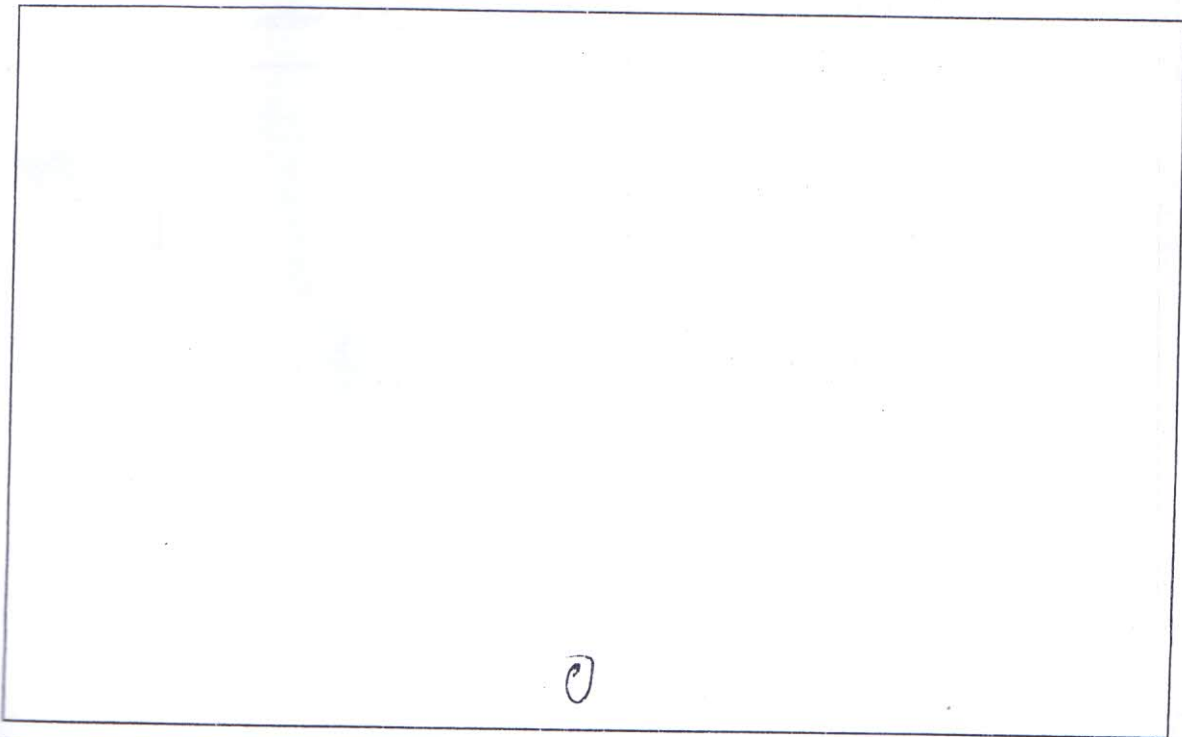b) (5 pt) Write a MATLAB code to find the factorial of any number (N). The input to the program is the number N and the output is the factorial of the number (do not use the factorial commands).



0

**Question no. 5** (9 points).

For the following two polynomials  $F_1 = 2x^4 - 5x^2 + 12x - 73$  and  $F_2 = x^2 + 3x - 9$   
Write a MATLAB commands to;

- i. Find the roots of  $F_1$  and  $F_2$ .

- ii.  $F_3 = F_1 * F_2$

- iii. The derivative of  $F_3$ .



كلية الآداب

قسم الهندسة

المادة: تاريخ مصر الاقتصادي

الفرقة: الأولى (جميع الشعب)

الزمن: ١٢٠ دقيقة

النهاية العظمى: ١٠:٠٠

امتحان الفصل الدراسي الثاني ٢٠١٤ - ٢٠١٥ م

أجب عن سؤالين فقط مما يأتي:

السؤال الأول: اكتب ما تعرفه عن سياسة الاحتكار في عهد محمد علي.

السؤال الثاني: تناول بالعرض والتحليل السياسة الاقتصادية في العهد العثماني في مصر.

السؤال الثالث: اشرح السياسة الاقتصادية للخديو إسماعيل.

السؤال الرابع: تناول بالشرح الاقتصاد المصري في العهد الملكي.

انتهت الأسئلة

مع تمنياتي بالتوفيق والنجاح

د. محمد سعد الدين

د. حامد مشهور



كلية الآداب

قسم الهندسة

المادة: تاريخ مصر الاقتصادي

الفرقة: الأولى (جميع الشعب)

الزمن: ساعتان

النهاية العظمى: ٤٠ > ٥٥

امتحان الفصل الدراسي الثاني ٢٠١٤ - ٢٠١٥ م

أجب عن سؤالين فقط مما يأتي:

السؤال الأول: اكتب ما تعرفه عن سياسة الاحتكار في عهد محمد علي.

السؤال الثاني: تناول بالعرض والتحليل السياسة الاقتصادية في العهد العثماني في مصر.

السؤال الثالث: اشرح السياسة الاقتصادية للخديو إسماعيل.

السؤال الرابع: تناول بالشرح الاقتصاد المصري في العهد الملكي.

انتهت الأسئلة

مع تمنياتي بالتوفيق والنجاح

د. محمد سعد الدين

د. حامد مشهور



Model Answer

**Attempt all questions, full mark: 20**


**Question #1 [6 Points]**

Choose the right answer:

- 1) If a transistor with higher  $\beta_{dc}$  is used in the circuit shown, The base current will

C

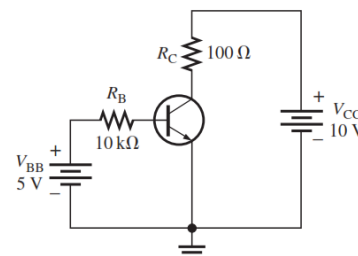- (A) increase (B) decrease  
(C) not change



- 2) In a certain voltage-divider biased *npn* transistor,  $V_B$  is 2.95 V. The dc emitter voltage is approximately

B

- (A) 0.7 V (B) 2.25 V  
(C) 2.95 V (D) 3.65 V

- 3) For operation as an amplifier, the base of an *npn* transistor must be

A

- (A) positive with respect to the emitter (B) negative with respect to the emitter  
(C) positive with respect to the collector (D) 0 V

- 4) For a common-emitter amplifier,  $R_C = 1 \text{ K}\Omega$ ,  $R_E$  is completely bypassed at the operating frequency,  $r_e' = 15 \Omega$ , and  $\beta_{ac} = 75$ . The magnitude of the voltage gain is

A

- (A) 66.7 (B) 2.56  
(C) 2.47 (D) 75

- 5) For a common-collector amplifier,  $R_E = 100 \Omega$ ,  $r_e' = 10 \Omega$ , and  $\beta_{ac} = 150$ . The ac input resistance at the base is

D

- (A) 1500  $\Omega$  (B) 15  $\Omega$   
(C) 110  $\Omega$  (D) 16.5 K $\Omega$

- 6) In a voltage-divider biased *npn* transistor, if the upper voltage-divider resistor (the one connected to  $V_{CC}$ ) opens,

A

- (A) the transistor goes into cutoff (B) the transistor goes into saturation  
(C) the transistor burns out (D) the collector current will decrease

**Question #2 [4 Points]**

Give the right answer:

- a) In a Darlington pair configuration, each transistor has  $\beta_{ac} = 80$ . If  $R_E$  is 330  $\Omega$ . Find the input resistance.

$$R_{in} = \beta_{ac}^2 \cdot R_E = 2.1 \text{ M}\Omega$$

- b) A differential amplifier stage has collector resistors of 5.1 K $\Omega$  each. If  $I_{C1} = 1.35 \text{ mA}$  and  $I_{C2} = 1.29 \text{ mA}$ , what is the differential output voltage?

$$V_o = (I_{C1} - I_{C2}) R_C = 0.306 \text{ V}$$

**Question #3** [5 Points]

The silicon npn transistor used in the common emitter amplifier in Fig.3 has  $\beta_{dc} = \beta_{ac} = 100$ .

- a) Find  $I_{CQ}$  and  $V_{CEQ}$ . (2 Points)
- b) Find  $r_e'$ . (1 Point)
- c) Find the voltage gain and input impedance of the amplifier. (2 Points)

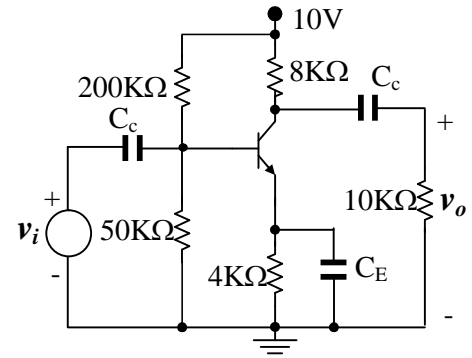


Fig.3

$I_{CQ} = 0.3 \text{ mA}$	$V_{CEQ} = 6.5 \text{ V}$	$r_e' = 83 \text{ h}$
$A_v = -54$	$Z_{in} = 6.9 \text{ Kh}$	

**Question #4** [5 Points]

The silicon npn transistor used in the common base amplifier of Fig.4 has  $\beta_{dc} = \beta_{ac} = 200$  and  $r_e' = 2.4 \Omega$  at the operating point.

- a) Draw the r-parameter ac-equivalent circuit of the amplifier. (2 Points)
- b) Find the voltage gain, current gain and input impedance of the amplifier. (3 Points)


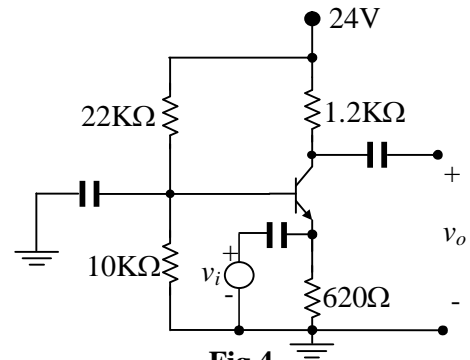


Fig.4

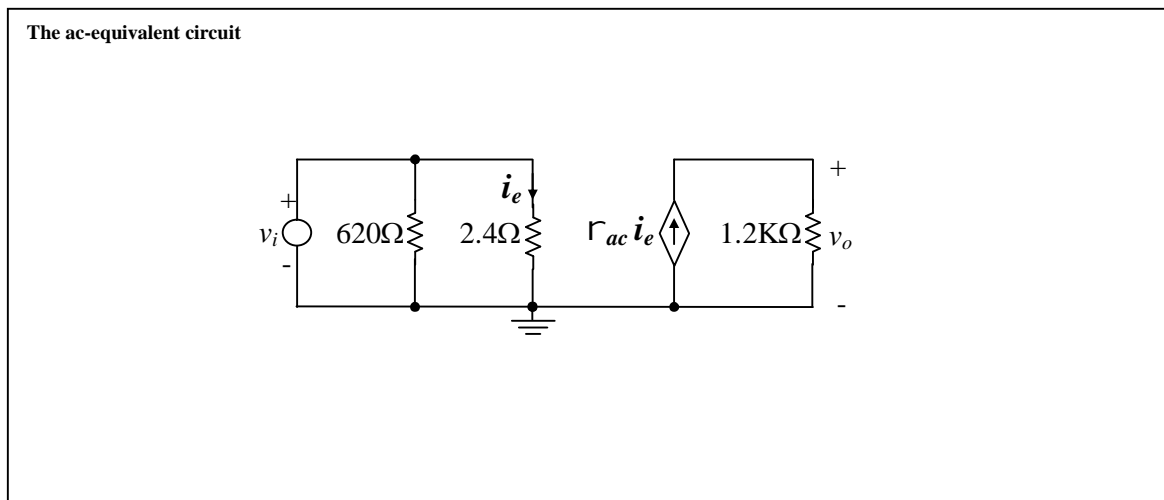

$A_v = 500$	$A_i = 0.995$	$Z_{in} = 2.39 \text{ h}$
-------------	---------------	---------------------------



**Attempt all questions, full mark: 40 Points**

**Time: 3 Hours**

**Question #1: (10 Points)**

Choose the right answer:

- 1) The overall voltage gain of three identical cascaded voltage amplifiers each has a no load voltage gain  $A_V = -10$ ,  $Z_i = 1 \text{ k}\Omega$ , and  $Z_o = 1 \text{ k}\Omega$  is:

**C** (A) 1000 (B) -1000

(C) -250 (D) -125

- 2) In cutoff,  $V_{CE}$  is

**C** (A) 0 V (B) minimum

(C) equal to  $V_{CC}$  (D) equal to  $V_{CC} - 0.7\text{V}$

- 3) In saturation,  $V_{CE}$  is

**B** (A) 0.7 V (B) minimum

(C) equal to  $V_{CC}$  (D) maximum

- 4) The peak current a class A power amplifier can deliver to a load depends on the

**B** (A) maximum rating of the power supply (B) quiescent current

(C) current in the bias resistors (D) size of the heat sink

- 5) Crossover distortion is a problem for

**C** (A) class A amplifiers (B) class AB amplifiers

(C) class B amplifiers (D) all of these amplifiers

- 6) For maximum output, a class A power amplifier must maintain a value of quiescent current that is

**A** (A) one-half the peak load current (B) twice the peak load current

(C) just above the cutoff value (D) at least as large as the peak load current

- 7) At cutoff, the JFET channel is

**B** (A) at its widest point (B) completely closed by the depletion region

(C) extremely narrow (D) reverse-biased

- 8) A MOSFET differs from a JFET mainly because

**C** (A) of the power rating (B) the MOSFET has two gates

(C) the JFET has a  $pn$  junction (D) MOSFETs do not have a physical channel

- 9) A JFET always operates with

**B** (A) the drain connected to ground (B) the gate-to-source  $pn$  junction reverse-biased

(C) the gate connected to the source (D) the gate-to-source  $pn$  junction forward-biased


- 10) A certain D-MOSFET is biased at  $V_{GS} = 0 \text{ V}$ . Its datasheet specifies  $I_{DSS} = 20 \text{ mA}$  and  $V_{GS(off)} = -5 \text{ V}$ . The value of the drain current

**C** (A) is 0 A (B) is 10 mA

(C) is 20 mA (D) cannot be determined

**Question #2: (10 Points)**

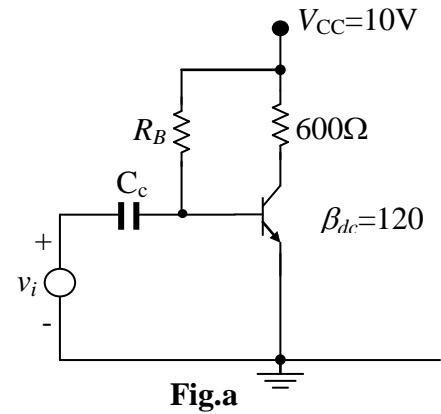- a) Assume that you wish to bias the transistor in Fig.a with  $I_C = 8 \text{ mA}$ . Find  $R_B$ .



$$I_B = I_C / \beta_{dc} = 66.7 \mu\text{A}$$

$$R_b = (V_{CC} - V_{BE}) / I_B = 139.5 \text{ K}\Omega$$

- b) In a common-emitter amplifier with voltage-divider bias,  $R_{in(base)} = 68 \text{ K}\Omega$ ,  $R_1 = 60 \text{ K}\Omega$ ,  $R_2 = 30 \text{ K}\Omega$ . Find the total ac input resistance

$$R_{in} = R_{in(base)} // R_1 // R_2$$

$$= 15.45 \text{ K}\Omega$$

- c) A differential amplifier has a differential mode gain  $A_d = 80$  and a common mode gain  $A_c = 0.5$ . Calculate the CMRR in dBs.

$$\text{CMRR} = 20 \log (A_d / A_c)$$

$$= 44 \text{ dBs}$$

- d) An n-channel E-MOSFET has  $I_{D(on)} = 18 \text{ mA}$  at  $V_{GS} = 4 \text{ V}$ , and  $V_{GS(th)} = 2.5 \text{ V}$ . Find  $I_D$  when  $V_{GS} = 3.25 \text{ V}$ .

$$I_D = k (V_{GS} - V_{th})^2$$

$$k = 8 \text{ mA/V}^2$$

$$I_D = 4.5 \text{ mA}$$



- e) In a certain common-source (CS) amplifier,  $R_D = 1.0 \text{ k}\Omega$ ,  $R_S = 560 \Omega$ ,  $V_{DD} = 10 \text{ V}$ , and  $g_m = 4500 \mu\text{S}$ . If the source resistor is completely bypassed. Find the voltage gain.

$$A_v = -g_m R_D = -4.5$$

**Question #3: (8 Points)**

A CE amplifier uses a silicon npn-transistor having  $\beta_{dc} = \beta_{ac} = 100$  and has  $R_C = 1\text{ k}\Omega$ ,  $R_E = 500\ \Omega$  and  $V_{CC} = 12\text{ volts}$ , is biased by a voltage divider with  $R_1 = 30\text{ k}\Omega$  and  $R_2 = 15\text{ k}\Omega$ . A  $1\text{ k}\Omega$  resistive load is connected through coupling capacitor to the collector terminal, and  $R_E$  is bypassed by  $C_E$ .

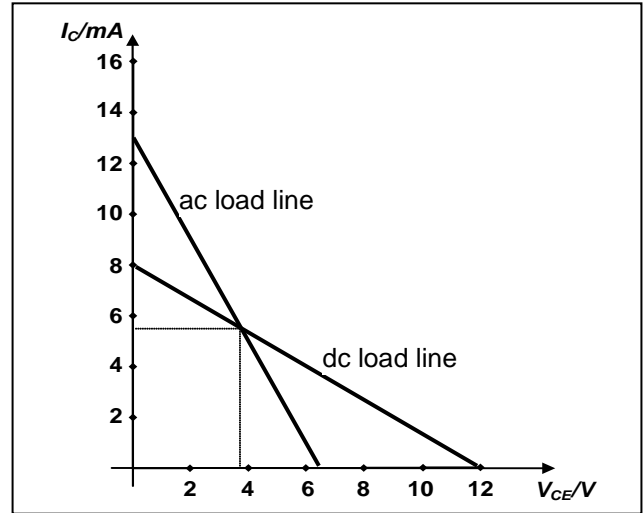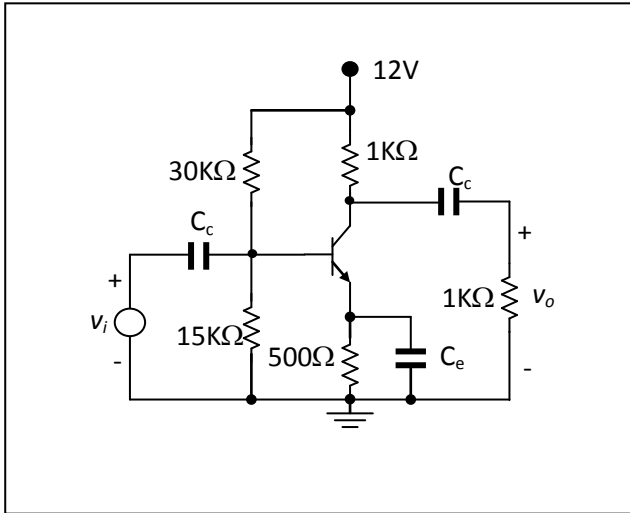- a) Draw the amplifier circuit diagram (1 Point)
- b) Find  $I_{CQ}$  and  $V_{CEQ}$ . (2 Points)
- c) Find  $r'_e$ . (1 Point)
- d) Find the voltage gain, current gain and input impedance of the circuit. (2 Points)
- e) Sketch the dc and ac load lines (2 Points)




$I_{CQ} =$ <span style="border: 1px solid black; padding: 5px; display: inline-block;">5.5 mA</span>	$V_{CEQ} =$ <span style="border: 1px solid black; padding: 5px; display: inline-block;">3.75 V</span>	$r'_e =$ <span style="border: 1px solid black; padding: 5px; display: inline-block;">4.55 <math>\Omega</math></span>
$A_v =$ <span style="border: 1px solid black; padding: 5px; display: inline-block;">- 110</span>	$A_i =$ <span style="border: 1px solid black; padding: 5px; display: inline-block;">100</span>	$Z_{in} =$ <span style="border: 1px solid black; padding: 5px; display: inline-block;">439 <math>\Omega</math></span>

**Question #4: (4 Points)**

The class AB amplifier in Fig.4 is operating with a single power supply.

- a) Assuming the input peak-to-peak voltage is 10 V; determine the power delivered to the load resistor and the amplifier efficiency. (2 Marks)
- b) What is the maximum power that could be delivered to the load resistor? (1 Mark)
- c) Assume the power supply voltage is raised to 30 V. What is the new maximum power that could be delivered to the load resistor? (1 Mark)

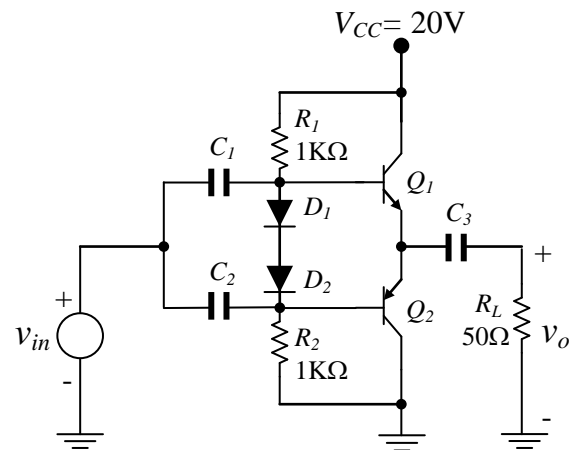


**Fig.4**

a) $P_{LD} =$ <span style="border: 1px solid black; padding: 5px; display: inline-block;">0.25 W</span>	$\text{Efficiency} =$ <span style="border: 1px solid black; padding: 5px; display: inline-block;">39.27 %</span>	
b) $P_{LD(max)} =$ <span style="border: 1px solid black; padding: 5px; display: inline-block;">1 W</span>		
c) $P_{LD(max)} =$ <span style="border: 1px solid black; padding: 5px; display: inline-block;">2.25 W</span>		

**Question #5: (8 Points)**

The JFET used in the circuit shown in Fig.5 has  $I_{DSS} = 4 \text{ mA}$ , and  $V_{GS(off)} = -2 \text{ volts}$ . Find:

- a) The Q-point parameters ( $V_{GSQ}$ ,  $I_{DQ}$ , and  $V_{DSQ}$ ). (3 points)
- b) The forward transconductance  $g_m$  at the Q-point. (1 point)
- c) The voltage gain, input and output resistances. (2 points)
- d) If it is desired to bias the above FET at the midpoint of its transfer characteristics ( $I_D = I_{DSS}/2$ ) and at  $V_{DS} = V_{DD}/2$ . Find the new values of  $R_s$  and  $R_d$ . (2 points)

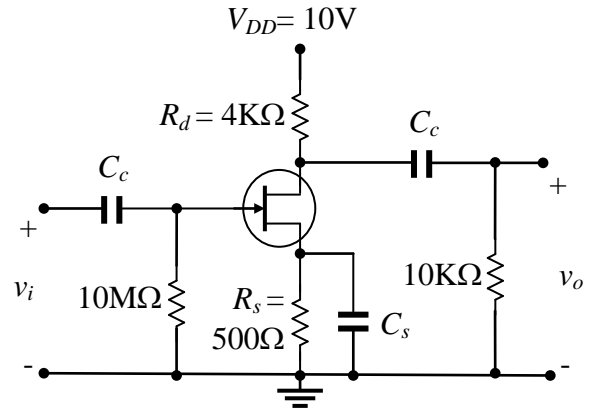

**Fig.5**

- |  |   |   |
|--|---|---|
| a) $V_{GSQ} =$ <span style="border: 1px solid black; padding: 5px; display: inline-block; min-width: 150px;">- 0.76 V</span> | $I_{DQ} =$ <span style="border: 1px solid black; padding: 5px; display: inline-block; min-width: 150px;">1.53 mA</span> | $V_{DSQ} =$ <span style="border: 1px solid black; padding: 5px; display: inline-block; min-width: 150px;">3.12 V</span> |
| b) $g_m =$ <span style="border: 1px solid black; padding: 5px; display: inline-block; min-width: 150px;">2.47 mS</span>      |   |   |
| c) $A_v =$ <span style="border: 1px solid black; padding: 5px; display: inline-block; min-width: 150px;">- 7.1</span>        | $Z_{in} =$ <span style="border: 1px solid black; padding: 5px; display: inline-block; min-width: 150px;">10 MΩ</span>   | $Z_{out} =$ <span style="border: 1px solid black; padding: 5px; display: inline-block; min-width: 150px;">4 KΩ</span>   |
| d) $R_s =$ <span style="border: 1px solid black; padding: 5px; display: inline-block; min-width: 150px;">294 Ω</span>        | $R_d =$ <span style="border: 1px solid black; padding: 5px; display: inline-block; min-width: 150px;">2.2 KΩ</span>     |   |

\*\*\*\*\* Best Wishes \*\*\*\*\*  
Prof. Magdy M. Doss



**Attempt all questions, full mark: 40 Points**

**Time: 3 Hours**

**Question #1: (10 Points)**

Choose the right answer:

- 1) If a sinusoidal voltage is applied to the base of a biased npn transistor and the resulting sinusoidal collector voltage is clipped near zero volts, the transistor is

**A** (A) being driven into saturation (B) being driven into cutoff  
(C) operating nonlinearly

- 2) The input resistance of a common-base amplifier is

**A** (A) very low (B) very high  
(C) the same as a CE (D) the same as a CC

- 3) The voltage gain of a common-base amplifier is

**C** (A) very low (B) very high  
(C) the same as a CE (D) the same as a CC

- 4) The input resistance at the base of a biased transistor depends mainly on

**D** (A)  $\beta$  (B)  $R_E$   
(C)  $R_B$  (D)  $\beta$  and  $R_E$

- 5) A differential amplifier

**D** (A) is used in op-amps (B) has one input and one output  
(C) has two outputs (D) answers (A) and (C)

- 6) The maximum efficiency of a class A power amplifier is

**A** (A) 25% (B) 50%  
(C) 75% (D) 78.5%

- 7) Crossover distortion is a problem for

**C** (A) class A amplifiers (B) class AB amplifiers  
(C) class B amplifiers (D) all of these amplifiers

- 8) For  $V_{GS}=0$ , the drain current in a JFET becomes constant when  $V_{DS}$  exceeds

**C** (A) cutoff (B)  $V_{DD}$   
(C)  $V_P$  (D) 0 V

- 9) A certain n-channel E-MOSFET has a  $V_{GS(th)}=2V$ . If  $V_{GS}=0V$ , the drain current is

**A** (A) 0 A (B)  $I_{D(ON)}$   
(C) maximum (D)  $I_{DSS}$

- 10) Which of the following characteristics does not necessarily apply to an op-amp?

**B** (A) High gain (B) Low power  
(C) High input impedance (D) Low output impedance

**Question #2: (5 Points)**



a) A certain transistor has  $\alpha_{DC} = 0.99$ . If the dc base current is  $10 \mu\text{A}$ , determine  $r_e'$ .

$$\beta = \alpha / (1 - \alpha) = 99$$

$$I_E = (\beta + 1)I_B = 1 \text{ mA}$$

$$r_e' = 25 / I_E = 25 \Omega$$

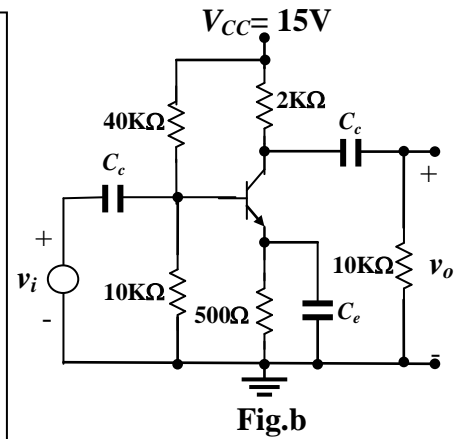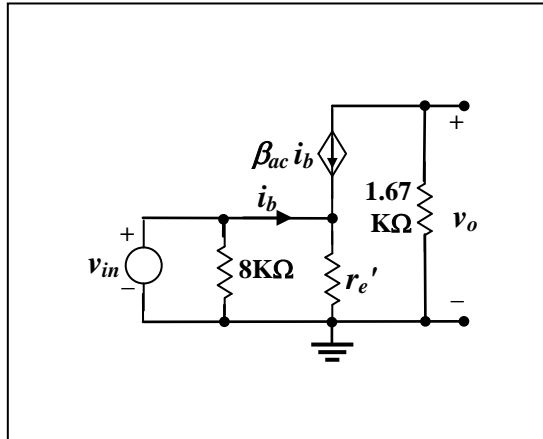b) Draw the ac equivalent circuit for the amplifier in Fig.b



c) An n-channel JFET has  $I_{DSS} = 5 \text{ mA}$  and  $V_{GS(off)} = -8 \text{ V}$ . What value of  $V_{GS}$  is required to set up a drain current of  $2.25 \text{ mA}$ .

$$I_D = 5[1 - V_{GS}/(-8)]^2 = 2.25$$

$$V_{GS} = -2.63 \text{ V}$$


d) A certain class A power amplifier has  $V_{CEQ} = 12 \text{ V}$  and  $I_{CQ} = 1 \text{ A}$ . Find the maximum signal power output.

$$P_{out(max)} = V_{CEQ}I_{CQ}/2$$

$$= 6 \text{ W}$$

e) Find  $V_o$  in the circuit of Fig.(e).

$$V_o = -18 \text{ V}$$

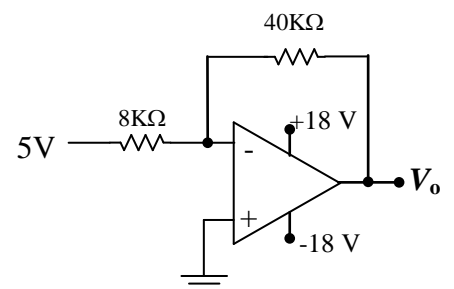

**Fig.(e)**



**Question #3: (5 Points)**

The silicon npn transistor used in the swamped amplifier shown in Fig.3 has  $\beta_{dc} = \beta_{ac} = 100$ .

- Find  $I_{CQ}$  and  $V_{CEQ}$ .
- Find  $r_e'$ .
- Find the voltage gain and input impedance of the amplifier.

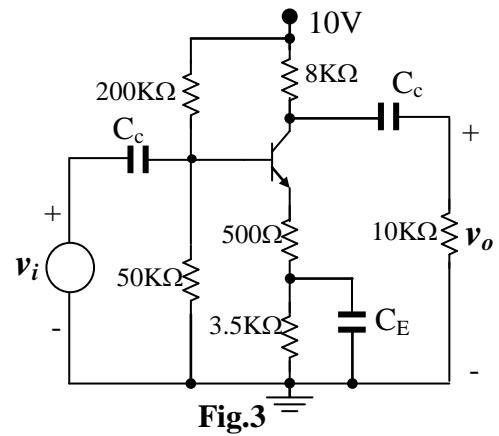


Fig.3

$I_{CQ} = 0.295 \text{ mA}$

$V_{CEQ} = 6.45 \text{ V}$

$r_e' = 84.6 \Omega$

$A_v = -7.6$

$Z_{in} = 23.75 \text{ K}\Omega$

**Question #4: (5 Points)**

A class-AB complementary-symmetry push-pull power amplifier is connected to a  $6 \Omega$  load. The supply voltages are  $\pm 24 \text{ V}$ .

- Draw the amplifier circuit diagram. (1 Point)
- Find the peak value of the collector current, the DC power delivered by the source, and the amplifier efficiency if the ac power delivered to the load is  $27 \text{ W}$ . (3 Points)
- What would be the maximum allowable output power? (1 Point)


$I_{Cp} = 3 \text{ A}$

$P_{DC} = 45.83 \text{ W}$

**Efficiency = 58.9%**

$P_{out(max)} = 48 \text{ W}$

The Circuit Diagram

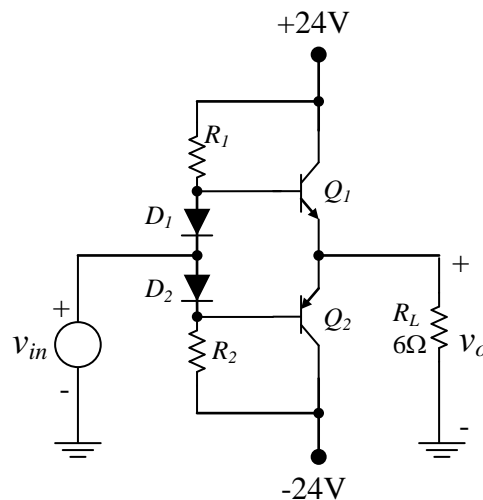

**Question #5: (5 Points)**

The JFET used in the common source amplifier of Fig.5 has  $V_{GS(off)} = -5V$  and  $I_{DSS} = 10\text{ mA}$ .

- a) Determine the operating point  $I_{DQ}$ ,  $V_{GSQ}$  and  $V_{DSQ}$ . (3 Points)
- b) Calculate the value of the transconductance  $g_m$  at the  $Q$ -point. (1 Point)
- c) Determine the amplifier voltage gain. (1 Point)

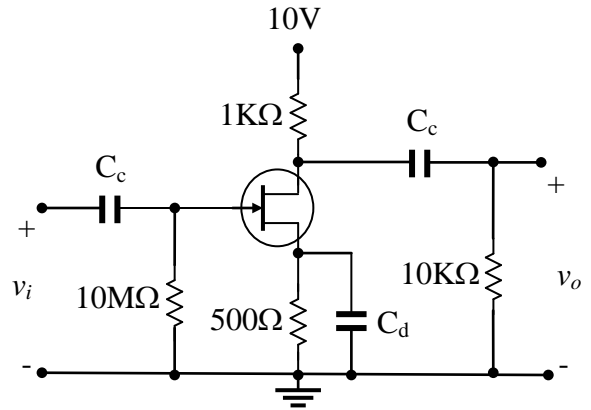


Fig.5

$I_{DQ} = 3.82\text{ mA}$

$V_{GSQ} = -1.91\text{ V}$

$V_{DSQ} = 4.27\text{ V}$

$g_m = 2.47\text{ mS}$


$A_v = -2.247$

**Question #6: (3 Points)**

- a) The data sheet for a 2N7008 E-MOSFET gives  $I_{D(on)} = 500\text{ mA}$  at  $V_{GS} = 10\text{ V}$  and  $V_{GS(th)} = 1\text{ V}$ . Determine the drain current for  $V_{GS} = 5\text{ V}$ . (1 Point)
- b) The transistor is to operate at:  $V_{GSQ} = 5\text{ V}$ ,  $V_{DSQ} = 10V$ . Draw a suitable circuit to bias this transistor giving suitable resistances values, assuming that  $V_{DD} = 15V$ . (2 Points)

$I_D = 98.765\text{ mA}$

The Circuit Diagram

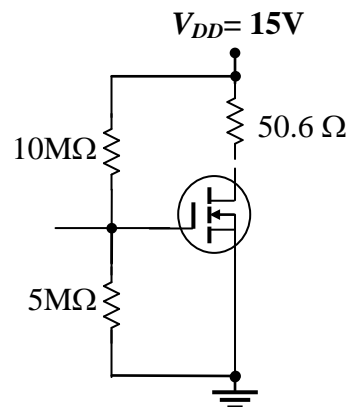

**Question #7: (3 Points)**

- a) Find the output voltage when the indicated input voltages are applied to the scaling adder of Fig.7. (2 Points)
- b) What is the value of the current through  $R_f$ ? (1 Point)

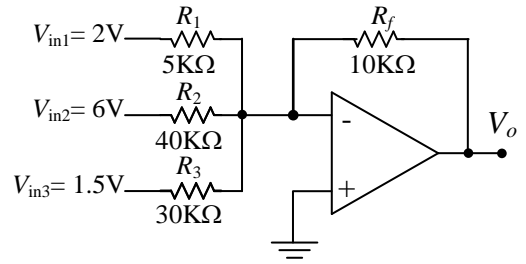


Fig.7

$V_o = -6 \text{ V}$

$I_f = 0.6 \text{ mA}$

**Question #8: (4 Points)**

The voltage waveform  $v_g$  shown in Fig.(8-a) is applied to the circuit of Fig.(8-b). Sketch  $v_o$  versus  $t$ , assuming ideal op-amp.

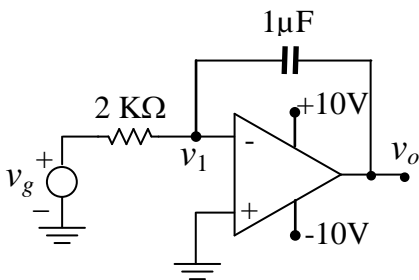


Fig. (8-b)

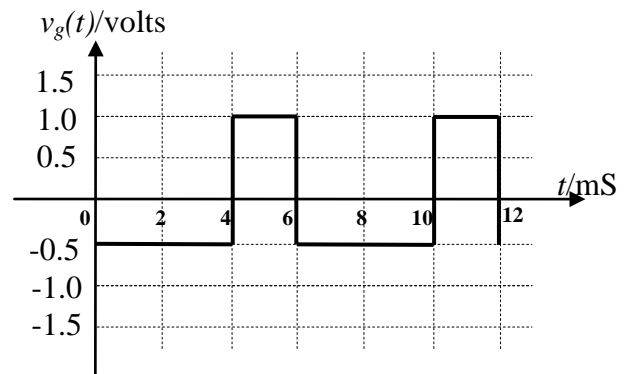


Fig. (8-a)

